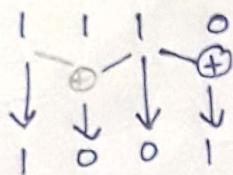


Note:


BINARY TO GRAY

(2m)



- 1st no as it is
- next nos take x. or y

GRAY TO BINARY

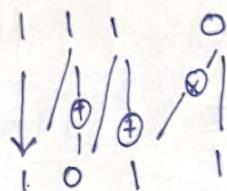

→ next ~~ans~~ value
take $x \text{-or}$.

5. convert binary 1101110 \Rightarrow gray code

$$\begin{array}{r} 1101110 \\ \downarrow \\ \hline 1011001 \end{array} \Rightarrow \text{gray code.}$$

6. Reduce the boolean expression using Boolean law.

$$A. \quad (A' + c)(A' + c') (A + B + c'D)$$

Using distribution law

$$(A' + CC')^o (A + B + C'D)$$

$$(A' + c') \downarrow$$

$$= A' (A + B + C'D)$$

$$= A' \cancel{A} + A'B + A'C'D$$

$$= A'B + A'C'D$$


$$= A'(B + C'D)$$

Implementation Using logic gates:

ONLY USING [NAND] AND [NOR]

$$Y = A'B + A'C'D$$
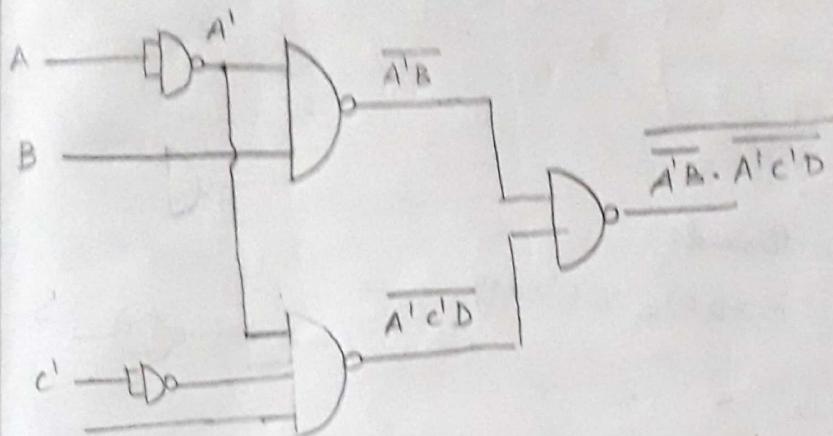
$$\overline{Y} = \overline{\overline{A'}B \cdot \overline{A'}C'D} \Rightarrow \text{only using NAND}$$



\Rightarrow only using NOR

$$Y = A'B + A'C'D$$


$$Y = \overline{\overline{A'}B \cdot \overline{A'}C'D}$$

$$Y = (\overline{A'} + \overline{B}) \cdot (\overline{A'} + \overline{C'} + \overline{D})$$

$$= (\overline{A} + \overline{B}) \cdot (\overline{A} + \overline{C} + \overline{D})$$

$$= (\overline{A} + \overline{B}) + \overline{\overline{A} + \overline{C} + \overline{D}}$$
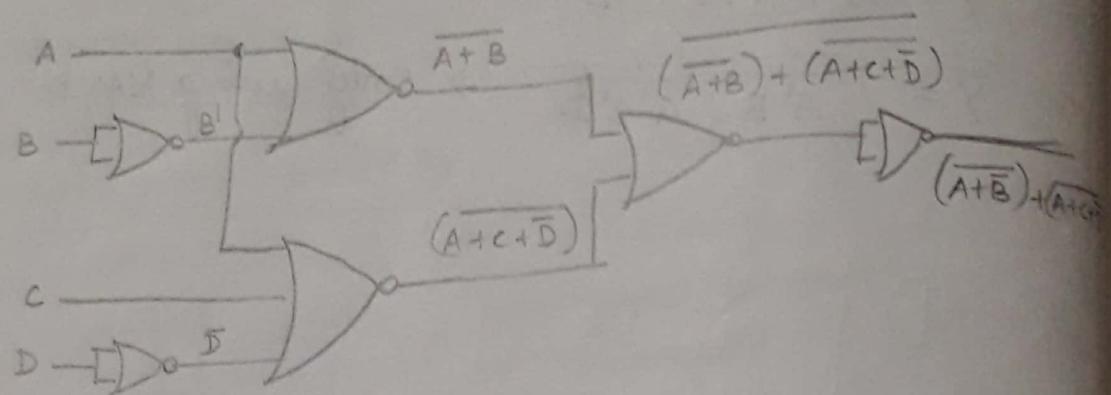
$$y = \overline{(A+B)} + (\overline{A+C+D})$$



1. (B) continued:

$(C3DF)_{16}$ to binary.

(hexa \rightarrow decimal)

$$\begin{array}{cccc}
 12 & 3 & 13 & 15 \\
 | & | & | & | \\
 & & & \xrightarrow{15 \times 16^0 = 15} \\
 & & & \xrightarrow{13 \times 16^1 = 208} \\
 & & & \xrightarrow{3 \times 16^2 = 768} \\
 & & & \xrightarrow{12 \times 16^3 = 49,152} \\
 & & & \hline
 & & & \underline{(50143)_{10}}
 \end{array}$$

(decimal \rightarrow binary)

- Repeated division by 2

$$2 | \underline{50143}$$

$$\text{Ans} \Rightarrow (1100 \ 0011 \ 1101 \ 1111)_2$$

decimal to binary

2	50143	
2	25071 - 1	
2	12535 - 1	
2	6267 - 1	
2	3133 - 1	$\Rightarrow (110000111101111)_2$
2	1566 - 1	
2	783 - 0	
2	391 - 1	
2	195 - 1	
2	97 - 1	
2	48 - 1	
2	24 - 0	
2	12 - 0	
2	6 - 0	
2	3 - 0	
	1 - 01	

7. Express the function

$(cd + b'c + bd')(b+d)$ sum of min terms &
pdts of max terms (CANONICAL FORM)

$$\Rightarrow (cd + b'c + bd')(b+d)$$

sum of min terms:-

$$\begin{aligned}
 F &= \cancel{bcd} + \cancel{bb'c}^{\cancel{0}} + \cancel{bd'}^{\cancel{0}} + cd + b'cd + \cancel{b'dd'}^{\cancel{0}} \\
 &= bcd + b(c+c')d' + (b+b')cd + b'cd \\
 &= bcd + bcd' + bc'd' + \cancel{bcd} + \cancel{b'cd} + \cancel{bc'd} \\
 &\quad \begin{matrix} 111 & 110 & 100 & + & 011 \\ 7 & 6 & 4 & & 3 \end{matrix} \\
 &\Sigma_m (3, 4, 6, 7)
 \end{aligned}$$

Pdt of max terms:-

8. Convert

$$A.) F(x,y,z) = \leq (1,3,5) \\ = \pi(0,2,4,6,7)$$

$$\begin{aligned}
 B) \quad f(A, B, C, D) &= \pi(3, 5, 8, 11) \\
 &= \{0, 1, 2, 4, 6, 7, 9, 10, 12, 13, 14, 15\} \\
 &= \{0, 1, 2, 4, 6, 7, 9, A, C, D, E, F\}
 \end{aligned}$$

9. convert:

- A. $(u+xw)(x+u'v)$ into sum of pdt and pdt of sum [standard form]

sum of pdt:

$$\begin{aligned} & (u+xw)(x+u'v) \\ &= \cancel{ux + x'} \cancel{ux + u'v} v + xw x + xw u'v \\ &= ux + xw u'v + xw \leftarrow \text{sum of pdt.} \end{aligned}$$

Pdt of sum:

$$\begin{aligned} & (u+xw)(x+u'v) \quad \text{Using distribution law,} \\ & (u+xw u'v)(x+xw u'v) \\ & \Rightarrow (u+x)(u+w)(u+u')(u+v)(x+x) \\ & \quad (x+w)(x+u')(x+v) \\ & \Rightarrow (u+x)(u+w)(u+v)(x+w)(x+u')(x+v) \quad (x+w) \\ & \Rightarrow (u+x)(u+w)(x+u') \overset{\text{Pdt of sum}}{(x+v)} \end{aligned}$$

10. Reduced using k-map.

A. $F(w, x, y, z) = \Sigma(2, 3, 12, 13, 14, 15)$

w	y	z	$\bar{y}\bar{z}$	$\bar{y}z$	yz	$y\bar{z}$
$\bar{w}\bar{x}$	00	00	0	1	1 ₃	1 ₂
$\bar{w}x$	01	01	4	5	7	6
wx	11	11	1 ₂	1 ₃	1 ₅	1 ₄
w \bar{x}	10	10	8	9	11	10

$$F(w, x, y, z) = w\bar{x} + \bar{w}\bar{x}y$$

B. $F = w'z + xz + x'y + w'x'z$

$w'z$	$y'z$	$\bar{y}z$	yz	$y\bar{z}$
wz	00	01	11	10
$w\bar{x}$	00	01	11	10
$w\bar{x}'$	00	01	11	10
wx	01	11	10	00
wx'	11	10	00	01
$w\bar{x}'z$	00	01	11	10

$x'y'z'$

$$F(w, x, y, z) = z + x'y$$

10. Using tabulation method find the reduced expression:-

A. $F = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$

	A	B	C	D
1	0	0	0	1
3	0	0	1	1-2
4	0	1	0	0
5	0	1	0	1-2
10	1	0	1	0-2
11	1	0	1	1-3
12	1	1	0	0-2
13	1	1	0	1-3
14	1	1	1	0-3
15	1	1	1	1-4

	A	B	C	D	<u>Iteration-I</u>	<u>Iteration-II</u>
1	0	0	0	1	✓ (1,3) 00-1°	(4,12,5,13) -10-
4	0	1	0	0	✓ (1,5) 0-01°	(10,11,14,15) 1-1-
3	0	0	1	1	✓ (4,5) 010- ✓	(10,14,11,15) 1-1-
5	0	1	0	1	✓ (3,11) -011°	(4,5,12,13) -10-
10	1	0	1	0	✓ (5,13) -101°	(12,13,14,15) 11--
12	1	1	0	0	✓ (10,11) 101- ✓	(12,14,13,15) -11--
11	1	0	1	1	✓ (12,13) 110- ✓	
13	1	1	0	1	✓ (12,14) 11-0 ✓	
14	1	1	1	0	✓ (11,15) 1-11 ✓	
15	1	1	1	1	✓ (13,15) 11-1 ✓ (14,15) 111- ✓	(4,12,5,13) -BC (10,11,14,15) -AC (12,13,14,15) -AB


PRIME IMPLICANTS:

Min terms	P.I	1?	3?	4	5	10	11	12	13	14	15
✓(1,3)	ĀB̄D	x	x								
1,5	ĀC̄D	x			x						
3,11	Ā̄BCD		x				x				
4,12,5,13	B̄C			x	x			x	x		
10,11,14,15	AC					x	x			x	x
12,13,14,15	AB						x	x	x	x	x

$$F = \overline{A} \overline{B} \overline{D} + B \overline{C} + AC.$$

$$F = \overline{A} \overline{B} D + B \overline{C} + AC.$$

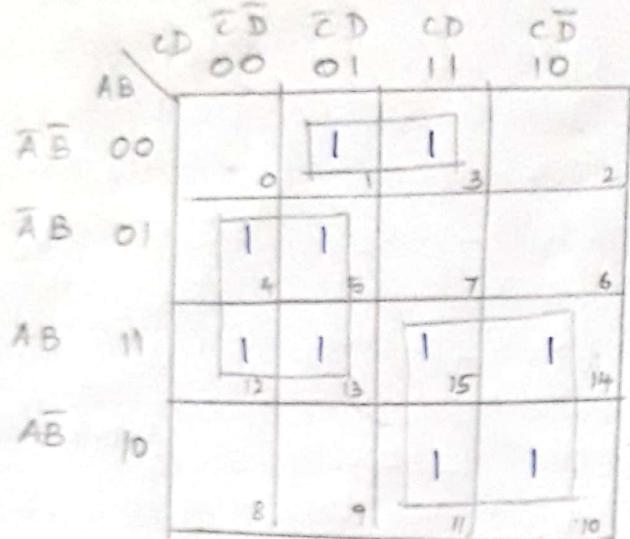Verification using K-map $F = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$



$$F = A B \bar{C} + A C + \bar{A} \bar{B} D$$

Hence Verified.

B. $F = \sum(5, 6, 7, 12, 14, 15)$
 $d = \sum(3, 9, 11)$

	A	B	C	D
3	0	0	1	1
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
9	1	0	0	1
11	1	0	1	1
12	1	1	0	0
14	1	1	1	0
15	1	1	1	1

	A	B	C	D	Iteration-1	Iteration-2
3	0	0	1	1	(3, 7) 0-11-	(3, 7, 11, 15) -11
5	0	1	0	1	(3, 11) -011	(3, 11, 7, 15) -11
6	0	1	1	0	(5, 7) 01-1	(6, 7, 14) -11
9	1	0	0	1	(6, 14) -110	(6, 14, 7, 15) -11
12	1	1	0	0	(9, 11) 10-1	
7	0	1	1	1	(12, 14) 11-D	(5, 7) $\bar{A}BD$
11	1	0	1	1	(7, 15) -111	(9, 11) $\bar{A}\bar{B}D$
14	1	1	1	0	(11, 15) 1-11	(12, 14) $AB\bar{D}$
15	1	1	1	1	(14, 15) 111-	(3, 7, 11, 15) $\rightarrow CD$
						(6, 7, 14, 15) $\rightarrow BC$

Min terms	P.I	3	5	6	7	9	11	12	14	15
$\checkmark 5, 7$	$\bar{A}BD$	(X)								
$\checkmark 9, 11$	$A\bar{B}D$									
$\checkmark 12, 14$	$AB\bar{D}$						(X)		X	
$\checkmark 3, 7, 11, 15$	CD					X				X
$\checkmark 6, 7, 14, 15$	BC		(X)	X				X	X	

$$F = \bar{A}BD + A\bar{B}\bar{D} + BC$$

AB	CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}00$					
$\bar{A}B01$					
$AB11$					
$A\bar{B}10$					
	0	1	3	2	
	4	(1)	(1)	1	
	5			7	6
	8	X		1	
	9			15	14
	10	X	X		
	11				
	12				
	13				
	14				
	15				

Verification using K-map.

$$F = BC + \bar{A}BD + AB\bar{D}$$

Hence Verified.


31.07.18

Unit - II Combinational CircuitsDigital logic circuitscombinational

- Half Adder
- Full Adder.
- Ripple carry adder
(parallel adder)
- Mux
- De Mux
- Decoder
- Encoder
- Comparator

sequential


- (Flip flops)
- Register
- Counter
- Shift register
- ALU
- Memory
- Control Unit

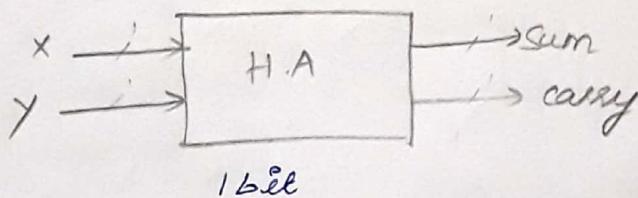Eg:- 1. Half Adder.


x	y	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = \overline{x}y + x\overline{y} = x \oplus y$$

$$\text{carry} = xy$$

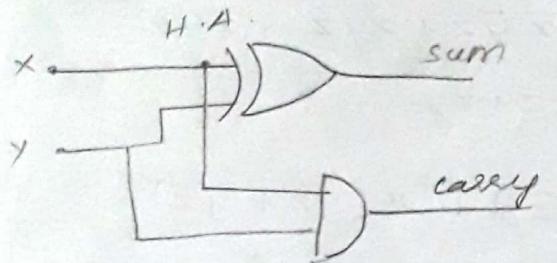

Full Adder:

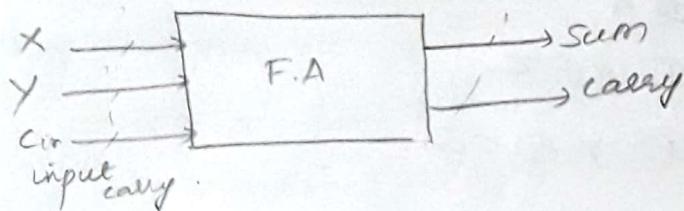

	x	y	cin	Sum	carry
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

	$\bar{y}z$	$\bar{y}z$	yz	$y\bar{z}$
$\bar{x}yz$	00	01	11	10
$\bar{x}xy$	0	1	3	2
xzy	4	5	7	6
xzx	1	1	1	1
sum				

$$F \Rightarrow S \text{ can} \Rightarrow x \bar{y} \bar{z} + \bar{x} \bar{y} z + x y z + \bar{x} y \bar{z}$$

y	80	90	11	1092
x_1	0	1	1	3
x_2	0	1	1	2
x_3	4	15	17	16

$$\text{carry} \Rightarrow \cancel{yz + xz + xy} \\ \underline{yz + xz + xy}$$

$$\text{sum: } xy\bar{z} + \bar{x}\bar{y}z + xyz + \bar{x}yz$$

$$\text{carry: } yz + xz + xy$$

$$\xrightarrow{\text{sum:}} \bar{x}(\bar{y}z + y\bar{z}) + x(yz + \bar{y}\bar{z})$$

$$\bar{x}(\underbrace{y \oplus z}_A) + x(\underbrace{y \odot z}_{\bar{A}})$$

$$= \bar{x}A + x\bar{A}$$

$$= x \oplus A$$


$$= x \oplus y \oplus z$$

$$= x \oplus y \oplus \text{cin.}$$

$$\text{carry: } yz + xz + xy$$

$$x(z+y) + yz$$

$$= xy + y \text{cin} + x \text{cin.}$$

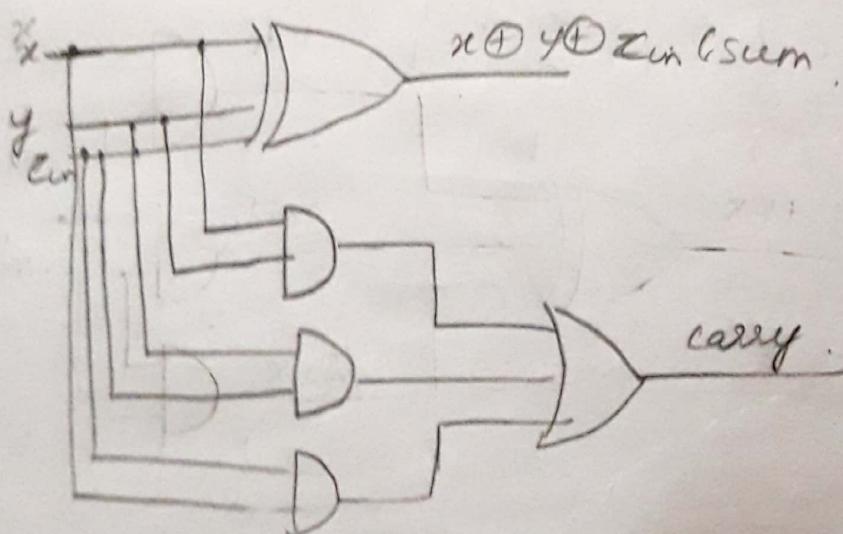

Half Adder:

1. Full Adder using 2 half adder & one OR gate.

$$\text{carry: } xy + y_{\text{cin}} + x_{\text{cin}}$$

$$= xy + (x + \bar{x})y_{\text{cin}} + x(y + \bar{y})_{\text{cin}}$$

$$= xy + x y_{\text{cin}} + \bar{x} y_{\text{cin}} + x \bar{y}_{\text{cin}} + x \bar{y} \bar{y}_{\text{cin}}$$


$$= \underbrace{xy + x y_{\text{cin}}}_{\text{sum}} + \underbrace{\bar{x} y_{\text{cin}} + x \bar{y} \bar{y}_{\text{cin}}}_{\text{carry}}$$

Using absorption law: $(A + AB = A)$

$$= xy + \text{cin}(\bar{x}y + x\bar{y})$$

$$\underline{\text{carry}} = xy + \text{cin}(x \oplus y)$$
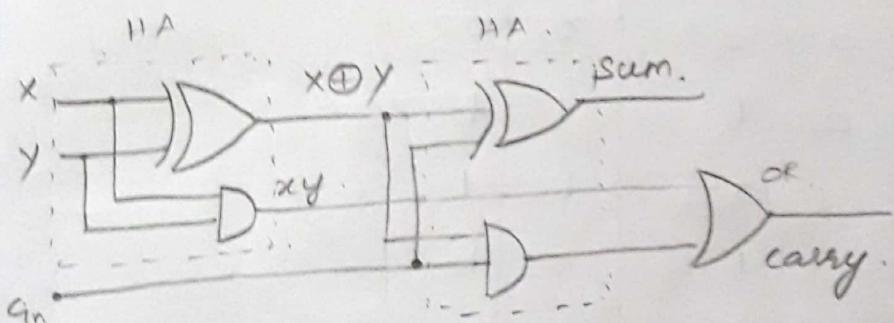
$$\underline{\text{sum}} = x \oplus y \oplus \text{cin}$$



2. Half Subtractor:

x	y	diff (D)	borrow (B)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


Difference:

$$D = \bar{x}y + x\bar{y} \\ = x \oplus y$$

$$\underline{\text{Borrow}} \\ B = \bar{x}y$$

Difference: $x \oplus y$

Borrow: $\bar{x}y$.

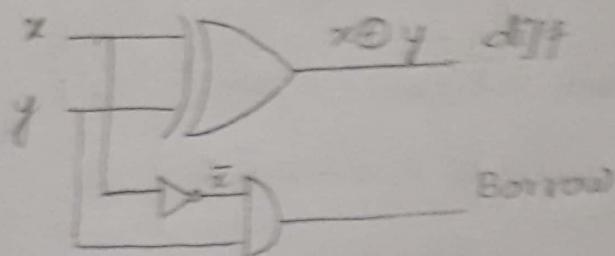

FULL SUBTRACTOR:

x	y	Cin	D	B	
0	0	0	0	0	
1	0	0	1	1	
2	0	1	0	1	
3	0	1	1	0	
4	1	0	0	1	
5	1	0	1	0	
6	1	1	0	0	
7	1	1	1	1	

$y_{in} \bar{y}_0$ \bar{y}_0 \bar{y}_1 y_c y_c \bar{y}_0 Difference

x	00	01	11	10	
00	0	1	1	0	
01	1	0	0	1	
11	4	5	7	6	

$$\text{Difference } D = x\bar{y}\bar{c}_{in} + \bar{x}\bar{y}c_{in} + xy c_{in} + \bar{x}y\bar{c}_{in}$$

$$D = \overline{x \oplus y \oplus c_{in}}$$

Borrow


	$y_{in} \bar{y}_c$ 00	\bar{y}_c 01	y_c 11	\bar{y}_c 10
x	0	1	1	1
\bar{x}			1	2
x'	4	5	7	6

$$B = \bar{x}C_{in} + \bar{x}y + y_c$$

$$\boxed{B = \cancel{\bar{x}}\bar{x}C + \bar{x}y + y_c}$$

$$= \bar{x}y + c\ell$$

2 half sub
+ R.

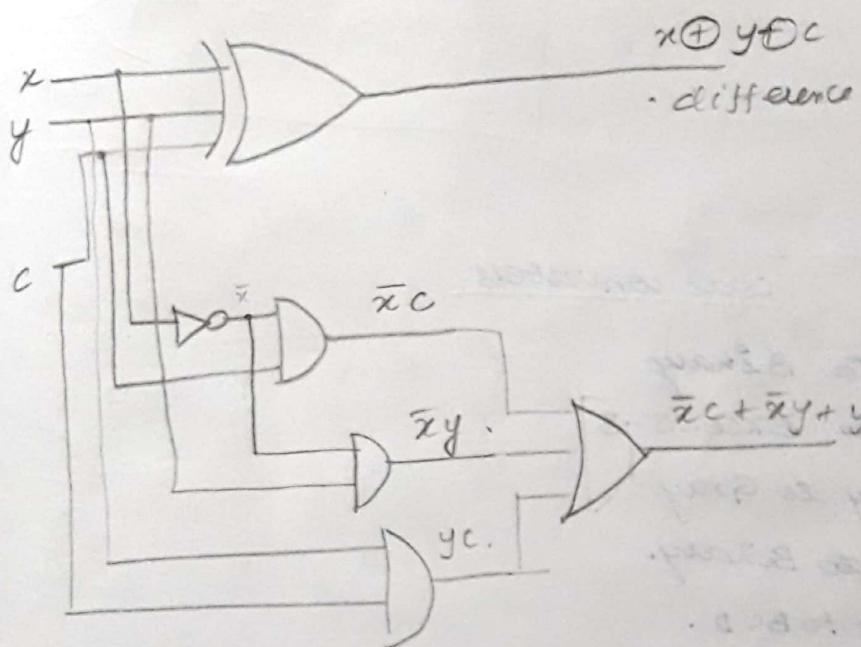

$$B = \bar{x}c + \bar{x}y + y_c$$

$$= \bar{x}y + \bar{x}(y + \bar{y})c + (x + \bar{x})y_c$$

$$= \bar{x}y + \underbrace{\bar{x}y_c}_{\cancel{\bar{x}y_c}} + \bar{x}\bar{y}c + xyc + \cancel{\bar{x}y_c}$$

~~$$\bar{x}y(\cancel{1c}) = \bar{x}y + c(\bar{x}\bar{y} + xy) + \bar{x}y_c$$~~

$$= \bar{x}y + c \odot xy + \bar{x}y_c$$

$$= \bar{x}y + \bar{x}\bar{y}c + xyc$$


$$= \bar{x}y + c(\bar{x}\bar{y} + xy)$$

~~$$= \bar{x}y + c \odot \bar{x}y (x \odot y)$$~~

$$B = \bar{x}y + c(x \odot y)$$

$$B = \bar{x}y + c(x \odot y)$$

$$D = x \oplus y \oplus c.$$

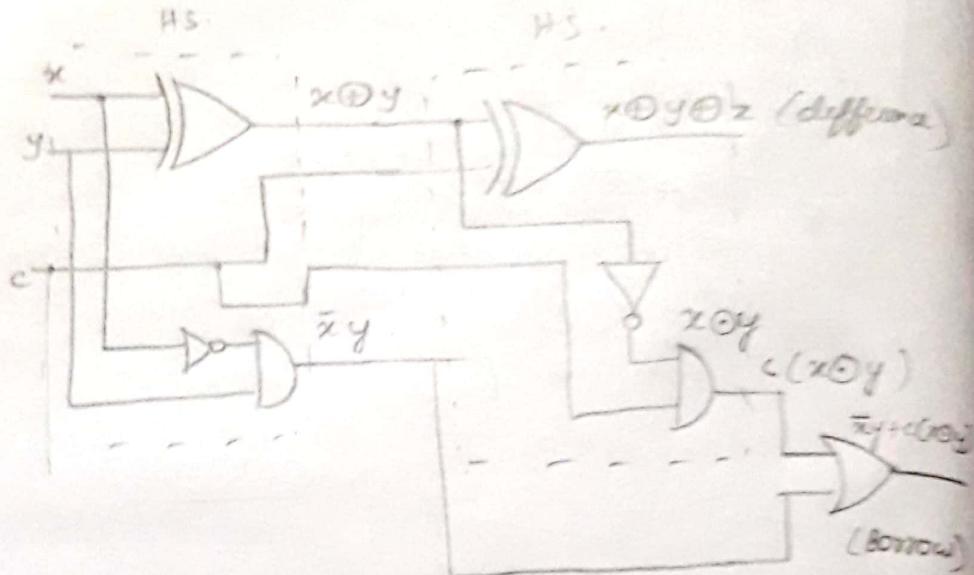

07.08.18

Code converters

1. BCD to Binary
2. BCD to EXCESS-3
3. Binary to Gray
4. Gray to Binary.
5. Binary to BCD.
6. Excess-3 to Binary.

I.	BCD	BINARY
	A ₃ A ₂ A ₁ A ₀	B ₃ B ₂ B ₁ B ₀
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 0
3	0 0 1 1	0 0 1 1
4	0 1 0 0	0 1 0 0
5	0 1 0 1	0 1 0 1
6	0 1 1 0	0 1 1 0
7	0 1 1 1	0 1 1 1
8	1 0 0 0	1 0 0 0
9	1 0 0 1	1 0 0 1
	4 0 1 0	
	1 0 1 1	
	1 0 1 0 0	
	1 1 0 1	
	1 1 1 0	
	1 1 1 1	

Don't care
nos.

BCD				A ₃ A ₂ A ₁ A ₀
0	0	0	0	0000
0	0	0	1	0001
0	0	1	0	0010
0	0	1	1	0011
0	1	0	0	0100
0				

BINARY

Draw K-maps for B₃ B₂ B₁ B₀

For B₃

		B ₃ A ₃ A ₂ A ₁ A ₀				
		00	01	11	10	
		00	0	0	0	0
		01	0	0	0	0
		11	X	X	X	X
		10	1	1	X	X

$$\boxed{B_3 = A_3}$$

BCD Excess 3.

BCD				E ₃ E ₂ E ₁ E ₀
0	0	0	0	0011
1	0	0	1	0100
2	0	0	10	0101
3	0	0	11	0110
4	0	1	0	0111
5	0	1	01	1000
6	0	1	10	1001
7	0	1	11	1010
8	1	0	0	1011
9	1	0	1	1100

K-map

		E ₃ A ₃ A ₂ A ₁ A ₀				
		00	01	11	10	
		00	0	0	0	0
		01	0	1	1	1
		11	X	X	X	X
		10	1	1	X	X

$$E_3 = A_3 + A_2 A_0 + A_2 A_1$$

$$= A_3 + A_2 (A_0 + A_1)$$

K-map for E₂.

		E ₂ A ₃ A ₂ A ₁ A ₀				
		00	01	11	10	
		00	1	1	1	1
		01	1	0	0	0
		11	X	X	X	X
		10	0	1	X	X

$$E_2 = \cancel{A_3 A_2} + \bar{A}_2 A_1 + \bar{A}_3 \bar{A}_2 \\ A_0 \bar{A}_2 + A_2 \bar{A}_1 \bar{A}_0$$

K map for E₀

		A ₃ A ₂	A ₁ A ₀		
		00	01	11	10
		00	1 0 1 0	1 0 1 1	1 0 1 2
		01	1 0 0 0	1 0 0 1	1 0 0 6
		11	X 12 X 13 X 15 X 14	X 13 X 15 X 14	X 14
		10	1 0 X 11	X 11 X 10	X 10

$$E_0 = \bar{A}_1 \bar{A}_0 + A_1 \bar{A}_0$$

$$E_0 = \bar{A}_0 (\bar{A}_1 + A_1)$$

K map for E₁

		A ₃ A ₂	A ₁ A ₀		
		00	01	11	10
		00	1 0 1 0	1 0 1 0	1 0 1 2
		01	1 0 0 0	1 0 0 1	1 0 0 6
		11	X 12 X 13 X 15	X 13 X 15 X 14	X 14
		10	1 0 X 11	X 11 X 10	X 10

$$E_1 = \bar{A}_1 \bar{A}_0 + A_1 A_0$$


~~$$E_3 = A_3 + A_2 (\bar{A}_1 + A_1)$$~~

$$E_2 = \bar{A}_2 (A_1 + A_0) + \bar{A}_1 \bar{A}_0 A_2$$

$$E_1 = \bar{A}_1 \bar{A}_0 + A_1 A_0$$

$$E_0 = \bar{A}_0 (\bar{A}_1 + A_1)$$

LOGIC DIAGRAM:

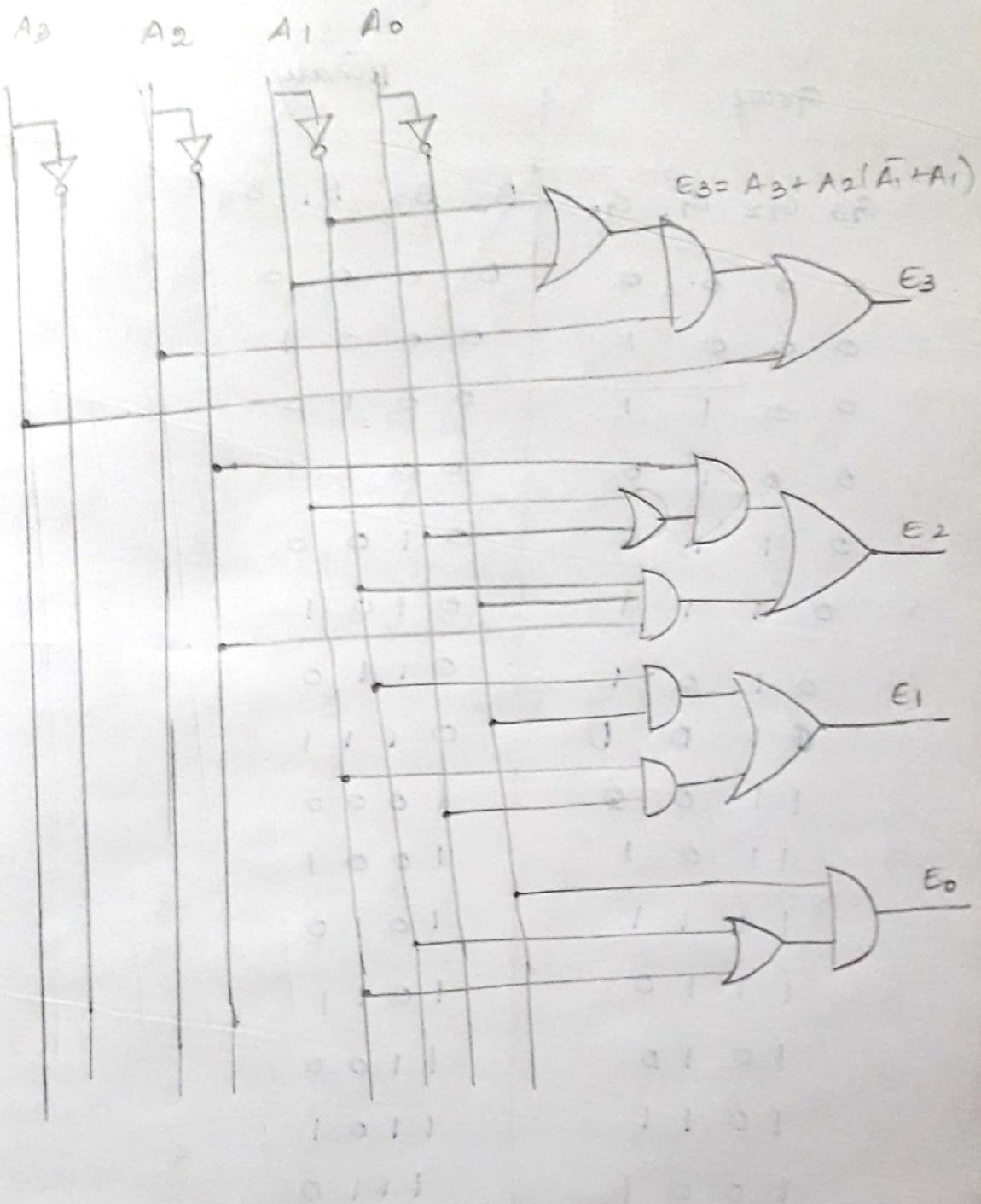

$$E_3 = A_3 + A_2(\bar{A}_1 + A_1) \quad \dots$$

$$E_2 = \bar{A}_2(A_1 + A_0) + \bar{A}_1\bar{A}_0A_2$$

$$E_1 = \bar{A}_1\bar{A}_0 + A_1A_0$$

$$E_0 = \bar{A}_0(\bar{A}_1 + A_1)$$

Using this logic diagram is shown above

31.

Gray to Binary

	Gray				Binary			
	G_3	G_2	G_1	G_0	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	1	0	0	1	0
3	0	0	1	0	0	0	1	1
4	0	1	1	0	0	1	0	0
5	0	1	1	1	0	1	0	1
6	0	1	0	1	0	1	1	0
7	0	1	0	0	0	1	1	1
8	1	1	0	0	1	0	0	0
9	1	1	0	1	1	0	0	1
10	1	1	1	1	1	0	1	0
11	1	1	1	0	1	0	1	1
12	1	0	1	0	1	1	0	0
13	1	0	1	1	1	1	0	1
14	1	0	0	1	1	1	1	0
15	1	0	0	0	1	1	1	1

 B_2

		$G_3 G_2 / G_1 G_0$			
		00	01	11	10
00	00	0	0	0	0
	01	1	1	1	1
01	11	0	0	0	0
	10	1	1	1	1

$$\boxed{B_3 = G_3}$$

$$B_2 = \bar{G}_3 G_2 + G_3 \bar{G}_2$$

$$\boxed{B_2 = G_3 \oplus G_2}$$

	$G_1 G_2$	$\bar{G}_1 G_2$	$G_1 \bar{G}_2$	$\bar{G}_1 \bar{G}_2$
$G_3 G_2$	0 0	1 1	0 1	1 0
$\bar{G}_3 G_2$	1 1	0 0	0 0	0 0
$G_3 \bar{G}_2$	0 0	1 1	1 1	0 0
$\bar{G}_3 \bar{G}_2$	1 1	0 0	0 0	0 0

$$\begin{aligned}
 B_1 &= G_3 \bar{G}_2 \bar{G}_1 + G_3 G_2 G_1 + \bar{G}_3 \bar{G}_2 G_1 + \bar{G}_3 G_2 \bar{G}_1 \\
 &= G_3 (\bar{G}_2 \bar{G}_1 + G_2 G_1) + \bar{G}_3 (\bar{G}_2 G_1 + G_2 \bar{G}_1) \\
 &= G_3 (G_2 \odot G_1) + \bar{G}_3 (G_1 \oplus G_2) \\
 &= \bar{G}_3 (G_1 \oplus G_2) + G_3 (G_1 \oplus G_2) \\
 &= \bar{G}_3 \oplus G_1 \oplus G_2 \\
 &= G_3 \oplus G_1 \oplus G_2 \oplus G_3 \\
 &= G_3 \oplus G_2 \oplus G_1
 \end{aligned}$$


	$G_1 G_2$	$\bar{G}_1 G_2$	$G_1 \bar{G}_2$	$\bar{G}_1 \bar{G}_2$
$G_3 G_2$	0 0	1 0	0 1	1 1
$\bar{G}_3 G_2$	0 1	1 0	1 1	0 0
$G_3 \bar{G}_2$	1 0	0 1	0 0	1 1
$\bar{G}_3 \bar{G}_2$	1 1	0 0	1 0	0 1

$$\begin{aligned}
 B_0 &= \bar{G}_3 \bar{G}_2 \bar{G}_1 G_0 + \bar{G}_3 \bar{G}_2 G_1 \bar{G}_0 + \\
 &\quad \bar{G}_3 G_2 \bar{G}_1 \bar{G}_0 + \bar{G}_3 G_2 G_1 G_0 + \\
 &\quad G_3 G_2 \bar{G}_1 G_0 + G_3 G_2 G_1 \bar{G}_0 + \\
 &\quad G_3 \bar{G}_2 \bar{G}_1 \bar{G}_0 + G_3 \bar{G}_2 G_1 G_0 \\
 &= \bar{G}_3 \bar{G}_2 (\bar{G}_1 G_0 + G_1 \bar{G}_0) + \bar{G}_3 \bar{G}_2 (\bar{G}_1 \bar{G}_0 + G_1 G_0) + \\
 &\quad G_3 G_2 (\bar{G}_1 G_0 + G_1 \bar{G}_0) + G_3 \bar{G}_2 (\bar{G}_1 \bar{G}_0 + G_1 G_0) \\
 &= \bar{G}_3 \bar{G}_2 (G_1 \oplus G_0) + \bar{G}_3 G_2 (G_1 \odot G_0) + G_3 G_2 (G_1 \oplus G_0) \\
 &\quad + G_3 \bar{G}_2 (G_1 \odot G_0) \\
 &= (\bar{G}_3 \bar{G}_2 + G_3 G_2)(G_1 \oplus G_0) + (\bar{G}_3 G_2 + \bar{G}_2 G_3)(G_1 \odot G_0) \\
 &= (G_3 \odot G_2)(G_1 \oplus G_0) + G_3 G_2 (G_1 \oplus G_0)
 \end{aligned}$$

$$\begin{aligned}
 &= (G_3 \odot G_2)(G_1 \oplus G_0) + (\overline{G_3 \oplus G_2}) \overline{(G_1 \oplus G_0)} \\
 &= (G_3 \odot G_2)(G_1 \oplus G_2) + (\overline{G_3 \odot G_2})(\overline{G_1 \oplus G_0}) \\
 &\quad \text{A} \qquad \text{B} \qquad \text{A} \qquad \text{B} \\
 &= \cancel{G_3 \odot G_2} \odot G_1 \oplus G_0 \\
 &= (G_3 \odot G_2)(G_1 \oplus G_0) + (G_3 \odot G_2)(\overline{G_0 \oplus G_1}) \\
 &\quad \text{A} \qquad \text{B} \qquad \text{A} \qquad \text{B} \\
 &= (G_3 \odot G_2) \odot G_1 \oplus G_0
 \end{aligned}$$

$$\begin{aligned}
 &= (\overline{G_3 \oplus G_2})(G_1 \oplus G_0) + (\overline{G_0 \oplus G_1})(G_2 \oplus G_3) \\
 &= G_3 \oplus G_2 \oplus G_1 \oplus G_0 \\
 B_0 &= G_0 \oplus B_2 \oplus G_1
 \end{aligned}$$

Design:-

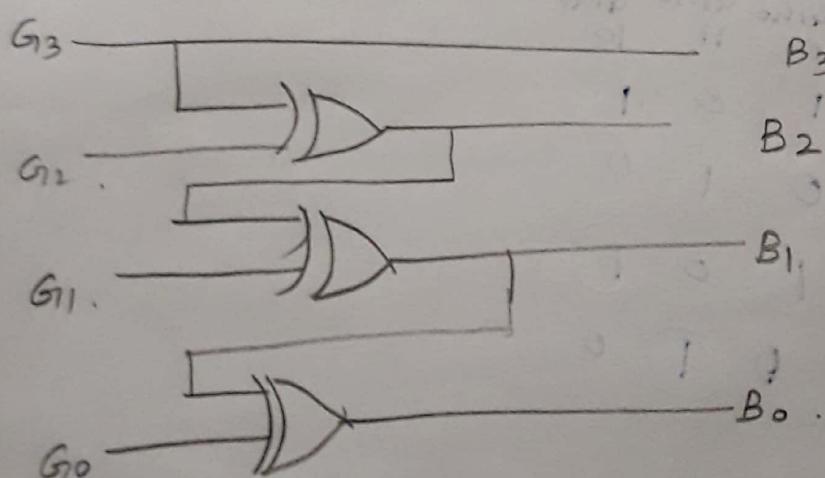

10.8.18

Binary parallel Adder.

Half adder - 2 bits of each input

Full adder - 3 bits 1 bit.

1. Ripple carry Adder (carry propagate Adder)


2. carry look ahead adder.

1. Ripple carry Adder :

(made of full adders)

If n bits are required, the n -number of full adders are required.

4-bit RCA.

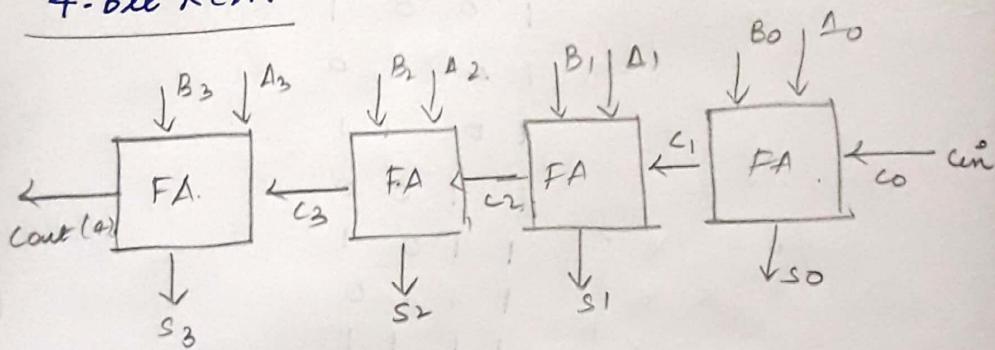

$$A = A_3 A_2 A_1 A_0 = 1101$$

$$B = B_3 B_2 B_1 B_0 = 1001$$

Initially top carry is zero.

$$A = A_3 \ A_2 \ \cancel{A_1} \ \cancel{A_0} \quad \cancel{c_0} = 0$$

3 inputs are added

$$B = B_3 \ B_2 \ \cancel{B_1} \ B_0$$

∴ full adders are used

$$\underline{\quad \quad \quad \quad}$$

$$S_3 \ S_2 \ S_1 \ S_0$$


$$\downarrow C_4$$

cout

Propagation delay: (Generally in nano second)

Time Delay between the input arrivals to the gate & the generation of carry.

propagation delay depends upon the gate.

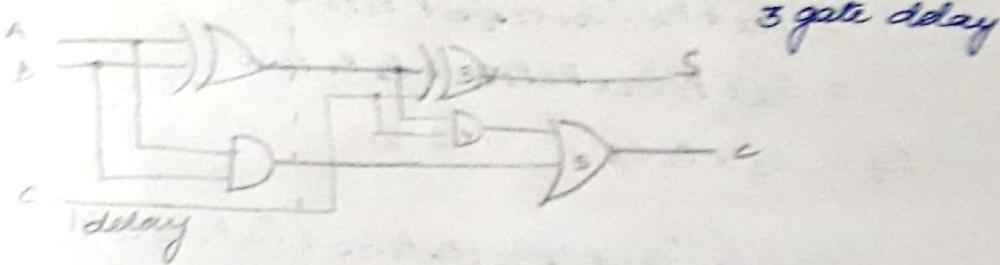


In full adder \rightarrow 3 gate delay. (in general)

disadvantage:

longest propagation delay.

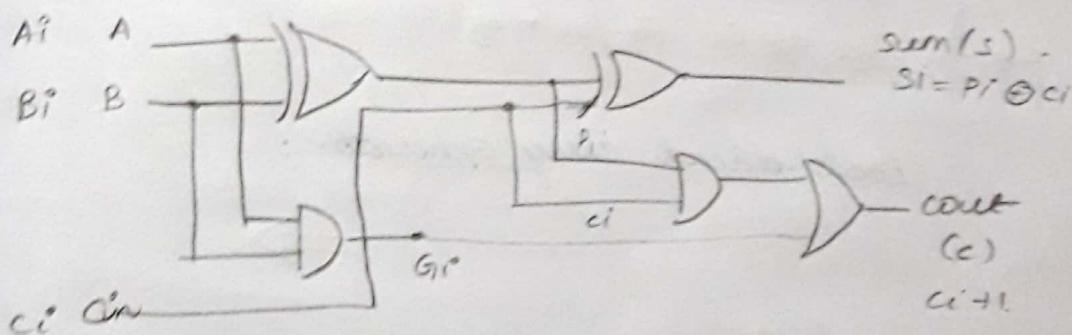2. carry look ahead adder: (high speed parallel adder)
All the carry are generated simultaneously.
we modify based on full adder
[consider it as single bit]



Assume $A \rightarrow A_i$, $B \rightarrow B_i$, $c_{in} \rightarrow c_i$

$P_i \rightarrow$ Propagate function $= A_i \oplus B_i$ (for i/p)

$G_i \rightarrow$ Generate function $= A_i B_i$. (And combination of inputs)

$$c_{i+1} = G_i + P_i c_i$$

apply $i=0$

$$\rightarrow C_1 = G_0 + P_0 C_0, \text{ where } C_0 \rightarrow \text{input carry.}$$

when $i=1$

$$\rightarrow C_2 = G_1 + P_1 C_1$$

sub C_1 in C_2

$$\begin{aligned} \rightarrow C_2 &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned}
 C_3 &= G_2 + P_2 C_2 \\
 &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\
 &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0.
 \end{aligned}$$

$$\begin{aligned}
 C_4 &= C_3 + P_3 C_3 \quad (\text{for } 4 \text{ bit CLA, } C_3 \text{ is the final carry}) \\
 &= C_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\
 &= C_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0
 \end{aligned}$$


$$\begin{aligned}
 C_n = G_{n-1} + P_{n-1} G_{n-2} + P_{n-1} P_{n-2} G_{n-3} + \dots + \\
 \dots + (P_{n-1} P_{n-2} \dots P_1 P_0 C_0)
 \end{aligned}$$

For 8 bit CLA:

$$\begin{aligned}
 \text{cout} = C_7 = G_7 + P_7 G_6 + P_7 P_6 G_5 + P_7 P_6 P_5 G_4 + \\
 P_7 P_6 P_5 P_4 G_3 + P_7 P_6 P_5 P_4 P_3 G_2 + \\
 P_7 P_6 P_5 P_4 P_3 P_2 G_1 + P_7 P_6 P_5 P_4 P_3 P_2 P_1 G_0 + \\
 P_7 P_6 P_5 P_4 P_3 P_2 P_1 \underline{P_0 C_0} \xrightarrow{\text{input carry}}
 \end{aligned}$$

→ Final O/p is in form of P & G

Look ahead carry Generator:


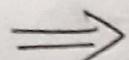


For 4 bit CLA;

we get 4 gate delay (fixed)
from i/p to output sum.
(Very high speed parallel adder)

to generate G_1 , $P \rightarrow 1$ gate
to generate sum = 1 gate.

Look ahead carry generator

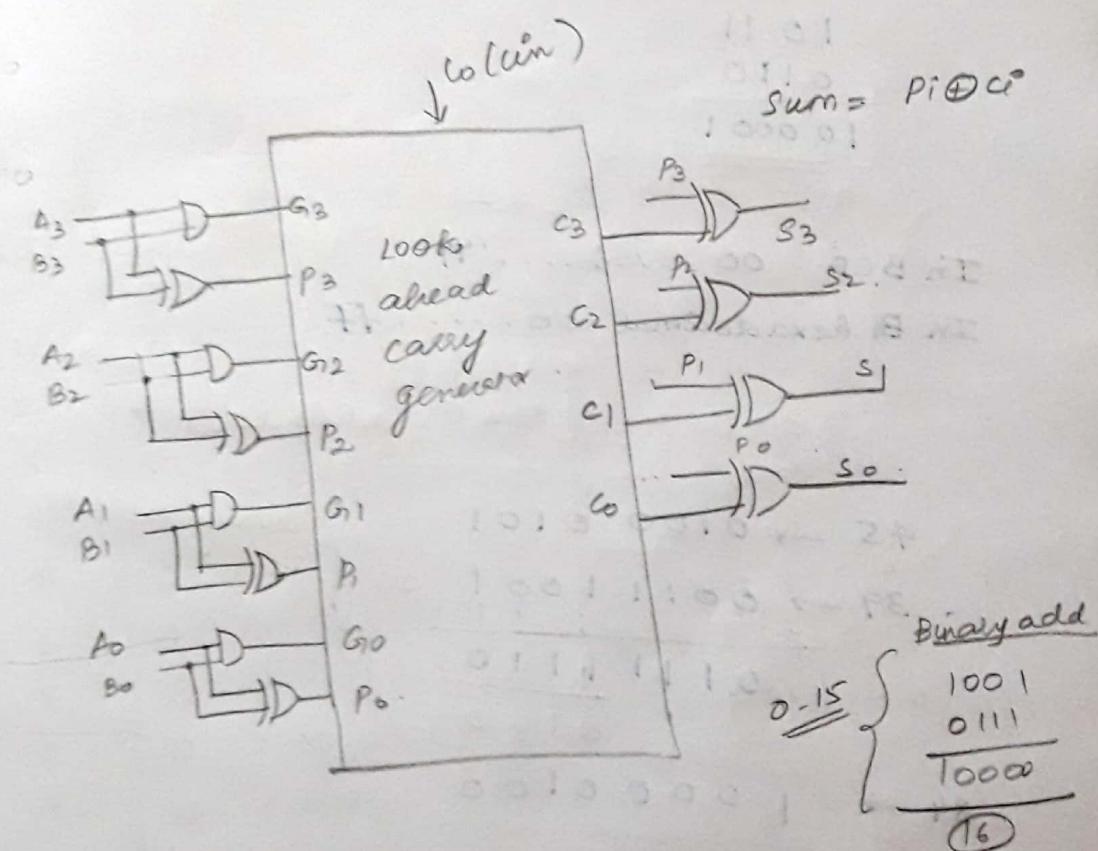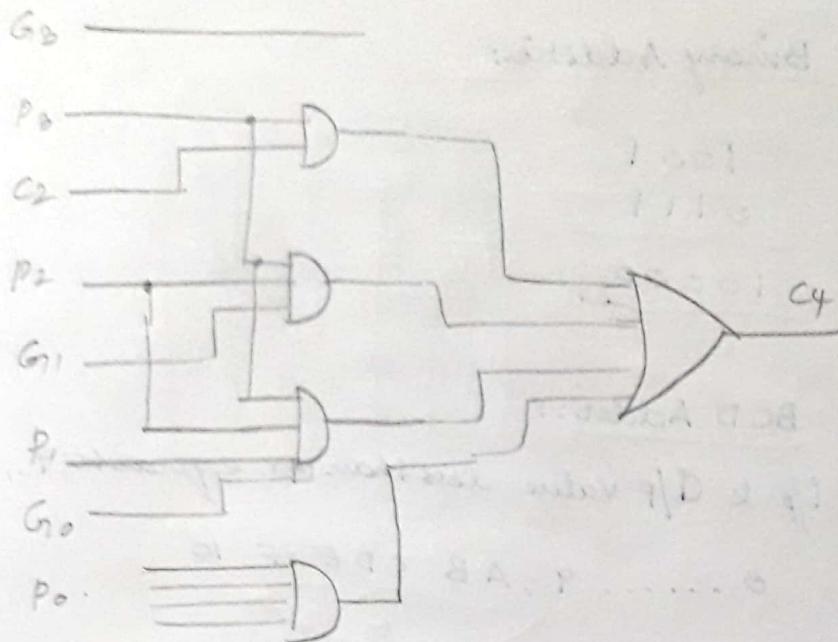

BCD addition

0 to 9
From 10 it repeats.


BCD Adder. (4 bit)

Binary Addition:

$$\begin{array}{r}
 1001 \\
 0111 \\
 \hline
 10000 \rightarrow [16]
 \end{array}$$

BCD Adder:

i/p & o/p value less than or equal to 9.

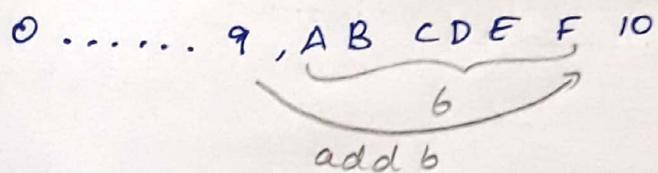

$$\begin{array}{r}
 1011 \\
 0110 \\
 \hline
 100001 \\
 \hline
 11
 \end{array}$$

In BCD 00 99 } highest value


In Bi hexadecimal 00 FF

If o/p is greater than 9, add 6 to it.

$$\begin{array}{r}
 45 \rightarrow 0100\ 0101 \\
 39 \rightarrow 0011\ 1001 \\
 \hline
 0111\ 1110 \\
 \hline
 0110
 \end{array}$$

} binary addition
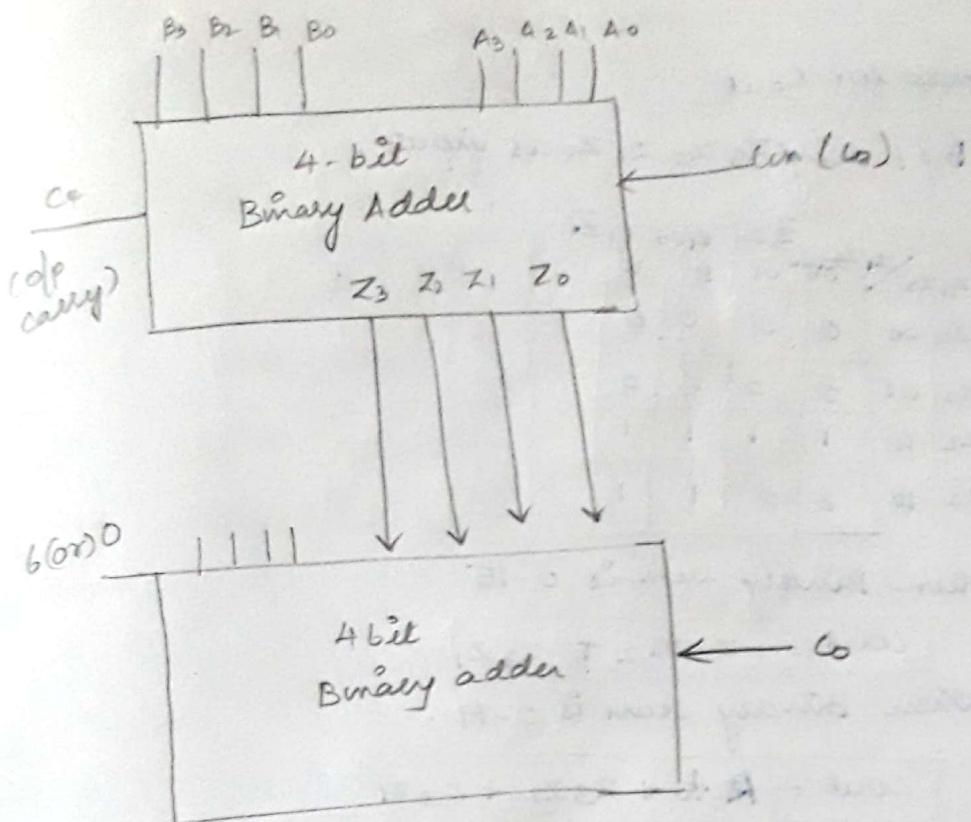
$$\begin{array}{r}
 84 \rightarrow 1000\ 0100
 \end{array}$$



DECIMAL	Binary sum					BCD sum.				
	K	Z ₃	Z ₂	Z ₁	Z ₀	out	S ₃	S ₂	S ₁	S ₀
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	1
5	0	0	1	0	1	0	0	1	1	0
6	0	0	1	1	0	0	0	1	1	1
7	0	0	1	1	1	0	1	0	0	0
8	0	1	0	0	0	0	1	0	0	1
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1				
13	0	1	1	0	1	1				
14	0	1	1	1	0	1				
15	0	1	1	1	1	1				
.										
.										

K map for Cout

By taking $Z_3 Z_2 Z_1 Z_0$ as inputs.


$Z_3 Z_2$	$\bar{Z}_1 Z_0$	$Z_1 \bar{Z}_0$	$Z_1 \bar{Z}_0$	$\bar{Z}_1 \bar{Z}_0$
$\bar{Z}_3 \bar{Z}_2 00$	0	0	0	0
$\bar{Z}_3 Z_2 01$	0	0	0	0
$Z_3 \bar{Z}_2 11$	1	1	1	1
$Z_3 Z_2 10$	0	0	1	1

When Binary sum is 0-15

$$\boxed{\text{Cout} = Z_3 Z_2 + Z_3 Z_1}$$

When Binary sum is 0-19.
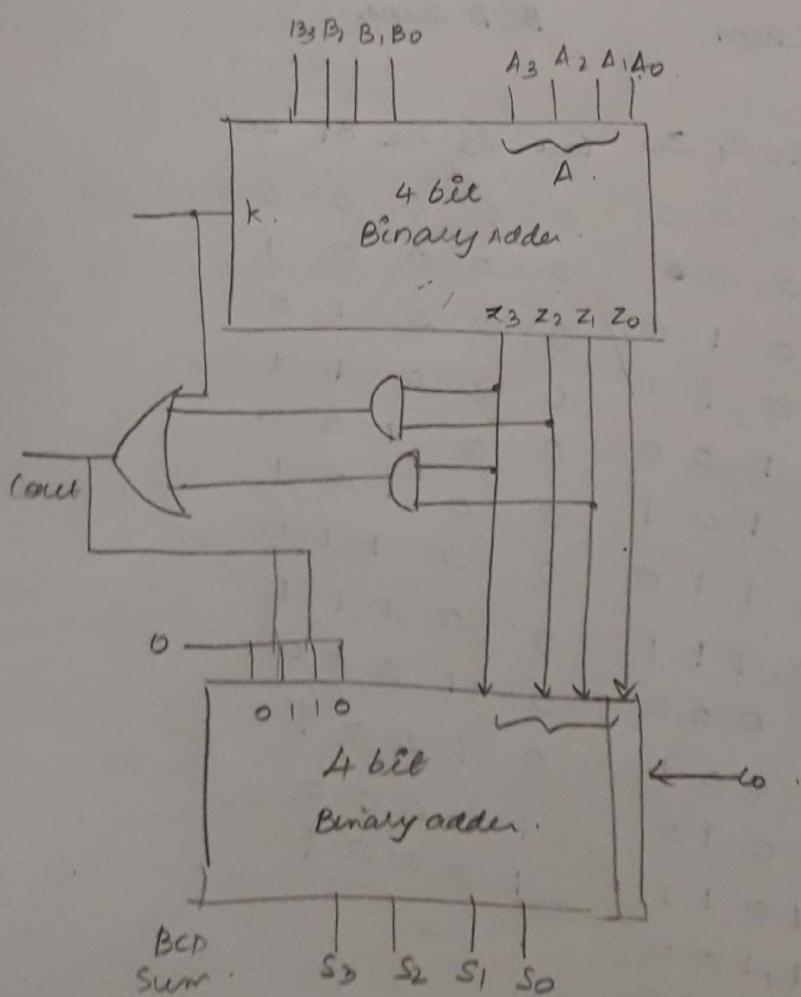
$$\boxed{\text{Cout} = \cancel{Z_3 \cdot k} + Z_3 Z_2 + Z_3 Z_1}$$



Magnitude comparison

Inputs

A		B		Outputs		
A_1, A_0	B_1, B_0			$A > B$	$A = B$	$A < B$
0 0	0 0			0	1	0
0 0	0 1			0	0	1
0 0	1 0			0	0	1
0 0	1 1			0	0	1
0 1	0 0			1	0	0
0 1	0 1			0	1	0
0 1	1 0			0	0	1
0 1	1 1			0	0	1
1 0	0 0			1	0	0
1 0	0 1			1	0	0
1 0	1 0			0	1	0
1 0	1 1			0	0	1
1 1	0 0			1	0	0
1 1	0 1			1	0	0
1 1	1 0			1	0	0
1 1	1 1			0	1	0

K map

		$A > B$			
		$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
		00	01	11	10
$\bar{A}_1 \bar{A}_0$	00	0	0	0	0
$\bar{A}_1 \bar{A}_0$	01	1	0	0	0
$\bar{A}_1 \bar{A}_0$	11	0	1	0	0
$\bar{A}_1 \bar{A}_0$	10	1	1	0	0

$A > B$

$= A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0 + A_1 \bar{B}_1$

$$(ii) \quad A = B \\ A = B$$

		B ₁ B ₀	00	01	11	10
		A ₁ A ₀	00	01	11	10
A ₁ A ₀	B ₁ B ₀	00	1	0	0	0
		01	0	1	0	0
A ₁ A ₀	B ₁ B ₀	11	0	0	1	0
		10	0	1	0	1

$$(iii) \quad A < B$$

		B ₁ B ₀	00	01	11	10
		A ₁ A ₀	00	01	11	10
A ₁ A ₀	B ₁ B ₀	00	0	1	1	1
		01	0	0	1	1
A ₁ A ₀	B ₁ B ₀	11	0	0	0	0
		10	0	0	1	0

$$\boxed{A=B} = \overline{A_1}\overline{A_0}\overline{B_1}\overline{B_0} + \overline{A_1}A_0\overline{B_1}B_0 \\ + A_1A_0B_1B_0 + A_1\overline{A_0}\overline{B_1}\overline{B_0}$$

$$\boxed{A < B} = \overline{A_1}B_1 + \overline{A_1}\overline{A_0}B_0 + \overline{A_0}B_1B_0$$

case(i) : $\boxed{A > B}$

$$\begin{aligned} A > B &= A_1\overline{B_1} + A_0\overline{B_1}\overline{B_0} + A_1A_0\overline{B_0} \\ &= A_1\overline{B_1} + (A_1 + \overline{A_1})A_0\overline{B_1}\overline{B_0} + A_1A_0(\overline{B_1} + \overline{B_1})\overline{B_0} \\ &= A_1\overline{B_1} + A_1A_0\overline{B_1}\overline{B_0} + \overline{A_1}A_0\overline{B_1}\overline{B_0} + \\ &\quad A_1A_0B_1\overline{B_0} + \cancel{A_1A_0\overline{B_1}\overline{B_0}} \\ &= A_1\overline{B_1} + A_1A_0\overline{B_1}\overline{B_0} + A_0\overline{B_0}(\overline{A_1}\overline{B_1} + A_1B_1) \\ &= \underbrace{A_1\overline{B_1}}_{\text{use adiompse law}} + A_1A_0\overline{B_1}\overline{B_0} + (A_1 \odot B_1)A_0\overline{B_0} \\ &= A_1\overline{B_1}(1 + A_0\overline{B_0}) + (A_1 \odot B_1)A_0\overline{B_0} \\ A > B &= A_1\overline{B_1} + (A_1 \odot B_1)A_0\overline{B_0} \end{aligned}$$

From (i), (ii) and (iii) cases:-

$$(A = B) = X_1X_0$$

$$(A > B) = A_1\overline{B_1} + X_1A_0\overline{B_0}$$

$$(A < B) = \overline{A_1}B_1 + X_1\overline{A_0}B_0$$

case (ii) : $A \subsetneq B$

$$\begin{aligned}
 A \subsetneq B &= \overline{A_1} B_1 + \overline{A_1} \overline{A_0} B_0 (B_1 + \overline{B_1}) + \overline{A_0} B_1 B_0 (A_1 + \overline{A_1}) \\
 &= \overline{A_1} B_1 + \overline{\overline{A_1} \overline{A_0} B_0} \overline{B_1} + \overline{\overline{A_1} \overline{A_0}} \overline{B_1} \overline{B_0} + \overline{A_1} \overline{\overline{A_0} B_1} B_0 \\
 &= \overline{A_1} B_1 (1 + \overline{A_0} B_0) + \overline{A_0} B_0 (\overline{A_1} \overline{B_1} + A_1 B_1) \\
 &= \overline{A_1} B_1 + \overline{A_0} B_0 \underbrace{(A_1 \odot B_1)}_{\text{from } \textcircled{1}} = \overline{A_1} B_1 + \overline{A_0} B_0 x_1
 \end{aligned}$$

case (ii) $A = B$:-

$$= \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 A_0 B_1 B_0 + \overline{A_1} \overline{A_0} B_1 \overline{B_0}$$

$$\begin{aligned}
 &= \overline{A_1} \overline{B_1} (\overline{A_0} \overline{B_0} + A_0 B_0) + A_1 B_1 (A_0 B_0 + \overline{A_0} \overline{B_0}) \\
 &= \overline{A_1} \overline{B_1} (A_0 \odot B_0) + A_1 B_1 (A_0 \odot B_0) \\
 &= (A_0 \odot B_0) (\overline{A_1} \overline{B_1} + A_1 B_1) \\
 &= (A_0 \odot B_0) (A_1 \odot B_1) \\
 &= x_0 x_1 + x_1 x_0
 \end{aligned}$$

Let $x_1 = A_1 \odot B_1$ } $\rightarrow \textcircled{1}$
 $x_0 = A_0 \odot B_0$

similarly $x_i = A_i \odot B_i$

While comparing:
LHS \rightarrow RHS
left to Right.

e.g.: $x > y$

$$x = 5 \underline{3} 4 \underline{3} 2 1 7 8$$

$$y = 5 3 4 \underline{2} 1 7 8 7$$

4-bit

$$A = A_3 \ A_2 \ A_1 \ A_0$$

$$B = B_3 \ B_2 \ B_1 \ B_0$$

1101
1101

$$(A > B) = A_3 \bar{B}_3 + X_3 A_2 \bar{B}_2 + X_3 X_2 A_1 \bar{B}_1 + X_3 X_2 X_1 A_0 \bar{B}_0$$

$$(A < B) = \bar{A}_3 B_3 + X_3 \bar{A}_2 B_2 + X_3 X_2 \bar{A}_1 B_1 + X_3 X_2 X_1 \bar{A}_0$$

$$(A = B) = X_3 X_2 X_1 X_0$$