

03-07-18

Chapter - 1

Number System .

1. Binary Number system
2. Decimal " "
3. Octal " "
4. Hexadecimal " "
(Hex)

2. Decimal $\Rightarrow 0, 1, 2, \dots, 9$

$$\begin{aligned}356 &= 3 \times 100 + 5 \times 10 + 6 \times 1 \\&= 3 \times 10^2 + 5 \times 10^1 + 6 \times 10^0\end{aligned}$$

Weights

Base or radix of decimal no. system = 10

1. Binary $\Rightarrow 0$ and 1

Base of no. is 2.

3. Octal $\Rightarrow 0, 1, 2, 3, 4, 5, 6, 7$

Base of system is 8

4. Hexadecimal $\Rightarrow 0, 1, 2, \dots, 10, 11, 12, 13, 14, 15$.

A B C D E F

Base of system is 16.

Conversion

1. of decimal base 10

Binary
(repeated division by 2)

$$\begin{array}{r} 2 | 356 \\ 2 | 178 - 0 \\ 2 | 89 - 0 \\ 2 | 44 - 1 \\ 2 | 22 - 0 \\ 2 | 11 - 0 \\ 2 | 5 - 1 \\ 2 | 2 - 1 \\ \hline 1 - 0 \end{array}$$

Octal
(repeated div by 8)

$$\begin{array}{r} 8 | 356 \\ 8 | 44 - 4 \\ 8 | 5 - 4 \\ \hline (544)_8 \end{array}$$

Hex.
(repeated \div 16)

$$\begin{array}{r} 16 | 356 \\ 16 | 22 - 4 \\ 16 | 1 - 6 \\ \hline (164)_{16} \end{array}$$

To octal

0.87

0.96

0.68

.87

0.87

0.92

0.72

0.52

To hex

CONVERSI

(11011

Resultant

Binary value $\Rightarrow (101100100)_2$

Octal value $\Rightarrow (544)_8$

Hex value $\Rightarrow (164)_{16}$

2. 356.87

.87

To binary :-

$$0.87 \times 2 = 1.74$$

$$0.74 \times 2 = 1.48$$

$$0.48 \times 2 = 0.96$$

$$0.96 \times 2 = 1.92$$

$$0.92 \times 2 = 1.84$$

$$0.84 \times 2 = 1.68$$

1. Take only decimal value repeatedly

2. Take the integer value from top to bottom

$356.87 \Rightarrow$ binary $\Rightarrow (101100100.110111)_{\underline{\underline{2}}}$

To octal

.87

$$\begin{array}{r}
 0.87 \times 8 = 6.96 \\
 0.96 \times 8 = 7.68 \\
 0.68 \times 8 = 5.44
 \end{array}
 \text{upto } 5 \text{ values.}$$

$$\Rightarrow (544.675)_8$$

To hex

.87

$$\begin{array}{r}
 0.87 \times 16 = 13.92 \Rightarrow D.92 \\
 0.92 \times 16 = 14.72 \Rightarrow E.72 \\
 0.72 \times 16 = 11.52 \Rightarrow B.52 \\
 0.52 \times 16 = 8.32 \Rightarrow 8.32
 \end{array}$$

$$\Rightarrow (164.DEB8)_{16}$$

CONVERSION OF BINARY TO DECIMAL.

$$(110110)_2 \Rightarrow (54)_{10} \text{ [decimal]}$$

$$\begin{array}{r}
 0 \times 2^0 = 0 \\
 + \\
 1 \times 2^1 = 2 \\
 + \\
 1 \times 2^2 = 4 \\
 + \\
 0 \times 2^3 = 0 \\
 + \\
 1 \times 2^4 = 16 \\
 + \\
 1 \times 2^5 = 32 \\
 \hline
 54
 \end{array}$$

CONVERSION OF BINARY TO OCTAL.

$$1.9) \underline{(110110)_2} = (66)_8$$

↓ MSB ↓ LSB

OCTAL IN BINARY :-

| |
|----------------|
| 0 - 000 |
| 1 - 001 |
| 2 - 010 |
| 3 - 011 |
| 4 - 100 |
| 5 - 101 |
| 6 - <u>110</u> |
| 7 - 111 |

① Start from least significant bit
[last value]


(or) LS B
↓
bit

MSB \Rightarrow Most significant bit

② Group it in terms of 3 from right (LSB)

I. convert

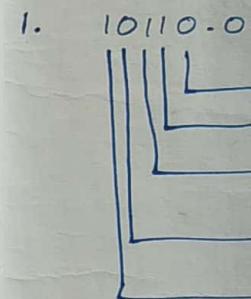1. 10110...
2. (16.5),
3. (26.24)
4. (DADA)



$$2.9) \underline{(001101111101)_2} = (1575)_8$$

CONVERSION OF BINARY TO HEXA DECIMAL.

0 - 0000 \rightarrow weight of binary

| |
|----------|
| 0 - 0000 |
| 1 - 0001 |
| 2 - 0010 |
| 3 - 0011 |
| 4 - 0100 |
| 5 - 0101 |
| 6 - 0110 |
| 7 - 0111 |
| 8 - 1000 |
| 9 - 1001 |
| A - 1010 |
| B - 1011 |
| C - 1100 |
| D - 1101 |
| E - 1110 |
| F - 1111 |

Group into 4

0.0
↓
0x2

2. (16.5)₁₆
-

0.5x

\Rightarrow

$$18) \underline{0110110}_2 = (36)_{16}$$

$$20) \underline{0110111101}_2 = (37D)_{16}$$

least
bit
value]

LSB
Bit

significant

terms
sign
(SB)

I convert the following numbers to DECIMAL

$$1. 10110.0101$$

$$2. (16.5)_{16}$$

$$3. (26.24)_8$$

$$4. (DADA.B)_{16}$$

$$1. 10110.0101$$

$$\begin{array}{r} | \\ 10110.0101 \\ | \quad | \\ 0 \times 2^0 \longrightarrow 0 \\ 1 \times 2^1 \longrightarrow 2 \\ 1 \times 2^2 \longrightarrow 4 \\ 0 \times 2^3 \longrightarrow 0 \\ 1 \times 2^4 \longrightarrow 16 \\ \hline 22 \end{array}$$

$$\begin{array}{r} 0101 \\ | \quad | \quad | \\ 0 \quad 1 \quad 0 \quad 1 \\ | \quad | \quad | \quad | \\ 2^0 \quad 2^1 \quad 2^2 \quad 2^3 \\ \frac{1}{2} + \frac{1}{4} \\ 22.3125 \end{array}$$

$$\begin{array}{r} 0.0101 \\ | \\ 0 \times 2^{-1} \quad | \quad | \\ 0 \times 2^{-3} \quad | \\ 1 \times 2^{-4} = \frac{1}{16} \\ 0 \times 2^{-2} \quad | \\ 1 \times 2^{-1} = \frac{1}{4} \end{array}$$

$$22 + \frac{1}{16} + \frac{1}{4} = (22.3125)_{10}$$

$$2. (16.5)_{16} \text{ to decimal}$$

$$\begin{array}{r} | \\ 6 \times 16^0 = 6 \\ | \\ 1 \times 16^1 = 16 \end{array}$$

$$0.5 \times 16^{-1} = 5/16$$

$$\Rightarrow 6 + 16 + 5/16 = (22.3125)_{10}$$

$$3. (26.24)_8$$

$$\begin{array}{r} \boxed{ } \\ \rightarrow 6 \times 8^0 \rightarrow 6 \\ \rightarrow 2 \times 8^1 \rightarrow 16 \end{array}$$

$$0.24$$

$$\begin{array}{r} \boxed{ } \\ \rightarrow 2 \times 8^{-1} = 2/8 \\ \rightarrow 4 \times 8^{-2} = 4/64 \end{array}$$

$$\Rightarrow 6 + 16 + 2/8 + 4/64 = \\ = 22 + 20/64 = 22 + 5/16 = (22.3125)_{10}$$

$$4. (DADA.B)_{16}$$


$$\begin{array}{c} D A D A . B \\ | | | | \downarrow \quad \downarrow \\ 13 \times 16^1 \quad 10 \times 16^0 \quad 11 \times 16^{-1} \\ | \quad | \quad | \\ 10 \times 16^2 \\ | \\ 13 \times 16^3 \end{array}$$

$$\Rightarrow 53248 + 2560 + 208 + 10 + 0.6875 \\ = (56026.6875)_{10}$$

6.7.18

1. 011011110110

to decimal.

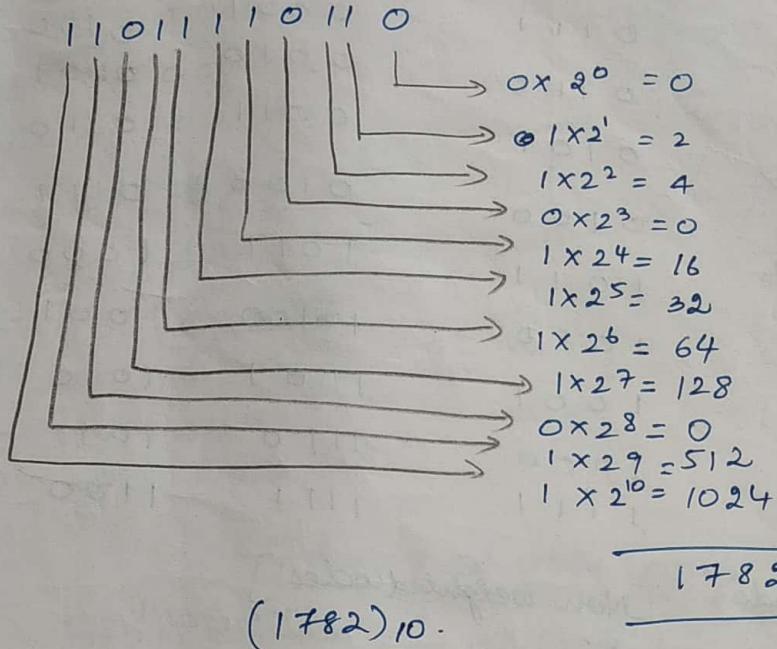

TO hexa decimal $\rightarrow (6F6)_{16}$, TO octal $(3366)_8$



3. 011011110110
 $(6F6)_{16}$



$(3366)_8$
011011110110

BINARY CODES

ASCII \rightarrow American Standard Code for Information Interchange

$\boxed{8421} \rightarrow$ Binary code $\Rightarrow 0 \text{ to } 15 \rightarrow$ Hexadecimal

84-2-1

$\checkmark 8421$

$\checkmark BCD$

$\checkmark Gray$

$\checkmark Biunary$

Exclns-3

Binary coded Decimal

8421

• BCD

8421

0 0000

1 0001

2 0010

3 0011

4 0100

5 0101

6 0110

7 0111

8 1000

9 1001

WEIGHTED CODES

84-2-1

0000

0111

0110

0101

0100

1011

1010

1001

1000

1111

Binary coded decimal

BCD

2421

84-2-1 \rightarrow 8

0000

0001

0010

0011

0100

0101

0110

0111

1000

1001

1010

1011

1100

1101

1110

1111

1000

1001

1010

1011

1100

1101

1110

1111

1000

1001

1010

1011

1100

1101

1110

1111

1000

1001

1010

1011

1100

1101

1110

1111

Bi quinary

Bi

50

0 01

1 01

2 01

3 01

4 01

5 10

6 10

7 10

8 10

9 10

• Gray code [Non weighted codes]

Reflected code (or) Unit distance code (or) cyclic

010

0 0000

1 0001

2 0011

3 0010

4 0110

5 0111

6 0101

7 0100

8 1100

9 1101

10 1111

11 1110

12 1010

13 1011

14 1001

15 1000

(0 to 15)

Excess-3

0011

0100

1011

1100

1101

1110

1111

sign

magn

f

+13 sign

-13 no.

0

13 000

+13 000

-13 100

MSB

38
 Non Weighted
 Excess 3
~~+3 to BCD~~

Biquinary (Weighted)

Bi quinary

| | | |
|------|----|---------|
| 0001 | 50 | 43210 |
| 0100 | 0 | 010001 |
| 0101 | 1 | 0100010 |
| 0110 | 2 | 0100100 |
| 0111 | 3 | 01000 |
| 1000 | 4 | 010000 |
| 1001 | 5 | 100001 |
| 1010 | 6 | 100010 |
| 1011 | 7 | 100100 |
| 1100 | 8 | 1001000 |
| 1101 | 9 | 1000000 |

Finding of ones parity.

01011000 → no of 1's is 3
 odd parity

11011000 → no of 1's is 4
 even parity.

Signed Numbers / Integers.

Sign magnitude form
 +13 (0)
 -13 (1)
 signed nos

One's complement
 (Diminished Radix Comp)
 + → same
 - → take complement
 1 → 0, 0 → 1

Decimal
 9's 10's
 (Diminished Radix)
 (Radix)
 → take complement
 1 → 0, 0 → 1
 add 1.

$$\begin{array}{r} 11110010 \\ + 1 \\ \hline 11110011 \end{array}$$

| | | |
|-----|----------|----------|
| 13 | 00001101 | 00001101 |
| +13 | 00001101 | 00001101 |
| -13 | 10001101 | 11110010 |

MSB add(1)

[Can be of 8 (or) 5 bit]

[In computers
 Subtraction is done
 in 2's complement]

BINARY ADDITION

| A | B | CY | Truth Table |
|---|---|----|-------------|
| 0 | 0 | 00 | |
| 0 | 1 | 00 | |
| 1 | 0 | 00 | |
| 1 | 1 | 10 | |

1011 = 11

$$\begin{array}{r} \text{19) } \quad \begin{array}{r} 11 \\ 10 \\ 11 \\ 11 \\ \hline 11010 \end{array} \\ \text{summation is more than} \\ \text{the required bit} \\ \text{it is called as} \\ \text{CARRY} \end{array}$$

$$\begin{array}{r} \text{29) } \quad \begin{array}{r} 1101 \\ 1101 \\ 1101 \\ \hline 100111 \end{array} \\ \text{25} \\ \text{12-1} \\ \text{6-0} \\ \text{3-0} \\ \text{1-1} \end{array}$$

$$\begin{array}{lll} \text{1-8) } & \begin{array}{l} \text{sign Mag.} \\ \text{1's comp} \\ \text{2's comp} \end{array} & \\ \begin{array}{l} 25 \\ +25 \\ -25 \end{array} & \begin{array}{l} 00011001 \\ 00011001 \\ 10011001 \end{array} & \begin{array}{l} 00011001 \\ 00011001 \\ 11100110 \end{array} \\ & & \begin{array}{l} 00011001 \\ 11100110 \\ +1 \\ \hline 11100111 \end{array} \end{array}$$

BINARY SUBTRACTION

$$\begin{array}{r} 1011 \\ (-) \quad 1101 \\ \hline 1101 \end{array}$$

0
1
10
11
100

By 2's comp method.

$$\begin{array}{r} 13 \rightarrow 1101 \rightarrow 1101 \\ 11 - 1011 \qquad \qquad 0101 \\ \hline \end{array}$$

$$\underbrace{10010}_{\text{1's comp}}$$

$$\begin{array}{r} 11 \quad 1011 \quad 1011 \\ - 13 \quad 1101 \quad 0011 \\ \hline 11010 \rightarrow 2^{\text{'}} \end{array}$$

- Steps
1. first no. take as it is
 2. 2nd no. take 2's comp
 3. add both 1's comp

$$\begin{array}{r} 0100 \\ + \quad 1 \\ \hline 0101 \end{array}$$

2's comp

$$\begin{array}{r} 0010 \\ 0001 \\ + \quad 1 \\ \hline 0010 \end{array}$$

LOGIC GATES

AND

$$Y = A \cdot B$$

OR

$$Y = A + B \quad [\text{diff from binary addition}]$$

NOT

$$Y = \bar{A}$$

{ NAND

$$Y = \overline{A \cdot B} \quad \text{NOT + AND}$$

} basic gates

NOR

$$Y = \overline{A + B} \quad \text{NOT + OR}$$

} universal gates

XOR

$$Y = A \oplus B \Rightarrow \overline{AB} + B\overline{A}$$

Both are complements of each other.

X NOR


$$Y = A \odot B \Rightarrow AB + \overline{A}\overline{B}$$

$$\begin{aligned} \overline{A \oplus B} &= A \odot B \\ \overline{A \odot B} &= A \oplus B \end{aligned}$$

Symbols


7.18

AND

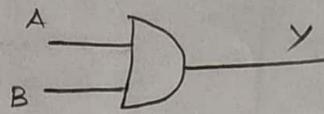


$$\text{AND} = Y$$

OR

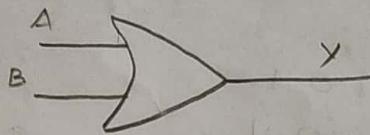


NOT

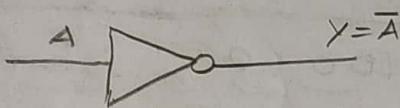


OR

| A |
|---|
| 0 |
| 0 |
| 1 |
| 1 |


NAND

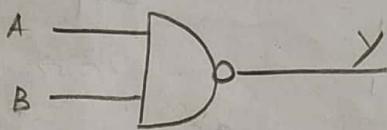


NOR

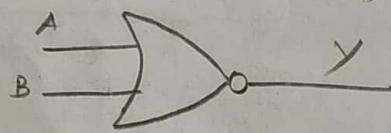

XOR

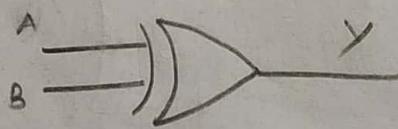

XNOR

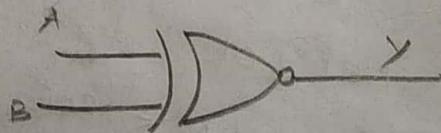

Inver

| A |
|---|
| 0 |
| 1 |

N

| A |
|---|
| 0 |
| 0 |
| 1 |
| 1 |

10.7.18

Logic gates

$$\text{AND} = Y = A \cdot B$$

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

XOR

| A | B | Y = A \oplus B |
|---|---|------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

OR

| A | B | Y = A + B |
|---|---|-----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

XNOR

| A | B | Y = A \odot B |
|---|---|-----------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Inverter (NOT)

| A | B | Y = \bar{A} |
|---|---|---------------|
| 0 | | 1 |
| 1 | | 0 |

NAND

| A | B | Y = $\overline{A \cdot B}$ |
|---|---|----------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

NOR

| A | B | Y = $\overline{A + B}$ |
|---|---|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

AND laws:-

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

OR laws:-

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + \bar{A} = 1$$

Double Inversion law:-

$$(A')' = \bar{\bar{A}} = A$$

Commutative laws:-

$$AB = BA$$

$$A+B = B+A$$

Associative laws:-

$$A(BC) = (AB)C$$

$$A+(B+C) = (A+B)+C$$

Distributive laws:-

$$A(B+C) = AB+AC$$

$$A+BC = (A+B)(A+C)$$

Absorption

$$A(A+B) = A$$

$$A+A = A$$

De Morgan

$$(A+B)' = \bar{A}\bar{B}$$

$$(AB)' = \bar{A}+\bar{B}$$

Boolean

$$Y = f(X)$$

Reduction

I. Use

$$1. \quad ?$$

$$2. \quad \alpha$$

$$3. \quad \beta$$

Answer

$$1. \quad x$$

$$2. \quad ?$$

$$= ?$$

$$= ?$$

Absorption law:

$$A(A+B) = A$$

$$A+AB = A$$

$$\begin{aligned} & \rightarrow A \cdot A + A \cdot B \\ &= A + A \cdot B \\ &= A(1+B) \\ &= A \end{aligned}$$

De Morgan's law:

$$(A+B)' = A'B'$$

$$(AB)' = A'B'$$

Boolean expression.

$$Y = A'B + B'CD$$

individuals are called as literals

Reduction of Boolean Expression.

1. Boolean laws (simple)
2. Karnaugh map. (complicated)
3. Tabulation method. (v. complicated)

I. Use Boolean laws & reduce the expression.

1. $xy + xy'$
2. $xyz + x'y + xy'z'$
3. $(a+b+c')(a'b'+c)$

Answers.

$$\begin{aligned} 1. \quad & xy + xy' \\ & x(y+y') = x \cdot 1 \\ & = x \end{aligned}$$

$$\begin{aligned} 2. \quad & xyz + x'y + xy'z' \\ & = xy(z+z') + x'y \\ & = xy + x'y \\ & = y(x+x') \\ & = y \cdot 1 = y \end{aligned}$$

$$3. (a+b+c')(a'b'+c)$$

$$\begin{aligned} &= aa'b' + a'b'b + a'b'c + ac + bc + \cancel{c'c} \\ &= 0 + 0 + a'b'c' + ac + bc \\ &= a'b'c' + ac + bc \quad // \end{aligned}$$

$$4. (BC' + A'D)(AB' + C'D')$$

$$\begin{aligned} &= \cancel{\frac{AB'BC'}{0}} + \cancel{\frac{BC'D'D'}{0}} + \cancel{\frac{AA'DB'}{0}} + \cancel{\frac{A'DC'D'}{0}} \\ &= 0 \end{aligned}$$

$$5. A'B(D' + c'D) + B(A + A'cD)$$

$$= A'BD' + \underline{A'BC'D} + BA + B\underline{A'C}D$$

$$= \cancel{A'D(BC')}$$

$$= A'BD(C' + c') + A'BD' + BA$$

$$= A'BD + A'BD' + BA$$

$$= A'B(D + D') + BA$$

$$= A'B + BA$$

$$= B(A + A')$$

$$= B$$

$$6. (A' + c)(A' + c')(A + B + c'D) = A'(B + c'D)$$

$$= (A'A' + A'c' + cA' + \cancel{cc'}) (A + B + c'D)$$

$$= A'(A' + c' + c)(A + B + c'D)$$

$$= A'(\cancel{A'A} + A'B + A'c'D + c'A + c'B + c'c'D + AC + CB + \cancel{Cc'D})$$

$$= A'(\cancel{A'B} + \cancel{A'c'D} + \cancel{c'A} + \cancel{c'B} + \cancel{c'c'D} + \cancel{Ac} + \cancel{CB})$$

$$= A' [B(c + c') + A(c + c') + c'c'D + A'c'D + A'B]$$

$$= A' [B + A + c'c'D + A'c'D + A'B]$$

$$\begin{aligned} & (A' + c'c) \\ &= A'(A + c) \\ &= A'(B + c) \end{aligned}$$

Implementation

$$y = \underline{xy}$$

x —

y —

x —

y →

NAND

$$y = \overline{\overline{y}} =$$

x —

y —


x —

y —

$$\begin{aligned}
 & (A' + cC') (A + B + C'D) \\
 &= A' (A + B + C'D) = A'A + A'B + A'C'D \\
 &= A'(B + C'D)
 \end{aligned}$$


Implementation using Logic gates.

$$Y = \underline{xy} + \underline{x}y'$$

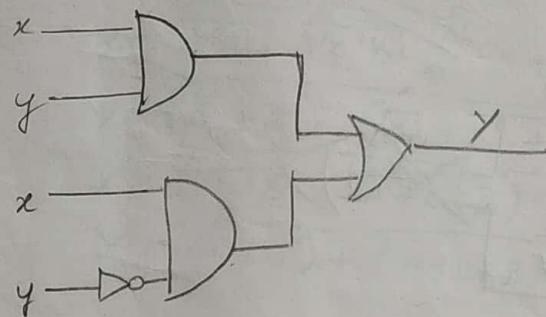

NAND
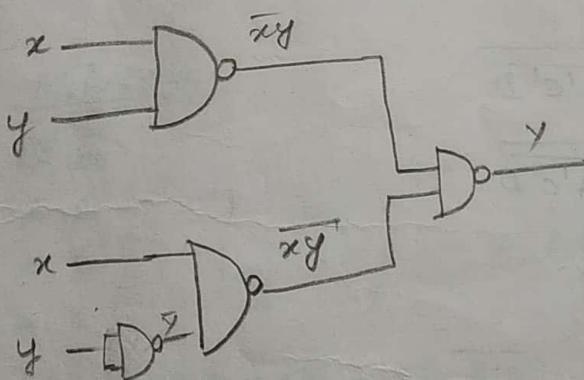
$$\begin{aligned}
 Y &= \overline{\overline{xy}} = \overline{\overline{xy} + \overline{x}y'} \\
 &= \overline{\overline{xy}} = \overline{\overline{xy} \cdot \overline{xy'}} \quad \text{NAND} \Leftrightarrow \text{NOR}
 \end{aligned}$$




NOR.

$$\begin{aligned} y &= \overline{\overline{xy} \cdot \overline{x'y'}} \\ &= \overline{(x'+y') (x'y)} \\ &= \overline{(x'+y')} + \overline{(x'y)} \end{aligned}$$

($x' + y'$) ($x + y$)
[Avoid multiplication]

only NOR

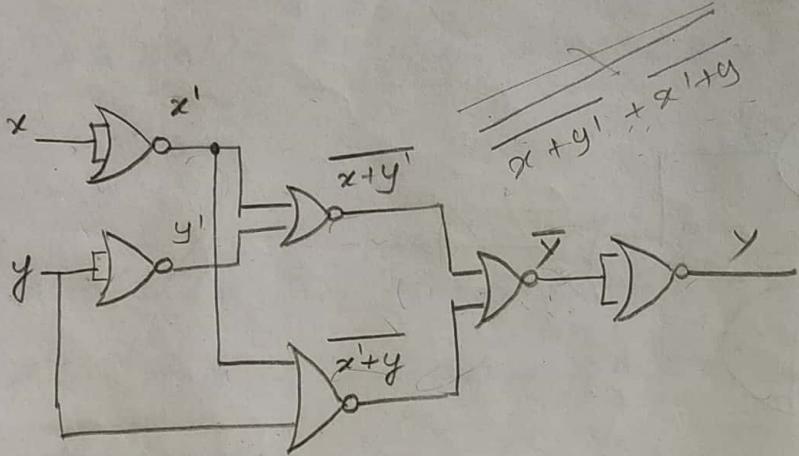


$$A'(B+C'D)$$

only NAND and only NOR.

\Rightarrow only NAND

$$y = A'B + A'C'D$$
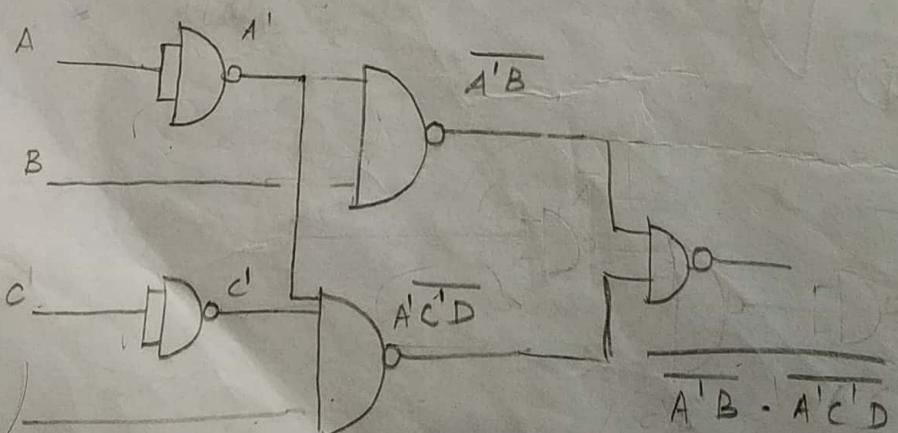
$$\begin{aligned} Y = \overline{\overline{y}} &= \overline{\overline{A'B} + \overline{A'C'D}} \\ &= \overline{\overline{A'}\overline{B} \cdot \overline{A'}\overline{C}\overline{D}} \end{aligned}$$



07.18

Mo



Min


$\bar{A} \bar{B}$

$\bar{A} B$

$A \bar{B}$

$A B$

only NOR

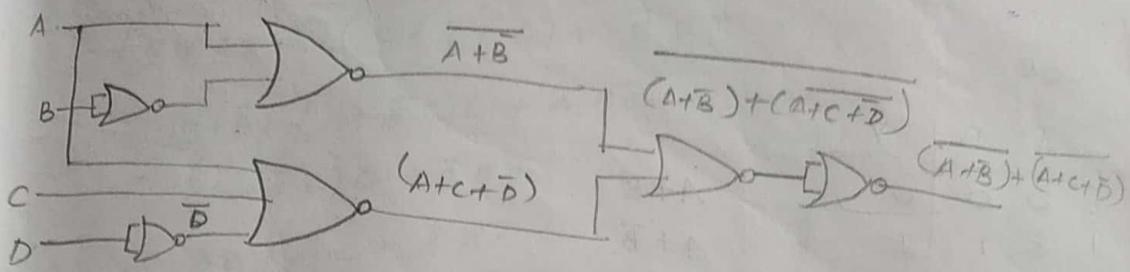

$$Y = \overline{A'B} \cdot \overline{A'C'D}$$

$$Y = (\bar{A} + \bar{B}) \cdot (\bar{A}' + \bar{C}' + \bar{D})$$


$$Y = (A + B) \cdot (A + C + \bar{D})$$

$$Y = (A + \bar{B}) + (A + C + \bar{D})$$

13.07.18

Maxterms and Minterms

OR

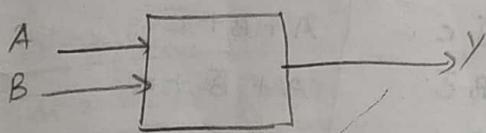

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Minterm:

$$\bar{A}\bar{B}$$

$$\bar{A}B$$

$$A\bar{B}$$

$$AB$$

0 → complemented

$$Y \bar{A} \text{ or } \bar{B}$$

canonical form → A (or) B

$$Y = \bar{A}B + A\bar{B} + AB \quad (\text{sum of pdts})$$

$$= B(\bar{A} + A) + A\bar{B}$$

$$= B + A\bar{B}$$

$$= (B + A)(\bar{B} + \bar{B})$$

$$= A + B \rightarrow \text{standard form}$$

→ consider only ones.

Max terms:

Sum of literals/variables

OR

| A | B | y |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 2 | 1 | 1 |
| 3 | 1 | 1 |

$$A+B$$

$$A+\bar{B}$$

$$\bar{A}+B$$

$$\bar{A}+\bar{B}$$

0 → A un complemented
1 → A complemented
(or) B

Max:

$$(A+B+C)$$

$$= (B+A)$$

$$= (B+A)$$

$$= B$$

$$=$$

$$=$$

$$Y = A+B$$

(plot of sum)

→ consider zeros.

Q)

| A | B | C | y | Min | Max |
|---|---|---|---|-------------------------|---------------------------|
| 0 | 0 | 0 | 0 | $\bar{A}\bar{B}\bar{C}$ | $A+B+C$ |
| 1 | 0 | 0 | 1 | $\bar{A}\bar{B}C$ | $A+B+\bar{C}$ |
| 2 | 0 | 1 | 1 | $\bar{A}B\bar{C}$ | $A+\bar{B}+C$ |
| 3 | 0 | 1 | 1 | $\bar{A}BC$ | $A+\bar{B}+\bar{C}$ |
| 4 | 1 | 0 | 0 | $A\bar{B}\bar{C}$ | $\bar{A}+B+\bar{C}$ |
| 5 | 1 | 0 | 0 | $A\bar{B}C$ | $\bar{A}+B+C$ |
| 6 | 1 | 1 | 0 | $AB\bar{C}$ | $\bar{A}+B+\bar{C}$ |
| 7 | 1 | 1 | 1 | ABC | $\bar{A}+\bar{B}+\bar{C}$ |

$$\begin{aligned}
 Y &= \bar{A}\bar{B}\bar{C} + \underline{\bar{A}\bar{B}\bar{C}} + \underline{\bar{A}B\bar{C}} + \underline{ABC} \\
 &= BC(\bar{A}+A) + \bar{A}\bar{B}C + \bar{A}B\bar{C} \\
 &= BC + \cancel{\bar{A}\bar{B}C} + \cancel{\bar{A}B\bar{C}} \\
 &= BC + \bar{A}(BC) \\
 &= \bar{A}B(C+\bar{C}) + C(\bar{A}\bar{B} + AB) \\
 &= \bar{A}B + C \\
 &= BC(\bar{A}+A) + \bar{A}\bar{B}C + \bar{A}B\bar{C} \\
 &= BC + \bar{A}\bar{B}C + \bar{A}B\bar{C}
 \end{aligned}$$

Max:

$$(A+B+C)$$

1. canonical

2. standard

sum
product

$$y = (A$$

$$= A$$

$$=$$

$\rightarrow A$ complemented
 $\rightarrow \bar{A}$ complemented
 (or) B

Max:

$$\begin{aligned}
 & (A+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C) \\
 & = (B+\bar{A}\bar{B}C)(C+\bar{A}\bar{B}C) + \bar{A}B\bar{C} \\
 & = (B+\bar{B})(B+\bar{A}C)C + \bar{A}B\bar{C} \\
 & = (B+\bar{A}C)C + \bar{A}B\bar{C} \\
 & = BC + \bar{A}(C+\bar{C})(C+B) \\
 & = BC + \bar{A}(B+C) \\
 & = BC + \bar{A}B + \bar{A}C
 \end{aligned}$$

std form
sum of pdt

Max:

$$(A+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)$$

[product of max terms] canonical

1. canonical form:
2. standard form

sum of Minterms. [all the variables are present]

Product of max terms.

sum of products

product of sums.

Q.

$$y = (A+A\bar{B}) \rightarrow \text{sum of pdt [std form]}$$

$$= A(B+\bar{B}) + A\bar{B}$$

$$= AB + A\bar{B} + A\bar{B}$$

$$= AB + A\bar{B} \rightarrow \text{sum of min terms [canonical form]}$$

$$= \Sigma(2, 3)$$

| | |
|-------|-------------|
| $A+B$ | $A+\bar{B}$ |
| 0 0 | 0 1 |
| 0 | 1 |

missing terms B means $B + \bar{B}$ takes

$B + \bar{B}$

takes

$$\begin{aligned}
 2. \quad y &= BC + \bar{A}B + \bar{A}C \rightarrow \text{sum of pdt} \\
 &= BC(A + \bar{A}) + \bar{A}B(C + \bar{C}) + \bar{A}C(B + \bar{B}) \\
 &= \underline{\underline{BCA}} + \underline{\underline{BC\bar{A}}} + \underline{\underline{\bar{A}BC}} + \underline{\underline{\bar{A}\bar{B}\bar{C}}} + \underline{\underline{\bar{A}CB}} + \underline{\underline{\bar{A}C\bar{B}}}
 \end{aligned}$$

$$\begin{aligned}
 &= ABC + \bar{A}BC + \bar{A}B\bar{C} + \bar{A}C\bar{B} \\
 &= \sum_m (1, 2, 3, 7)
 \end{aligned}$$

$$T_m = [(A+0+0)(\bar{A}+B+C)(\bar{A}+B+\bar{C})(\bar{A}+C+\bar{B})]$$

$$3. \quad y = (\bar{A} + \bar{B})(\bar{A} + B + \bar{C})(\bar{B} + C) \rightarrow \text{pdः of sum}$$

missing variable

$$\begin{aligned}
 &= (\bar{A} + \bar{B} + C\bar{C})(A + B + \bar{C})(A\bar{A} + \bar{B} + C) \rightarrow C\bar{C} \Rightarrow 0 \\
 &= (\bar{A} + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C}) \not\in A + B + \bar{C} (A + \bar{B} + C) \\
 &\quad (A + \bar{B} + C) \\
 &= \prod_m (1, 2, 6, 7)
 \end{aligned}$$

$$Q. 4. \quad y = (c' + d)(b + c')$$

$$5. \quad y = (b + cd)(c + bd)$$

$\sum (3)$

6. convert

$$4. \quad y = (c' + d)(b + c')$$

$$\Rightarrow \cancel{b\bar{c} + c}$$

$$= (\bar{c} + d + b\bar{c})(b + \bar{c} + d\bar{d})$$

$$= (\bar{c} + d + b)(\bar{c} + d + \bar{b})(b + \bar{c} + d)(b + \bar{c} + \bar{d})$$

$$= \underbrace{(b + \bar{c} + d)}_2 (\underbrace{\bar{b} + \bar{c} + d}_6) (\underbrace{b + \bar{c} + d}_{\cancel{d}})(b + \bar{c} + \bar{d}) \quad (if) F(A, B, C, D)$$

$$= \prod_m (2, 3, 6) \quad 3$$

$$= \sum_m (0, 1, 4, 5, 7)$$

6. convert
i) $f(x, y, z)$

j) $F(A, B, C, D)$

$$\begin{aligned}
 \text{So } y &= (b+c\bar{d})(c+b\bar{d}) \\
 y &= \cancel{(b(c+\bar{c})(d+\bar{d}) + c\bar{d}(b+\bar{b}))} \\
 &\quad \cancel{(b+\bar{b})c(d+\bar{d}) + (c+\bar{c})b\bar{d}} \\
 &= (b+c)(b+d)(c+b)(c+d) \\
 &= (b+c+d\bar{d}) \{ b\bar{d} + d + c\bar{c} \} (c+b+d\bar{d}) \{ c+d + b\bar{b} \} \\
 &= \cancel{(b+c+d)} \cancel{(b+c+\bar{d})} \cancel{(b+c+d)} \cancel{(b+\bar{c}+\bar{d})} \\
 &\quad \cancel{(b+c+d)} \cancel{(b+c+\bar{d})} \cancel{(b+c+d)} \cancel{(b+\bar{c}+\bar{d})} \\
 &= \pi(0, 1, 2, 4)
 \end{aligned}$$

$$= \Sigma(3, 5, 6, 7) = \pi(0, 1, 2, 4)$$

6. convert

6. convert to other canonical form. 0 - 8

$$\begin{aligned}
 \text{(i) } f(x, y, z) &= \Sigma(1, 3, 5) \rightarrow \pi(0, 2, 4, 6, 7, \cancel{8}) \\
 f(xyz) &= (\cancel{x}\cancel{y}z + \cancel{x}yz + x\cancel{y}z) \\
 &\quad \cancel{8} \quad \cancel{3} \quad \cancel{5}
 \end{aligned}$$

$$\begin{aligned}
 \text{(ii) } F(A, B, C, D) &= \pi(3, 5, 8, 11) \\
 &= \Sigma(0, 1, 2, 4, 6, 7, 9, 10, 12, 13, 14, 15)
 \end{aligned}$$

$\pi \Leftarrow \Sigma$

complemental to each other

$$F(A, B, C, D) = \prod (3, 5, 8, 11)$$

Karnaugh Map (K-Map)

Variables -

Q)

| | | | | | |
|---|-----------|-----------|------------------|--------------|--------|
| | 2 | 1 | B | $\bar{B}(0)$ | $B(1)$ |
| | A | \bar{A} | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB |
| 0 | \bar{A} | 0 | 0 | 1 | |
| 1 | A | 1 | \bar{A} | AB | 1 |


$A \rightarrow \text{MSB}$

$B \rightarrow \text{LSB}$

$\Rightarrow 2$ variable
K-map

Truth table:

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

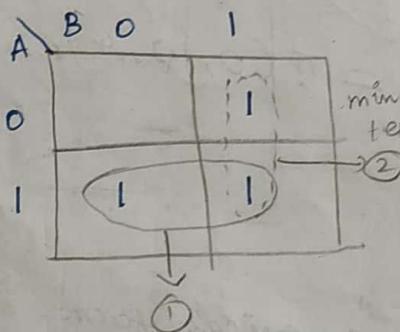

STEPS:

[consider

adjacent ones]

\Rightarrow only in vertical (or)
horizontal way.

\Rightarrow consider in
powers of 2
(ie) 1, 2, 4, 8, 16...

\Rightarrow group the higher
no. of adjacent
ones.

① $\rightarrow A$

② $\rightarrow B$

$$Y = A + B$$

| | | | |
|---|--|---|---|
| 1 | | | 1 |
| 1 | | 1 | 1 |

due to folding & combinations
are possible

$$F = \bar{C} + AB$$

3 Vari

AB

| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 2 | 0 | 0 |
| 3 | 0 | 1 |
| 4 | 1 | 0 |
| 5 | 1 | 0 |
| 6 | 1 | 1 |
| 7 | 1 | 1 |


1. $F(x, y, z)$

| | |
|-----------|----|
| A | BC |
| \bar{A} | O |
| A | I |

$$Y = B$$

3 Variable form

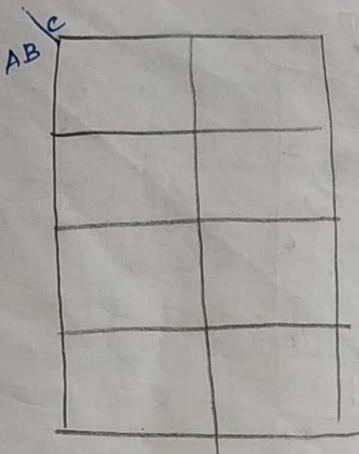[adjacent box \rightarrow 1 bit variation]



| | | A\BC | 00 | 01 | 101 | 10 |
|------|---|------|-------------------|-------------------|-------------------|-------------------|
| | | 0 | $\bar{A}\bar{B}C$ | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $\bar{A}B\bar{C}$ |
| | | 1 | $A\bar{B}\bar{C}$ | $A\bar{B}C$ | ABC | $A\bar{B}C$ |
| (or) | A | 0 | 0 | 1 | 3 | 2 |
| | | 1 | 4 | 5 | 7 | 6 |

Q)

| | A | B | C | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

| | | BC\B̄C | 00 | 01 | 101 | 10 |
|--|---|--------|----|----|-----|----|
| | | 0 | 1 | 1 | 1 | 1 |
| | | 1 | 0 | 1 | 1 | 1 |
| | A | 0 | 0 | 1 | 1 | 1 |
| | | 1 | 4 | 5 | 7 | 6 |

$$Y = \bar{A}C + \bar{A}B + BC$$

1. $F(x, y, z) = \Sigma(3, 4, 5, 7)$

| | | BC\B̄C | 00 | 01 | 11 | 10 |
|--|---|--------|----|----|----|----|
| | | 0 | 0 | 1 | 1 | 1 |
| | | 1 | 1 | 1 | 1 | 1 |
| | A | 0 | 0 | 1 | 1 | 1 |
| | | 1 | 4 | 5 | 7 | 6 |

$$Y = BC + \cancel{\bar{A}C} + \bar{A}\bar{B} + \cancel{\bar{A}C}$$


including
or excluding
give the same
value

$\boxed{1 \ 5 \ 7}$
redundant term

[not necessary]

4 Variable Map

- 16 square boxes.

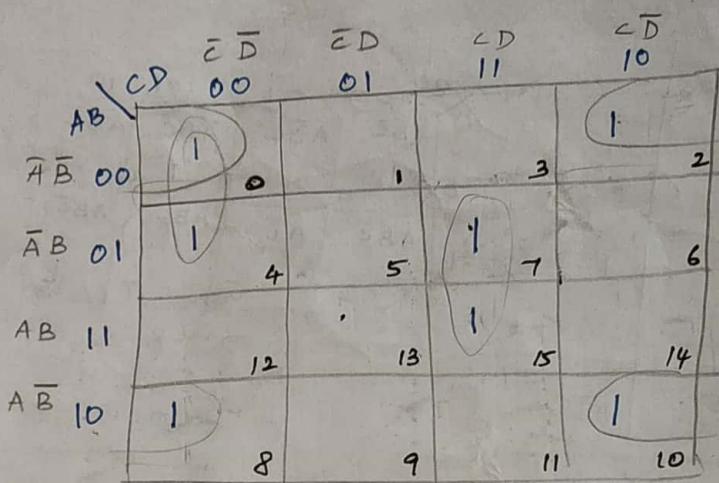


$$Y = \overline{B} \overline{D} + \overline{A} \overline{C} \overline{D} + B C D$$

17.07.18

Reduce the boolean expression using k-map.

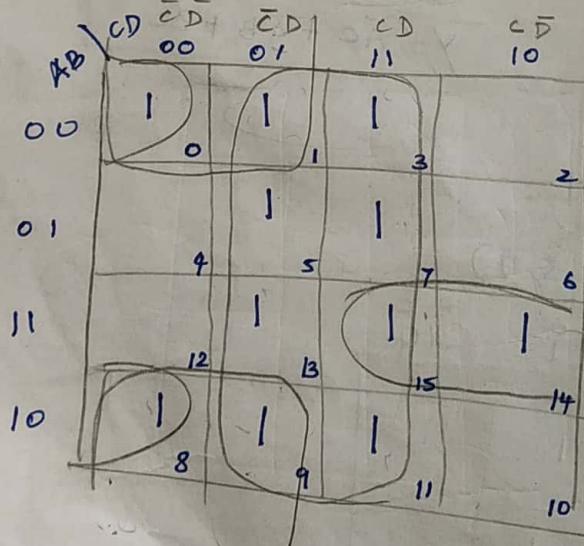1. $F(A, B, C, D) = \sum(0, 1, 3, 5, 7, 8, 9, 11, 13, 14, 15)$



$$Y = \overline{B} \overline{C} \overline{D} + \overline{D} + A B C$$

2. $F(A, B, C, D)$

$$\begin{array}{l} 0011 \\ 0101 \\ 0100 \\ 0011 \end{array}$$

$$\begin{array}{l} \overline{CD} 0 \\ AB \\ 00 \\ 01 \\ 11 \\ 10 \end{array}$$

3. $F(w, x, y)$

$$\begin{array}{l} y_1 \\ w+x \\ \overline{w}x \\ w\overline{x} \\ \overline{w}\overline{x} \end{array}$$

$$\begin{array}{l} \overline{w}z \\ w\overline{z} \\ wz \\ \overline{w}\overline{z} \end{array}$$

$$= w\bar{z}y(z)$$

$$= z w \bar{x}$$

$$(xw -$$

$$= \underline{\underline{wxzy}}$$

$$xw y \bar{z}$$

$$\overline{w} \bar{z} x$$

$$2. F(A, B, C, D) = \prod (5, 6, 7, 9, 10, 11, 13, 15) \\ = \sum (0, 1, 2, 3, 4, 8, 12, 14)$$

0 0 1 1 A B
1 0 1 A B
1 0 0 A B
0 1 1 A B

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | 1 | 1 | 1 | 1 |
| | 01 | 1 | 0 | 0 | 0 |
| 11 | 00 | 1 | 0 | 0 | 1 |
| | 10 | 1 | 0 | 0 | 0 |

$$= \bar{A}\bar{B} + \bar{C}\bar{D} + A\bar{B}\bar{D}$$

$$= (\bar{B}+\bar{D})(\bar{A}+\bar{D})(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C})$$

$$3. F(w, x, y, z) = w\bar{x}y + \bar{x}\bar{y}\bar{z} + y\bar{z} + \bar{w}\bar{z}$$

| | | yz | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| wx | 00 | 1 | 0 | 1 | 2 |
| | 01 | 1 | 4 | 5 | 6 |
| wx | 11 | 12 | 13 | 15 | 14 |
| | 10 | 1 | 8 | 9 | 11 |

~~wxyz~~

~~y = w~~

$$y = y\bar{z} + \bar{w}\bar{z} +$$

$$w\bar{x}y$$

$$y = y\bar{z} + w\bar{x}y + \bar{w}\bar{z} + \bar{x}\bar{z}$$

$$= w\bar{x}y(z+\bar{z}) + \bar{x}\bar{y}\bar{z}(w+\bar{w}) + (x+\bar{x})(w+\bar{w})y\bar{z} + \bar{w}\bar{z}(x+\bar{x})(y+\bar{y})$$


$$= w\bar{x}yz + w\bar{x}y\bar{z} + \bar{x}\bar{y}\bar{z}w + \bar{x}\bar{y}\bar{z}\bar{w} + (xw+x\bar{w}+\bar{x}w+\bar{x}\bar{w})y\bar{z} + \bar{w}\bar{z}(xy+x\bar{y}+\bar{x}y+\bar{x}\bar{y})$$

$$= \cancel{w\bar{x}yz} + w\bar{x}y\bar{z} + \bar{x}\bar{y}\bar{z}w + \bar{x}\bar{y}\bar{z}\bar{w} + xw\bar{y}\bar{z} + x\bar{w}y\bar{z} + \bar{x}wy\bar{z} + \bar{x}\bar{w}y\bar{z} + \bar{w}\bar{z}xy + \bar{w}\bar{z}x\bar{y} + \bar{w}\bar{z}\bar{x}y + \bar{w}\bar{z}\bar{x}\bar{y}$$

$$(11, 15, 8, 0, 14, 6, 10, 2, 5, 4, 2, 0)$$

$$(0, 1, 2, 4, 8, 6, 8, 10, 11, 14)$$
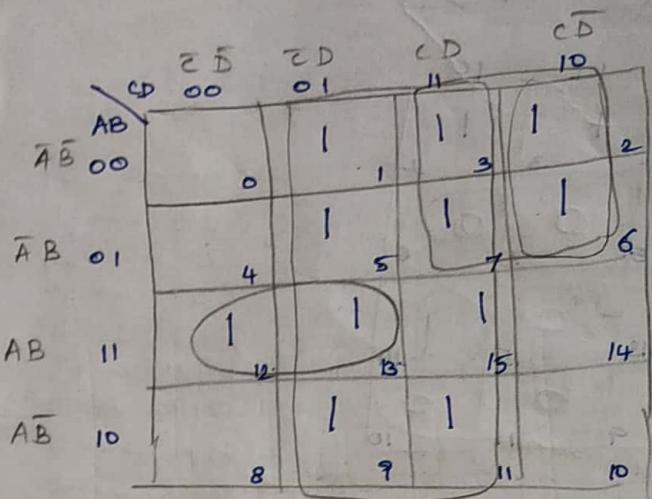
$$4. F = \sum (1, 2, 3, 5, 6, 7, 9, 11, 12, 13, 15)$$




$$Y = D + \bar{A}C + ABC$$

20/07/18

K-map with don't care. 'X'.

$$1. F () = \sum_m (2, 5, 7, 9, 11, 12, 14) + \sum_d (3, 4, 6)$$


↙
don't care. 'X'

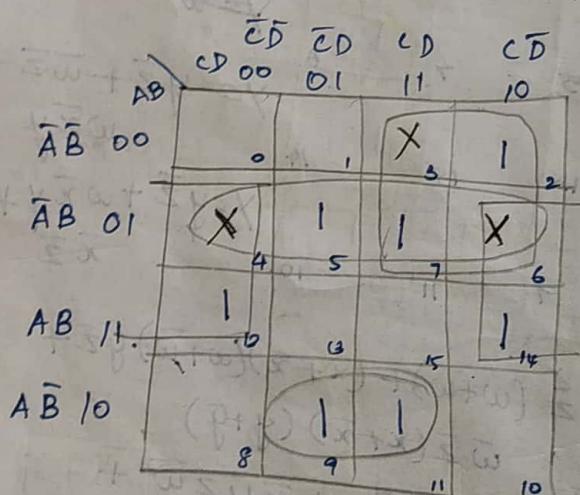

X → may be 1 (or) 0

$$F = \bar{A}B + \bar{A}C + B\bar{D} + A\bar{B}\bar{D}$$

3Q)

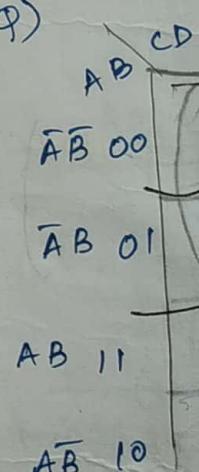

$Y = \bar{A}$

$X = A$

28)

$$F = \bar{x}\bar{y}z + x\bar{y}\bar{z} + x\bar{y}z$$

38. $F(ABCD) = \sum (0, 6, 8, 13, 14) -$
 $D(ABCD) = \sum (2, 4, 10)$

29). $F = \bar{x}yz + x\bar{y}\bar{z} + x\bar{y}z$

| | $\bar{y}\bar{z}$ 00 | $\bar{y}z$ 01 | $y\bar{z}$ 11 | yz 10 |
|------------|------------------------|------------------|------------------|------------|
| $\bar{x}0$ | 0 | 3 | 1 | 2 |
| $x1$ | 1 | 1 | 5 | 7 |
| | 4 | | 7 | 6 |

$$Y = x\bar{y} + \bar{x}yz$$

39)

| | $\bar{C}\bar{D}$ 00 | $\bar{C}D$ 01 | CD 11 | $C\bar{D}$ 10 |
|--------------------|------------------------|------------------|------------|------------------|
| $\bar{A}\bar{B}00$ | 1 | 0 | 3 | 2 |
| $\bar{A}\bar{B}01$ | X | 4 | 5 | 6 |
| $A\bar{B}11$ | 12 | 13 | 15 | 14 |
| $A\bar{B}10$ | 8 | 9 | 11 | 10 |

No need to map all x.


~~$$Y = \bar{A}\bar{C}\bar{D} + A.B\bar{C}D + \bar{B}\bar{C}\bar{D} \quad \bar{B}\bar{D} + \bar{A}\bar{D} + C\bar{D}$$~~

~~$$Y = ABCD + \bar{B}\bar{D} + \bar{A}\bar{D} + C\bar{D}$$~~

5 VARIABLE MAP. (0-31)

Q. $F = \sum (0, 1, 3, 5, 7, 9, 10, 11, 12, 15, 18, 19, 20, 21, 25, 30, 31)$

$F = \overline{CDE} + A$

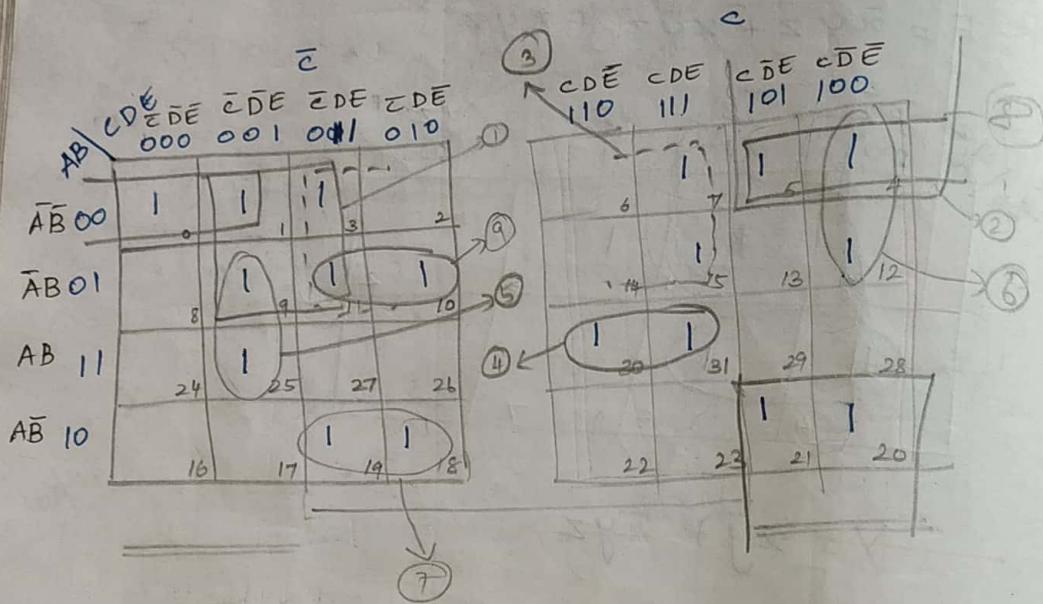


$$F = \overline{ACE} + \overline{ABD} + \overline{ADE} + ABCD + B\overline{CDE} + \overline{ACDE} + \\ A\overline{BCD} + \overline{BCD} + \overline{ABC}$$

TABULATION METHOD

5 Variable (Quine McHaleky Method)

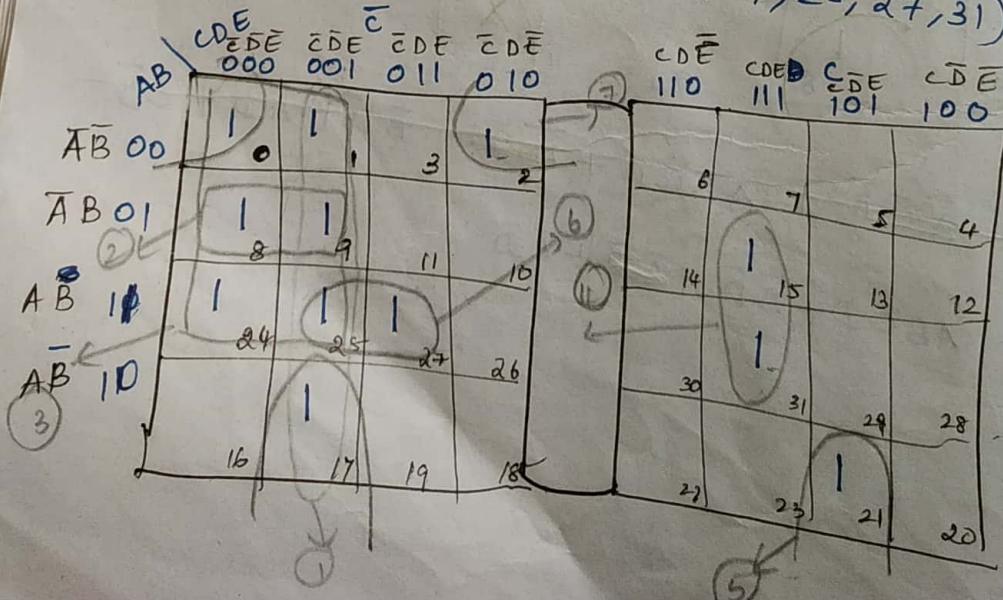Q. $F = \sum (0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31)$



Q. Total 6 groups

| |
|----|
| 0 |
| 1 |
| 2 |
| 8 |
| 9 |
| 17 |
| 24 |
| 21 |
| 25 |
| 15 |
| 27 |
| 31 |

Iteration

$$F = \cancel{E\bar{D}C} + \bar{A}\bar{C}\bar{D} + B\bar{C}\bar{D} + BCDE + A\bar{B}\bar{D}E + A\bar{B}\bar{C}E + \\ \bar{A}\bar{B}\bar{C}\bar{E}$$

TABULATION METHOD

(Quine McCluskey Method)

[consider the highest number]

→ convert into binary

→ group with no of ones

(-) → don't care symbol.

Iteration - 1

Q.

Total
6 groups

| | A | B | C | D | E | |
|----|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | ✓ |
| 1 | 0 | 0 | 0 | 0 | 1 | ✓ |
| 2 | 0 | 0 | 0 | 1 | 0 | ✓ |
| 8 | 0 | 1 | 0 | 0 | 0 | ✓ |
| 9 | 0 | 1 | 0 | 0 | 1 | ✓ |
| 17 | 1 | 0 | 0 | 0 | 1 | ✓ |
| 24 | 1 | 1 | 0 | 0 | 0 | ✓ |
| 21 | 1 | 0 | 1 | 0 | 1 | |
| 25 | 1 | 1 | 0 | 0 | 1 | ✓ |
| 15 | 0 | 1 | 1 | 1 | 1 | ✓ |
| 27 | 1 | 1 | 0 | 1 | 1 | ✓ |
| 31 | 1 | 1 | 1 | 1 | 1 | ✓ |

Iteration - 2

Iteration - 1

| | |
|----------|-----------|
| (0, 1) | 0000 - ✓ |
| (0, 2) | 000 - 0 |
| (0, 8) | 0 - 000 ✓ |
| (1, 9) | 0 - 001 ✓ |
| (1, 17) | - 0001 ✓ |
| (8, 9) | 0100 - ✓ |
| (8, 24) | - 1000 |
| (9, 25) | - 1001 ✓ |
| (17, 21) | 10 - 01 |
| (17, 25) | 1 - 001 ✓ |
| (24, 25) | 1100 - |
| (25, 27) | 110 - 1 |
| (15, 31) | - 111 1 |
| (27, 31) | 11 - 11 |

Iteration 2

| | |
|----------------|----------|
| (0, 1, 8, 9) | 0 - 00 - |
| (0, 8, 17, 25) | 0 - 00 - |
| (1, 9, 17, 25) | -- 001 |
| (1, 17, 9, 25) | - 001 |
| (8, 9, 24, 25) | - 100 - |
| (8, 24, 9, 25) | 100 - |

steps

1. Single entry from each column

Prime Implicants

| | |
|----------------|-----------------------------------|
| (0, 2) | $\bar{A} \bar{B} \bar{C} \bar{E}$ |
| (17, 21) | $A \bar{B} \bar{D} E$ |
| (28, 27) | $A \bar{B} \bar{C} E$ |
| (15, 31) | $B C D E$ |
| (27, 31) | $A B D E$ |
| (0, 1, 8, 9) | $\bar{A} \bar{C} \bar{D}$ |
| (1, 9, 17, 25) | $\bar{C} \bar{D} E$ |
| (8, 9, 24, 25) | $B \bar{C} \bar{D}$ |

| nts | Minterm | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | |
|--------|---------|---|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| (0, 2) | 0 | ✓ | ? | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 |

| P. Implicants | Minterm | 0 | 1 | 2 | 8 | 9 | 15 | 17 | 21 | 24 | 25 | 27 | 31 | steps |
|--------------------------------|------------------|---|---|-----|---|-----|----|----|----|----|----|----|----|--|
| $\bar{A}\bar{B}\bar{C}\bar{E}$ | (0, 2) \odot | x | * | (x) | | | | | | | | | | 1. Single entry from each column should be selected as essential P.I |
| $A\bar{B}\bar{D}E$ | (17, 21) \odot | | | | x | (x) | | | | | | | | 2. They have to be marked & put a tick mark |
| $\bar{A}\bar{B}\bar{C}E$ | (25, 27) | | | | | | x | | x | | | | | 3. their min terms are selected and ticked [on the top] |
| $B\bar{C}DE$ | (15, 31) \odot | | | | | | | | | x | | | | 4. The left over values are denoted as (?) |
| $\bar{A}BDE$ | (27, 31) | | | | | | | | | x | | | | (i.e) 1, 27 |
| $\bar{A}\bar{C}\bar{D}$ | (0, 1, 8, 9) | x | x | x | x | x | x | x | x | x | x | x | | |
| $\bar{C}\bar{D}E$ | (1, 9, 17, 25) | x | x | x | x | x | x | x | x | x | x | x | | |
| $B\bar{C}\bar{D}$ | (8, 9, 24, 25) | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | |

$$P =$$

$$\bar{A}\bar{B}\bar{C}\bar{E} + A\bar{B}\bar{D}E + BCDE + A\bar{C}\bar{D} + B\bar{C}\bar{D}$$

$$2. F = \{1, 3, 4, 5, 10, 11, 12, 13, 14, 15\}$$

| | A | B | C | D |
|----|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

[separate according to
no. of 1's]

PRIME impl.

(4, 5, 12, 1)

(10, 11, 14,

(12, 13, 14

(1, 3) -

(1, 5) -

(3, 11)

| P.I | Mint |
|-------------------|------|
| $\bar{A}\bar{B}D$ | (1 |
| $\bar{A}C\bar{D}$ | (1 |
| $\bar{B}C\bar{D}$ | (1 |
| $B\bar{C}$ | (1 |
| AC | (1 |
| AB | (1 |

| | A | B | C | D | Iteration-I | Iteration-II |
|-----|---|---|---|---|-----------------|-----------------------|
| | | | | | ABC'D | ABC'D |
| ✓1 | 0 | 0 | 0 | 1 | (1, 3) 00-1 | (4, 5, 12, 13) -10- |
| ✓4 | 0 | 1 | 0 | 0 | (1, 5) 0-01 | (4, 12, 5, 13) -10- |
| ✓3 | 0 | 0 | 1 | 1 | (4, 5) 010- ✓ | (10, 11, 14, 15) 1-1- |
| ✓5 | 0 | 1 | 0 | 1 | (4, 12) -100 ✓ | (10, 14, 11, 15) 1-1- |
| ✓10 | 1 | 0 | 1 | 0 | (3, 11) -011 | (12, 13, 14, 15) 11-- |
| ✓12 | 1 | 1 | 0 | 0 | (5, 13) -101 ✓ | (12, 14, 13, 15) 11-- |
| ✓11 | 1 | 0 | 1 | 1 | (10, 14) 1-10 ✓ | |
| ✓13 | 1 | 1 | 0 | 1 | (12, 13) 110- ✓ | |
| ✓4 | 1 | 1 | 1 | 0 | (12, 14) 11-0 ✓ | |
| ✓5 | 1 | 1 | 1 | 1 | (1, 15) 1-11 ✓ | |
| ✓15 | 1 | 1 | 1 | 1 | (13, 15) 11-1 ✓ | |
| | | | | | (14, 15) 111- ✓ | |

PRIME implicants:-

$$(4, 5, 12, 13) \rightarrow B\bar{C}$$

$$(10, 11, 14, 15) \rightarrow AC$$

$$(12, 13, 14, 15) \rightarrow AB$$

$$(1, 3) \longrightarrow \bar{A}\bar{B}D$$

$$(1, 5) \longrightarrow \bar{A}\bar{C}D$$

$$(3, 11) \longrightarrow \bar{B}CD$$

1
3
4
5
10
11
12
13
14
15

| P.I | Minterm | 1 | 3 | 4 | 5 | 10 | 11 | 12 | 13 | 14 | 15 |
|-------------------|------------------|---|---|---|---|----|----|----|----|----|----|
| $\bar{A}\bar{B}D$ | (1, 3) | x | x | | | | | | | | |
| $\bar{A}\bar{C}D$ | (1, 5) | x | | x | | | | | | | |
| $\bar{B}CD$ | (3, 11) | | x | | | x | | | | | |
| $B\bar{C}$ | (4, 5, 12, 13) | | | x | x | | | x | x | | |
| AC | (10, 11, 14, 15) | | | | x | x | | | x | x | |
| AB | (12, 13, 14, 15) | | | | | | x | x | x | x | |

$$\Rightarrow \bar{A}\bar{B}D + B\bar{C} + AC$$

27.7.18

HW

$$Q. F = (A, B, C, D) = \Sigma_m (0, 6, 8, 13, 14)$$

$$d (A, B, C, D) = \Sigma_d (2, 4, 10)$$

Follow the same procedure for both Σ
Exclude don't care in PI table.

| | | Iteration - I | Iteration - II |
|----|------|----------------|----------------------|
| 0 | 0000 | (0, 2) 00-0✓ | (0, 2, 4, 6) 0--0 |
| 1 | 0010 | (0, 4) 0-00✓ | (0, 2, 8, 10) -0-0 |
| 4 | 0100 | (0, 8) -000✓ | (0, 4, 2, 6) 0- -0 |
| 8 | 1000 | (2, 6) 0-10✓ | (2, 8, 2, 10) -0-0 |
| 6 | 0110 | (4, 6) 01-0✓ | (2, 6, 10, 14) - -10 |
| 10 | 1010 | (6, 14) -110✓ | (2, 10, 6, 14) - -10 |
| 13 | 1101 | (10, 14) 1-10✓ | |
| 14 | 1110 | | |

(Neglect the don't care terms in the table)

P.I

$$(0, 2, 4, 6) \rightarrow \bar{A}\bar{D}$$

$$(0, 2, 8, 10) \rightarrow \bar{B}\bar{D}$$

$$(2, 6, 10, 14) \rightarrow \bar{C}\bar{D}$$

$$0, 2, 4, 6, 8, /10, 14$$

| P.I | Minterms | 0 | 6 | 8 | 14 | 13 |
|--------------------------|----------------|---|---|---|----|----|
| $\bar{A}\bar{D}$ | (0, 2, 4, 6) | X | X | | | |
| $\bar{B}\bar{D}$ | (0, 2, 8, 10) | X | | X | | |
| $\bar{C}\bar{D}$ | (2, 6, 10, 14) | | X | | X | |
| $A\bar{B}\bar{C}\bar{D}$ | 13 | | | | | X |

$$ABC\bar{D} + \bar{A}\bar{D} + \bar{B}\bar{D} + C\bar{D}$$

7.7.18

Tutorial on Unit -1.

-

1. Do the following conversion:

- convert $(27.315)_{10}$ to binary
- $\leftrightarrow (C3DF)_{16}$ to binary
- $(26.24)_8$ to decimal
- $(DADA.B)_{16}$ to decimal

2. Obtain 1's and 2's complement of the number.

- 11011010
- 1010.1101

3. e. Perform subtraction using 2's complement of the subtrahend

- $1001 - 110101$
- $101000 - 10101$

4. Convert Perform the binary equivalent of 49 and 29 (of base 10) using signed 2's complement representation.

Then perform

- $(-29) + (+49)$
- $(-29) + (-49)$

convert the answer back to decimal and verify the result.

5. Convert the binary 1101110 to gray code.

6. Reduce the Boolean expression using boolean law.

A] $(A' + C)(A' + C')(A + B + C'D)$

for the reduced ^{eqn} draw circuit using universal gates.

7. Express the function

$(cd + b'c + bd')$ (b+d) sum of min terms &
pdt of max terms (canonical form)

8. Express convert A.F(x,y,z) = $\sum(1,3,5)$
to other canonical form.

B. $F(A,B,C,D) = \Pi(3,5,8,11)$

9. Convert:

A. $(u+xw)(x+u'v)$ into sum of pdt
and pdt of Scem (standard form)

10. Reduce using k-map

A. $F(w,x,y,z) = \sum(2,3,12,13,14,15)$

B. $F = w'z + xz + x'y + wz'$

c.

11. Using Tabulation method find the
reduced expression

A. $F = \sum(1,3,4,5,10,11,12,13,14,15)$

B. $F = \sum(5,6,7,12,14,15)$

$d = \sum(3,9,11,15)$

Verify the results using k-map.

A. (27.315)

| | |
|---|----|
| 2 | 27 |
| 2 | 13 |
| 2 | 6 |
| 2 | 3 |
| | 1 |

.315 X2

.63 X2

.26 X2

.52 X

:04 X

(27.315)

B. (C3D)

12

12

ANSWERS. for Tutorial on Unit -1

I. A. $(27.315)_{10} \rightarrow (11011.0101)_2$

$$\begin{array}{r} 27 \\ 2 | \quad \quad \\ 13 - 1 \\ 2 | \quad \quad \\ 6 - 1 \\ 2 | \quad \quad \\ 3 - 0 \\ 1 - 1 \end{array}$$

$$.315 \times 2 = 0.63$$

$$.63 \times 2 = 1.26$$

$$.26 \times 2 = 0.52$$

$$.52 \times 2 = 1.04$$

$$.04 \times 2 = 0.08$$

$$(27.315)_{10} \Rightarrow (11011.0101)_2$$

B. $(C3DF)_{16}$ to binary.

| | | | | | |
|----|----|----|----|----|----|
| A | B | C | D | E | F |
| 10 | 11 | 12 | 13 | 14 | 15 |

$$\begin{aligned}
 15 \times 16^0 &= 15 \\
 13 \times 16^1 &= 208 \\
 3 \times 16^2 &= 768 \\
 12 \times 16^3 &= 49,152
 \end{aligned}$$

$$\begin{aligned}
 15 \times 16^0 &= 15 \\
 13 \times 16^1 &= 208 \\
 3 \times 16^2 &= 768 \\
 12 \times 16^3 &= 49,152
 \end{aligned}$$

(or) $\underline{(1100\ 0011\ 1101\ 1111)_2} \quad (50143)_{10}$

C. $(26.24)_8$ to decimal:

$$\begin{array}{r} 26 \\ \times 8 \\ \hline 6 \\ + 2 \times 8^1 = 16 \\ \hline 22 \end{array}$$

$\cdot 24$

$$\begin{array}{r} 4 \times 8^{-1} = 0.5 \\ 2 \times 8^{-2} = 0.03125 \\ \hline 0.53125 \end{array}$$

$$(26.24)_8 = (22.053125)_{10}$$

D. $(DADA.B)_{16}$ to decimal:

$$\begin{array}{r} D A D A \\ | | | | \\ 10 \times 16^0 = 10 \\ 13 \times 16^1 = 208 \\ 10 \times 16^2 = 2560 \\ 13 \times 16^3 = 53,248 \\ \hline 56,027.6875 \end{array}$$

$$(DADA.B)_{16} = (56027.6875)_{10}$$

1's & 2's complement

A. 11011011

1's \rightarrow 0

2's

2's \rightarrow -

B. 1010.110

1's \rightarrow 2's

2's

3. Subtraction

A. 1001

0

(+) 0

0

B. 10100

(+) 0

1

2. 1's & 2's complement.

A. 11011010

$$1's \rightarrow 001\ 00101$$

2's

$$\begin{array}{r} 2's \rightarrow \\ + 1 \\ \hline 00100110 \end{array}$$

B. 1010.1101

$$1's \rightarrow 0101.0010$$

$$\begin{array}{r} 2's \\ + 1 \\ \hline 0110.0010 \end{array}$$

$$0101.0010$$

$$\begin{array}{r} 11001 + 1 \\ \hline 0101.0011 \end{array}$$

3. Subtraction

Answer

$$\begin{array}{r} 1001 - 0110101 \Rightarrow 2's \rightarrow 1001011 \\ 9 \quad 53 = -40 \\ 32 \quad 8 \quad 4 \quad 2 \quad 1 \\ 001001 \\ (+) 001001 \\ \hline 010100 \end{array}$$

$$\begin{array}{r} 000100 \\ 1001011 \\ 1010100 \\ 64+16+8+4=44 \\ (-) 010100 \\ \hline 32+8+4=44 \end{array}$$

$$B. 101000 - 10101 \Rightarrow 2's \rightarrow 1010101100$$

$$\begin{array}{r} 101000 \\ (+) 01011 \\ \hline 11111 \\ 101000 \\ (+) 101011 \\ \hline 100011 \\ 1010101100 \\ - 10101 \\ \hline 010011 \end{array}$$

(without 2's complement)



Note:

1's complement

$$\boxed{r^n - r^m - N}$$

For 2's complement

$$\boxed{r^n - N}$$

Using 2's complement:

$$2^5 \rightarrow \begin{array}{r} 10100 \\ 10101 \\ \hline 1010011 \\ \underbrace{11}_{\text{borrow}} \quad 1010 \end{array}$$

$$\begin{array}{r} 01010101 \\ 1010010010 \\ \hline 01100100 \end{array}$$

$$\begin{array}{r} (-29) + (+49) \\ -29 \rightarrow 111 \\ +49 \rightarrow \cancel{001} \\ \hline 1000 \end{array}$$

$$\begin{array}{r} i) (-29) + (-49) \\ -29 \rightarrow 111 \\ -49 \rightarrow \cancel{111} \\ \hline 111 \end{array}$$

$$(-29) + (+49)$$

$$\begin{array}{r} 49 \\ 2 \overline{)49} \\ 2 \overline{)24} -1 \\ 2 \overline{)12} -0 \\ 2 \overline{)6} -0 \\ 2 \overline{)3} -0 \\ 1 -1 \end{array}$$

$$\begin{array}{r} 29 \\ 2 \overline{)29} \\ 2 \overline{)14} -1 \\ 2 \overline{)7} -0 \\ 2 \overline{)3} -1 \\ 1 -1 \end{array}$$

$$(49)_{10} \rightarrow (110001)_2$$

$$(-29)_{10} \rightarrow (11101)_2$$

Sign Magnitude Form.

| | Sign Mag. | 1's | 2's |
|-----|-----------|----------|----------|
| +49 | 00110001 | 00110001 | 00110001 |
| -49 | 10110001 | 11001110 | 11001111 |
| 29 | 00011101 | 00011101 | 00011101 |
| +29 | 00011101 | 00011101 | 00011101 |
| -29 | 10011101 | 11100010 | 11100011 |

$$(-29) + (-49)$$

$$64 \leftarrow$$

(Translating 3's complement form)

$$(i) (-29) + (+49)$$

$$\begin{array}{r} -29 \rightarrow 11100011 \\ +49 \rightarrow 00110001 \\ \hline 100010100 \end{array}$$

$$\begin{array}{r} 49 \\ -29 \\ \hline 20 \end{array}$$

$$(ii) (-29) + (-49)$$

$$\begin{array}{r} -29 \rightarrow 11100011 \\ -49 \rightarrow 11001111 \\ \hline 110110010 \end{array}$$

$$110110010$$

$$\begin{array}{r} 25 \\ 25 \\ \hline 01001110 \end{array}$$

$$(-29) + (+49) \Rightarrow 20 \quad [\text{To verify (i)}]$$

$$\begin{array}{r} 00010100 \\ | \quad | \quad | \quad | \quad | \quad | \\ \rightarrow 0 \times 2^0 = 0 \\ \rightarrow 0 \times 2^1 = 0 \\ \rightarrow 1 \times 2^2 = 4 \\ \rightarrow 0 \times 2^3 = 0 \\ \rightarrow 1 \times 2^4 = 16 \end{array}$$

$$20 \rightarrow (i) \text{ is verified}$$

$$(-29) + (-49) \Rightarrow 01001110$$


$$\begin{array}{r} 64 \leftarrow 1 \times 2^6 \\ | \quad | \quad | \quad | \quad | \quad | \quad | \\ \rightarrow 0 \times 2^0 \\ \rightarrow 1 \times 2^1 \Rightarrow 2 \\ \rightarrow 2^2 \Rightarrow 4 \\ \rightarrow 2^3 \Rightarrow 8 \\ \rightarrow 0 \times 2^4 \\ \rightarrow 0 \times 2^5 \end{array}$$

$$2 + 4 + 8 + 64 = 78 \rightarrow (ii) \text{ is verified.}$$

Note:


(2m)

BINARY TO GRAY

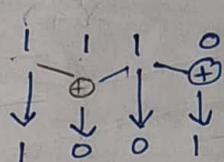

→ 1st no as it is
→ next nos take X-OR

GRAY TO BINARY

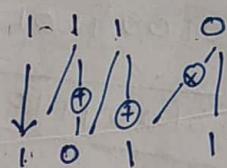

→ next nos ans value
take X-OR.

5. Convert binary $1101110 \Rightarrow$ gray code

1101110

\downarrow

$1011001 \Rightarrow$ gray code.

6. Reduce the boolean expression using Boolean law.

$$A' + c)(A' + c')(A + B + c'D)$$

Using distribution law

$$(A' + c)c'(A + B + c'D) = (A' + c')(A + B + c'D)$$

$$= A'(A + B + c'D)$$

$$= A'A + A'B + A'C'D$$


$$= A'B + A'C'D$$

$$= A'(B + C'D)$$

implementation

ONLY US
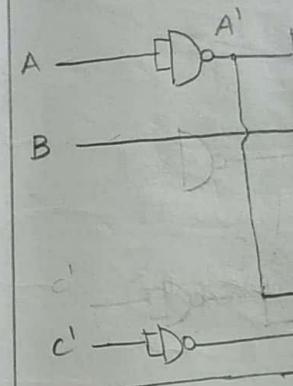
$$y = A'B + \\ \overline{y} = \overline{\overline{A'B}}$$



⇒

$$y = A'B$$

$$y = \overline{A'B}$$

$$y = \overline{\overline{A'B}}$$

=

=


(2m)

implementation using universal logic gates:

ONLY USING NAND AND NOR

$$\text{LHS } Y = A'B + A'C'D$$
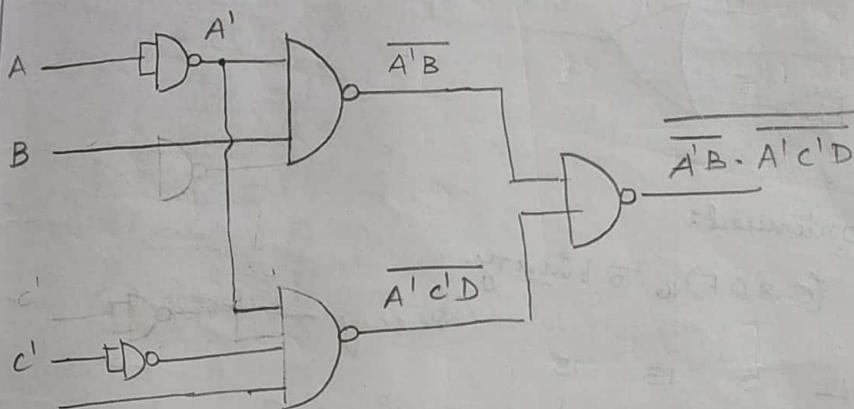
$$\bar{Y} = \overline{\overline{A'}B \cdot \overline{A'C'D}} \Rightarrow \text{Only using NAND}$$



\Rightarrow only using NOR

$$Y = A'B + A'C'D$$


$$Y = \overline{\overline{A'}B \cdot \overline{A'C'D}}$$

$$Y = (\overline{A'} + \overline{B}) \cdot (\overline{A'} + \overline{C} + \overline{D})$$

$$= \overline{(A + B)} \cdot \overline{(A + C + D)}$$

$$= (A + \overline{B}) + \overline{A + C + D}$$
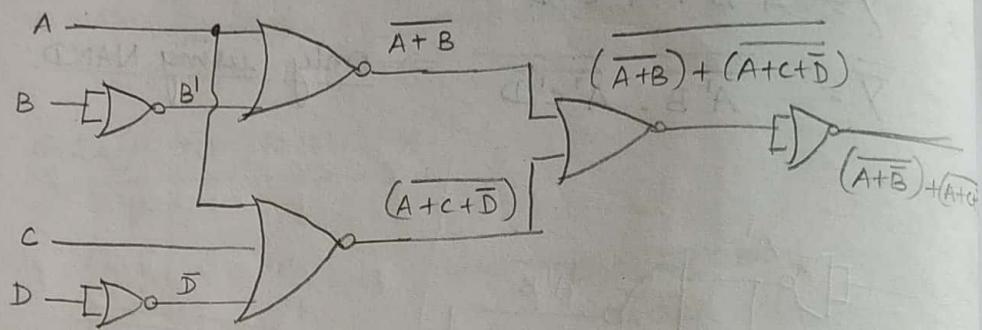
$$Y = \overline{(A+B)} + (\overline{A+C+D})$$



1. (B) continued:

$(CBDF)_{16}$ to binary.

(hexa \rightarrow decimal)

$$\begin{array}{cccc}
 12 & 3 & 13 & 15 \\
 | & | & | & | \\
 \hline
 & & & \rightarrow 15 \times 16^0 = 15 \\
 & & & \rightarrow 13 \times 16^1 = 208 \\
 & & & \rightarrow 3 \times 16^2 = 768 \\
 & & & \rightarrow 12 \times 16^3 = 49,152 \\
 & & & \hline
 & & & \underline{(50143)_{10}}
 \end{array}$$

(decimal \rightarrow binary)

- Repeated division by 2

$$\underline{2 | 50143}$$

$$\text{Ans} \Rightarrow (1100 \ 0011 \ 1101 \ 1111)_2$$

decimal to binary

| | |
|---|-----------|
| 2 | 50 143 |
| 2 | 250 71 -1 |
| 2 | 125 35 -1 |
| 2 | 62 67 -1 |
| 2 | 31 33 -1 |
| 2 | 15 66 -1 |
| 2 | 7 83 -0 |
| 2 | 3 91 -1 |
| 2 | 1 95 -1 |
| 2 | 0 97 -1 |
| 2 | 0 48 -1 |
| 2 | 0 24 -0 |
| 2 | 0 12 -0 |
| 2 | 0 6 -0 |
| 2 | 0 3 -0 |
| | 1 -01 |

$$\Rightarrow (110000111101111)_2$$

7. Express the function

$(cd + b'c + bd')(b+d)$ sum of min terms &
pdt of max terms (CANONICAL FORM)

$$\Rightarrow (cd + b'c + bd')(b+d)$$

sum of min terms:-

$$\begin{aligned}
 F &= bcd + b b' c + b d' + cd + b' c d + b d d' \\
 &= bcd + b(c+c')d' + (b+b')cd + b'cd \\
 &= bcd + bcd' + b'c'd' + \cancel{bcd} + \cancel{b'cd} + \cancel{b'cd}
 \end{aligned}$$

111 110 100 011
 7 6 4 3

$$\Sigma_m (3, 4, 6, 7)$$

Pdt of max terms:-

$$\begin{aligned} &= \underline{bcd + bcd' + bc'd' + b'cd} \\ &= cd(b+b') + bd'(c+c') \\ &= cd + bd' \\ &\Rightarrow bd' + cd \quad \text{By distributive law} \\ &= (bd'+c)(bd'+d) \\ &= (b+c)(d'+c)(b+d)(d+d') \\ &= (b+c+dd')(bb'+c+d')(b+cc'+d) \\ &= \cancel{(b+c+d)} \cancel{(b+c+d')} \\ &\quad \cancel{(b+c+d')} \cancel{(b'+c+d')} \\ &\quad \cancel{(b+c+d)} \cancel{(b+c'+d)} \\ &= \cancel{(b+c+d)} \cancel{(b+c+d')} \cancel{(b'+c+d')} \cancel{(b+c'+d)} \\ &= \pi_m(0, 1, 2, 5) \end{aligned}$$

8. Convert

A.) $F(x,y,z) = \sum(1, 3, 5)$
 $= \pi(0, 2, 4, 6, 7)$

B.) $F(A, B, C, D) = \pi(3, 5, 8, 11)$
 $= \sum(0, 1, 2, 4, 6, 7, 9, 10, 12, 13, 14, 15)$
 $= \sum(0, 1, 2, 4, 6, 7, 9, A, C, D, E, F)$

9. Convert:

A. $(u+xw)(x+u'v)$ into sum of pdt and pdt of sum [standard form]

sum of pdt:

$$\begin{aligned} & (u+xw)(x+u'v) \\ &= \cancel{ux + x'} \quad ux + \cancel{u u' v}^{\uparrow 10} + xw x + xw u' v \\ &= ux + xw u' v + xw \leftarrow \text{sum of pdt.} \end{aligned}$$

Pdt of sum:

$$\begin{aligned} & (u+xw)(x+u'v) \quad \text{Using distribution law,} \\ & (u+xw u' v)(x+xw u' v) \\ \Rightarrow & (u+x)(u+w)(u+u') \cancel{(u+v)}^{\uparrow 10} (x+x) \\ & (x+w)(x+u')(x+v) \\ \Rightarrow & (u+x)(u+w)(u+v)(x+w)(x+u')(x+v) \\ \Rightarrow & (u+x)(u+w) \frac{\text{Pdt of sum}}{(x+u')(x+v)} \end{aligned}$$

10. Reduced using k-map.

A. $F(w, x, y, z) = \Sigma(2, 3, 12, 13, 14, 15)$

| w | y | z | $\bar{y}\bar{z}$ | $\bar{y}z$ | yz | $y\bar{z}$ |
|------------------|----|----|------------------|------------|------|------------|
| $\bar{w}\bar{x}$ | 00 | 00 | 00 | 01 | 11 | 10 |
| $\bar{w}x$ | 01 | 01 | 01 | 10 | 10 | 11 |
| w | 11 | 11 | 12 | 13 | 15 | 14 |
| $w\bar{x}$ | 10 | 10 | 01 | 01 | 11 | 10 |

$$F(w, x, y, z) = w\bar{x} + \bar{w}\bar{x}y$$

B. $F = w'z + xz + x'y + wx'z$

| wx | $y^2\bar{y}\bar{z}$ | \bar{y}^2 | yz | $y\bar{z}$ |
|------------|---------------------|-------------|------|------------|
| $w\bar{x}$ | 00 | 00 | 11 | 10 |
| wx | 01 | 01 | 11 | 11 |
| $w\bar{x}$ | 11 | 12 | 13 | 14 |
| wx | 10 | 10 | 11 | 10 |
| | 8 | 9 | 11 | 10 |

10 x 42

$x'yz'$

$$F(w, x, y, z) = z + x'y$$

10. Using tabulation method find the reduced expression:-

A. $F = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$

| | A | B | C | D |
|----|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

| A |
|----|
| 1 |
| 4 |
| 3 |
| 5 |
| 10 |
| 12 |
| 11 |
| 13 |
| 14 |
| 15 |

Min terms

✓(1,3)

1,5

3,11

✓12,5,11

10,11,14,1

12,13,14,1

xyz'

| | A | B | C | D | | Iteration-I | | Iteration-II |
|----|---|---|---|---|---|-----------------|--|--------------|
| 1 | 0 | 0 | 0 | 1 | ✓ | (1,3) 00-1° | | |
| 4 | 0 | 1 | 0 | 0 | ✓ | (1,5) 0-01° | | |
| 3 | 0 | 0 | 1 | 1 | ✓ | (4,5) 010- ✓ | | |
| 5 | 0 | 1 | 0 | 1 | ✓ | (4,12) -100 ✓ | | |
| 10 | 1 | 0 | 1 | 0 | ✓ | (3,11) -011° | | |
| 12 | 1 | 1 | 0 | 0 | ✓ | (5,13) -101° | | |
| 11 | 1 | 0 | 1 | 1 | ✓ | (10,14) 1-10 ✓ | | |
| 13 | 1 | 1 | 0 | 1 | ✓ | (12,13) 110- ✓ | | |
| 14 | 1 | 1 | 1 | 0 | ✓ | (11,15) 1-11+ ✓ | | |
| 15 | 1 | 1 | 1 | 1 | ✓ | (13,15) 11-1 ✓ | | |
| | | | | | | (14,15) 111- ✓ | | |

PRIME IMPlicants:

- (1,3) - $\bar{A}\bar{B}D$
- (1,5) - $\bar{A}\bar{C}D$
- (3,11) - $\bar{B}CD$
- (4,12,5,13) - $B\bar{C}$
- (10,11,14,15) - AC
- (12,13,14,15) - AB

| Min terms | P.I | 1° | 3° | 4 | 5 | 10 | 11 | 12 | 13 | 14 | 15 |
|----------------|-------------------|----|----|---|---|----|----|----|----|----|----|
| ✓(1,3) | $\bar{A}\bar{B}D$ | x | x | | | | | | | | |
| 1,5 | $\bar{A}\bar{C}D$ | x | | x | | | | | | | |
| 3,11 | $\bar{B}CD$ | | x | | | x | | | | | |
| ✓(12,5,13) | $B\bar{C}$ | | | x | x | | x | x | | | |
| ✓(10,11,14,15) | AC | | | | x | x | | | x | x | |
| ✓(12,13,14,15) | AB | | | | | x | x | x | x | x | |

$$F = \bar{A}\bar{B}D + B\bar{C} + AC.$$

$$F = \bar{A}\bar{B}D + B\bar{C} + AC.$$

Verification using K-map $F = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$

| $\bar{A}\bar{B}$ | CD | $\bar{C}\bar{D}$ | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|------|------------------|------------|------|------------|
| $\bar{A}B$ | 00 | 00 | 01 | 11 | 10 |
| $A\bar{B}$ | 01 | 11 | 11 | 11 | 10 |
| AB | 11 | 11 | 11 | 11 | 11 |
| $A\bar{B}$ | 10 | - | - | 11 | 10 |
| | 8 | 9 | 11 | 11 | 10 |

$$F = A\bar{B}\bar{C} + AC + \bar{A}\bar{B}D$$

Hence verified.

B. $F = \sum(5, 6, 7, 12, 14, 15)$

$d = \sum(3, 9, 11)$

| | A | B | C | D |
|----|---|---|---|---|
| 3 | 0 | 0 | 1 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

| | A | B |
|----|---|---|
| 3 | 0 | 0 |
| 5 | 0 | 1 |
| 6 | 0 | 1 |
| 9 | 1 | 0 |
| 12 | 1 | 1 |
| 7 | 0 | 1 |
| 11 | 1 | 0 |
| 14 | 1 | 1 |
| 15 | 1 | 1 |

| Min terms | P: |
|---------------|-----------|
| ✓5, 7 | \bar{A} |
| ✓9, 11 | A |
| ✓12, 14 | A |
| ✓3, 7, 11, 15 | C |
| ✓6, 7, 14, 15 | C |

| F |
|--------------------|
| $\bar{A}\bar{B}00$ |
| $\bar{A}B01$ |
| $AB11$ |
| $A\bar{B}10$ |

5, 10, 11, 12, 13, 14, 15

| | A | B | C | D | Iteration-1 | Iteration-2 |
|----|---|---|---|---|-----------------|--|
| 3 | 0 | 0 | 1 | 1 | (3, 7) 0-11 ✓ | (3, 7, 11, 15) ABC'D --11 |
| 5 | 0 | 1 | 0 | 1 | (3, 11) -011 ✓ | (3, 11, 7, 15) --11 |
| 6 | 0 | 1 | 1 | 0 | (5, 7) 01-10 | (6, 7, 14, 15) -11- |
| 9 | 1 | 0 | 0 | 1 | (6, 14) -110 ✓ | (6, 14, 7, 15) -11- |
| 12 | 1 | 1 | 0 | 0 | (9, 11) 10-10 | |
| 7 | 0 | 1 | 1 | 1 | (12, 14) 11-D 0 | (5, 7) A BD |
| 11 | 1 | 0 | 1 | 1 | (7, 15) -111 ✓ | (9, 11) A B A B D |
| 14 | 1 | 1 | 1 | 0 | (11, 15) 1-11 ✓ | (12, 14) ABD |
| 15 | 1 | 1 | 1 | 1 | (14, 15) 111- ✓ | (3, 7, 11, 15) → CD |
| | | | | | | (6, 7, 14, 15) → BC |

| Min terms | P.I | 3 | 5 | 6 | 7 | 9 | 12 | 14 | 15 |
|---------------|-------------|-----|-----|---|---|-----|----|----|----|
| ✓5, 7 | $\bar{A}BD$ | (X) | | | X | | | | |
| ✓9, 11 | $A\bar{B}D$ | | | | | | | | |
| ✓12, 14 | $AB\bar{D}$ | | | | | (X) | | X | |
| ✓3, 7, 11, 15 | CD | | | | X | | | | X |
| ✓6, 7, 14, 15 | BC | | (X) | X | | | X | X | |

$$F = \bar{A}BD + A\bar{B}D + BC$$

| AB | CD | 00 | 01 | 11 | 10 | |
|------------------|----|----|----|----|----|---------------------------|
| $\bar{A}\bar{B}$ | 00 | 0 | 1 | 3 | 2 | verification using k-map. |
| $\bar{A}B$ | 01 | 4 | 5 | 1 | 1 | |
| AB | 11 | 1 | X | 1 | 1 | Hence Verified. |
| $A\bar{B}$ | 10 | 8 | X | X | 10 | |
| | | 9 | | 11 | | |

$$F = BC + \bar{A}BD + A\bar{B}D$$


31.07.8

Unit - II combinational circuits

Digital logic circuits

- combinational sequential
 o/p depends upon present i/p (Flip flops)
- Half Adder
 - Full Adder.
 - Ripple carry adder
 - Parallel adder)
 - Mux
 - De Mux
 - Decoder
 - Encoder
 - Comparator
 - Register
 - Counter
 - Shift register
 - ALU
 - Memory
 - Control Unit

Eg:- 1. Half Adder.

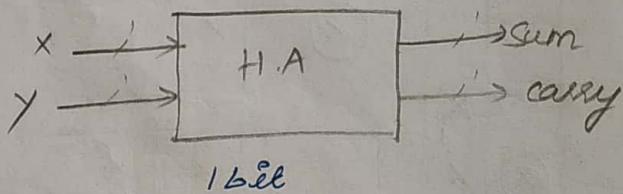

| x | y | sum | carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$\text{Sum} = \bar{x}y + x\bar{y} = x \oplus y$$

$$\text{carry} = xy$$


Full Adder

X —
Y —
Cor —
Input —
Carry —


| x | y |
|---|----|
| 0 | 00 |
| 1 | 00 |
| 2 | 01 |
| 3 | 01 |
| 4 | 10 |
| 5 | 10 |
| 6 | 11 |
| 7 | 11 |

| x | y | z |
|---|----|----|
| 0 | 00 | yz |
| 1 | 01 | 00 |

| x | y | z |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 1 | 1 |

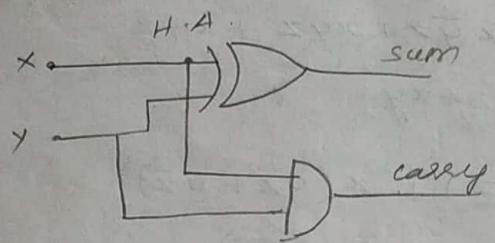

Full Adder:

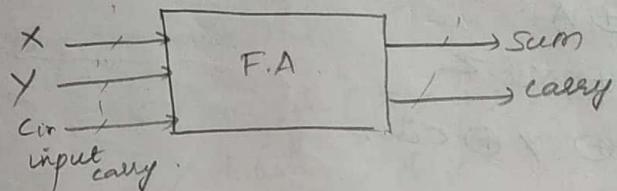

| x | y | cin | sum | carry |
|---|---|-----|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 2 | 0 | 1 | 1 | 0 |
| 3 | 0 | 1 | 0 | 1 |
| 4 | 1 | 0 | 1 | 0 |
| 5 | 1 | 0 | 0 | 1 |
| 6 | 1 | 1 | 0 | 1 |
| I | 1 | 1 | 1 | 1 |

| | | Sum | | | |
|-----------|----|------------------|------------|------------|------|
| | | $\bar{y}\bar{z}$ | $\bar{y}z$ | $y\bar{z}$ | yz |
| | | 00 | 01 | 11 | 10 |
| \bar{x} | 00 | 0 | 1 | 1 | 2 |
| x | 01 | 1 | 0 | 1 | 6 |

$$F \Rightarrow \text{sum} \Rightarrow x\bar{y}\bar{z} + \bar{x}\bar{y}z + xy\bar{z} + \bar{x}yz$$

| $\bar{y}\bar{z}$ | $\bar{y}z$ | $y\bar{z}$ | yz |
|------------------|------------|------------|------|
| 0 | 0 | 1 | 3 |
| 1 | 4 | 5 | 7 |
| | | | 6 |

$$\text{carry} \Rightarrow \cancel{yz} + \cancel{xz} + \cancel{xy} \\ \underline{yz + xz + xy}$$

$$\text{sum: } xy\bar{z} + \bar{x}\bar{y}z + xyz + \bar{x}y\bar{z}$$

$$\text{carry: } yz + xz + xy$$

$$\xrightarrow{\text{sum:}} \bar{x}(\bar{y}z + y\bar{z}) + x(yz + \bar{y}\bar{z}) \\ \bar{x}(\underbrace{y \oplus z}_A) + x(\underbrace{y \odot z}_{\bar{A}})$$

$$= \bar{x}A + x\bar{A}$$

$$= x \oplus A$$


$$= x \oplus y \oplus z$$

$$= x \oplus y \oplus \text{cin.}$$

$$\text{carry: } yz + xz + xy$$

$$\cancel{x(z+y)} + yz$$

$$= xy + y \text{cin} + x \text{cin.}$$

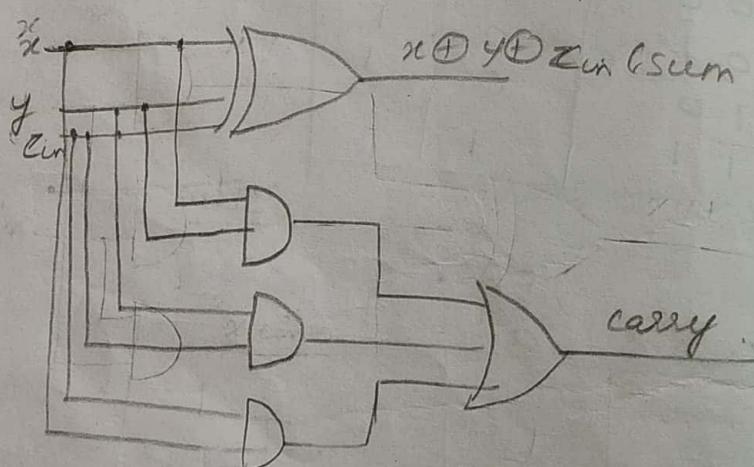

Half Adder

Full Adder


Carry:

=


=

Using

carry
sum

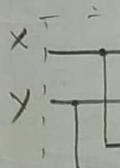

Half Adder

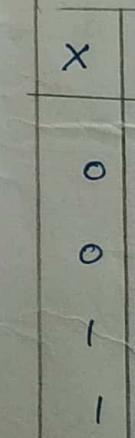

Half Adder..

1. Full Adder using 2 half adder & one OR gate.

carry: $XY + Y_{cin} + X_{cin}$.

$$= XY + (X + \bar{X})Y_{cin} + X(Y + \bar{Y})_{cin}$$

$$= XY + XY_{cin} + \bar{X}Y_{cin} + XY_{cin} + X\bar{Y}_{cin}$$


$$= \underbrace{XY}_{\text{sum}} + \underbrace{\bar{X}Y_{cin} + X\bar{Y}_{cin}}_{\text{carry}}$$

Using absorption law: $(A+AB=A)$

$$= XY + \text{cin}(\bar{X}Y + X\bar{Y})$$

$$\underline{\text{carry}} = XY + \text{cin}(X \oplus Y)$$
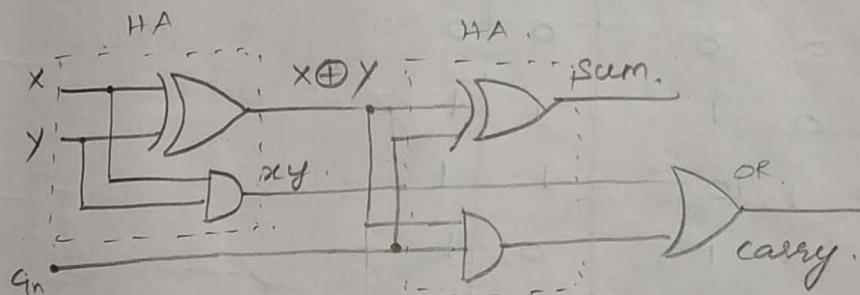
$$\underline{\text{sum}} = X \oplus Y \oplus \text{cin}$$



2. Half Subtractor.

| X | Y | diff (D) | borrow (B) |
|---|---|-------------|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

Difference:

$$D = \bar{X}Y + X\bar{Y}$$


$$= X \oplus Y$$

Borrow

$$B = \bar{X}Y$$

Difference: $x \oplus y$

Borrow: $\bar{x}y$.

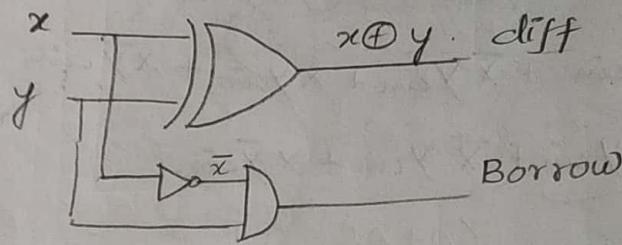

FULL SUBTRACTOR:

| x | y | c_{in} | D | B |
|-----|-----|----------|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 1 | 1 |
| 3 | 0 | 1 | 0 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 0 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 1 |

$$\begin{array}{r} D \\ 10 \\ - 1 \\ \hline 1 \end{array}$$

| x | y | c_{in} | D | B |
|-----|-----|----------|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 1 | 1 |
| 3 | 0 | 1 | 0 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 0 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 1 |

| x | y | c_{in} | D | B |
|-----|-----|----------|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 1 | 1 |
| 3 | 0 | 1 | 0 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 0 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 1 |

$$\text{Difference } D = x\bar{y}\bar{c}_{in} + \bar{x}\bar{y}c_{in} + xyc_{in} + \bar{x}y\bar{c}_{in}$$
$$D = \overline{x \oplus y \oplus c_{in}}$$


| | $y_{in} \bar{y}_c$ | \bar{y}_c | y_c | \bar{y}_c |
|-----------|--------------------|-------------|-------|-------------|
| x | 0 | 1 | 1 | 1 |
| \bar{x} | 0 | 1 | 1 | 1 |
| x | 4 | 5 | 17 | 6 |

$$B = \bar{x}C_{in} + \bar{x}y + yc$$

$$\boxed{B = \bar{x}C + \bar{x}y + yc}$$

= $\bar{x}y + yc$

2 half sub
+ R,

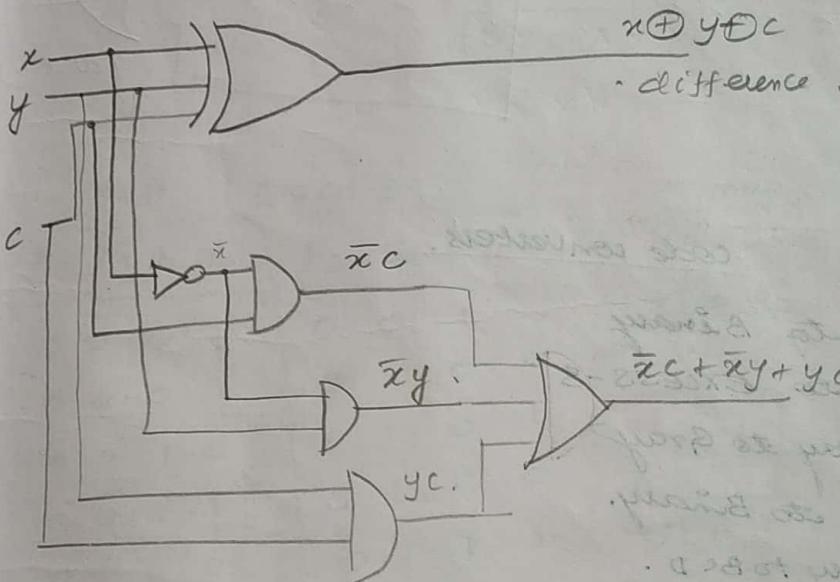

$$B = \bar{x}c + \bar{x}y + yc$$

$$= \bar{x}y + \bar{x}(y + \bar{y})c + (x + \bar{x})yc$$

$$= \underbrace{\bar{x}y}_{\cancel{x}y(1c)} + \underbrace{\bar{x}yc}_{c(\bar{x}\bar{y} + xy)} + \underbrace{\bar{x}\bar{y}c}_{xy} + \underbrace{xy}_{\cancel{xy}} + \underbrace{\bar{x}yc}_{\cancel{xy}c}$$

$$= \bar{x}y + c \oplus xy + \bar{x}yc$$

$$= \bar{x}y + \bar{x}\bar{y}c + xy$$


$$= \bar{x}y + c(\bar{x}\bar{y} + xy)$$

$$= \cancel{\bar{x}y + c \oplus \bar{x}y} (x \oplus y)$$

$$B = \bar{x}y + c(x \oplus y)$$

$$B = \bar{x}y + c(x \odot y)$$

$$D = x \oplus y \oplus c.$$

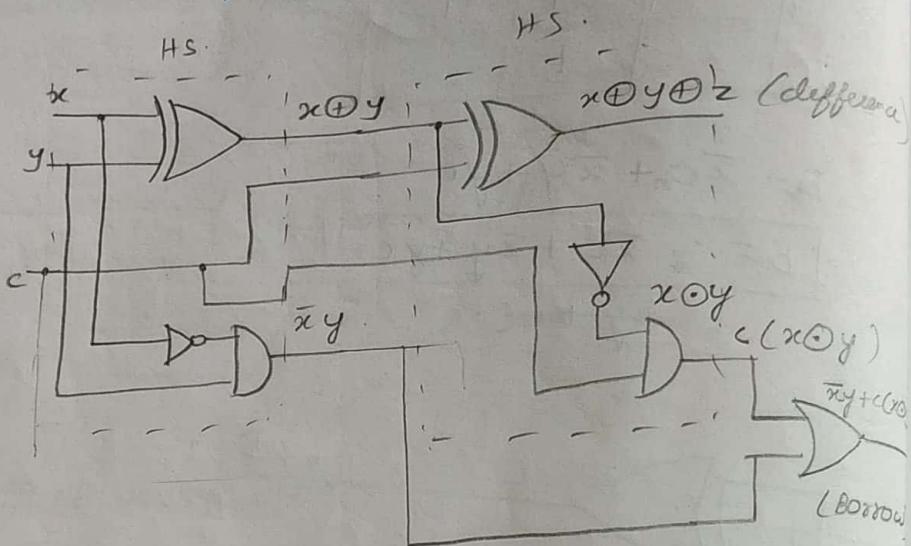

07.08.18

code converters.

1. BCD to Binary
2. BCD to EXCESS-3
3. Binary to Gray
4. Gray to Binary.
5. Binary to BCD.
6. Excess-3 to Binary.

I. BCD


| | BCD | | | | BINARY | | | | |
|----|-------|-------|-------|-------|------------|-------|-------|-------|--|
| | A_3 | A_2 | A_1 | A_0 | B_3 | B_2 | B_1 | B_0 | |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | |
| 2 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | |
| 3 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | |
| 4 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | |
| 5 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | |
| 6 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | |
| 7 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | |
| 8 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | |
| 9 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | |
| 10 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | |
| 11 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | |
| 12 | 1 | 0 | 1 | 0 | Don't care | — | — | — | |
| 13 | 1 | 1 | 0 | 1 | — | — | — | — | |
| 14 | 1 | 1 | 0 | 0 | — | — | — | — | |
| 15 | 1 | 1 | 1 | 0 | — | — | — | — | |

| BCD | A_3 | A_2 | A_1 | A_0 |
|-----|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 0 | 0 |
| 3 | 0 | 0 | 0 | 0 |
| 4 | 0 | 0 | 1 | 1 |
| 5 | 0 | 0 | 1 | 0 |
| 6 | 0 | 0 | 1 | 0 |
| 7 | 0 | 0 | 1 | 1 |
| 8 | 0 | 1 | 0 | 0 |
| 9 | 0 | 1 | 0 | 1 |
| 10 | 0 | 1 | 1 | 0 |
| 11 | 0 | 1 | 1 | 1 |
| 12 | 1 | 0 | 0 | 0 |
| 13 | 1 | 0 | 0 | 1 |
| 14 | 1 | 0 | 1 | 0 |
| 15 | 1 | 0 | 1 | 1 |

| | | | | |
|-------|-------|-------|-------|-------|
| K map | A_3 | A_2 | A_1 | A_0 |
| | 1 | 1 | 1 | 0 |
| | 1 | 1 | 0 | 0 |
| | 1 | 0 | 1 | 1 |
| | 1 | 0 | 0 | 0 |
| | 0 | 1 | 1 | 1 |
| | 0 | 1 | 0 | 0 |
| | 0 | 0 | 1 | 1 |
| | 0 | 0 | 0 | 0 |

| | |
|--------------------------|------|
| $A_3 A_2 A_1 A_0$ | 0000 |
| $\bar{A}_3 \bar{A}_2 00$ | 0 |
| $\bar{A}_3 A_2 01$ | 1 |
| $A_3 A_2 11$ | X |
| $\bar{A}_3 \bar{A}_2 10$ | 0 |

$y \oplus z$ (difference)

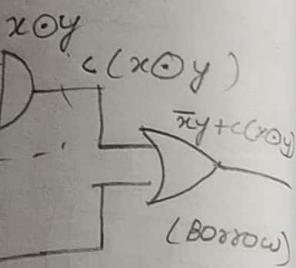

| BCD | | A ₃ A ₂ | | A ₁ A ₀ | |
|-----|---|-------------------------------|---|-------------------------------|---|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |

BINARY

Draw K maps for B₃ B₂ B₁ B₀

For B₃

| A ₃ A ₂ | | A ₁ A ₀ | |
|-------------------------------|----|-------------------------------|----|
| 00 | 00 | 00 | 00 |
| 00 | 00 | 01 | 01 |
| 00 | 01 | 00 | 01 |
| 00 | 01 | 01 | 00 |
| 01 | 00 | 00 | 00 |
| 01 | 00 | 01 | 01 |
| 01 | 01 | 00 | 00 |
| 01 | 01 | 01 | 01 |

A₃ A₂ 11
A₃ A₂ 10

$$B_3 = A_3$$

$$B_2 = A_2$$

$$B_1 = A_1$$

$$B_0 = A_0$$

BCD Excess 3.

| A ₃ A ₂ A ₁ A ₀ | | E ₃ E ₂ E ₁ E ₀ | | | | E ₃ |
|---|------|---|---|---|----|----------------|
| 0 | 0000 | 00 | 1 | 1 | X | X |
| 1 | 0001 | 01 | 0 | 0 | X | X |
| 2 | 0010 | 01 | 0 | 1 | X | X |
| 3 | 0011 | 01 | 1 | 0 | X | X |
| 4 | 0100 | 01 | 1 | 1 | 11 | X |
| 5 | 0101 | 10 | 0 | 0 | 10 | 1 |
| 6 | 0110 | 10 | 0 | 1 | 1 | X |
| 7 | 0111 | 10 | 1 | 0 | X | X |
| 8 | 1000 | 10 | 1 | 1 | X | X |
| 9 | 1001 | 11 | 0 | 0 | X | X |

$$E_3 = A_3 + A_2 A_0 + A_2 A_1$$

$$= A_3 + A_2 (A_0 + A_1)$$

$$(A_1 + \bar{A}_1)_{\text{ex3}} = 03$$

K map for E₂.

| A ₃ A ₂ | | A ₁ A ₀ | | A ₁ A ₀ | | A ₁ A ₀ | |
|----------------------------------|----|-------------------------------|----|-------------------------------|----|-------------------------------|----|
| A ₃ A ₂ 00 | 00 | 00 | 00 | 01 | 11 | 11 | 10 |
| A ₃ A ₂ 01 | 01 | 00 | 01 | 01 | 00 | 01 | 00 |
| A ₃ A ₂ 11 | 11 | 10 | 11 | 11 | 11 | 10 | 11 |
| A ₃ A ₂ 10 | 10 | 11 | 10 | 10 | 11 | 10 | 10 |

$$E_2 = A_3 A_0 + \bar{A}_2 A_1 + \bar{A}_3 \bar{A}_2$$

$$A_0 \bar{A}_2 + A_2 \bar{A}_1 \bar{A}_0$$

K map for E_0

| | | A ₁ A ₀ | |
|-------------------------------|----|-------------------------------|-----------------|
| | | 00 | 01 |
| A ₃ A ₂ | 00 | 1 ₀ | 0 ₁ |
| | 01 | 1 ₄ | 0 ₅ |
| A ₃ A ₂ | 11 | X ₁₂ | X ₁₃ |
| | 10 | 1 ₈ | X ₉ |

$$E_0 = \bar{A}_1\bar{A}_0 + A_1\bar{A}_0$$

$$E_0 = \bar{A}_0(\bar{A}_1 + A_1)$$

K map for E_1

| | | A ₁ A ₀ | |
|-------------------------------|----|-------------------------------|-----------------|
| | | 00 | 01 |
| A ₃ A ₂ | 00 | 1 ₀ | 0 ₁ |
| | 01 | 1 ₄ | 0 ₅ |
| A ₃ A ₂ | 11 | X ₁₂ | X ₁₃ |
| | 10 | 1 ₈ | X ₉ |

$$E_1 = \bar{A}_1\bar{A}_0 + A_1A_0 = A_1 \oplus A_0$$

$$E_3 = A_3 + A_2(\bar{A}_1 + A_1)$$

$$E_2 = \bar{A}_2(A_1 + A_0) + \bar{A}_1\bar{A}_0A_2$$

$$E_1 = \bar{A}_1\bar{A}_0 + A_1A_0$$


$$E_0 = \bar{A}_0(\bar{A}_1 + A_1)$$

LOGIC

A₃



LOGIC DIAGRAM:

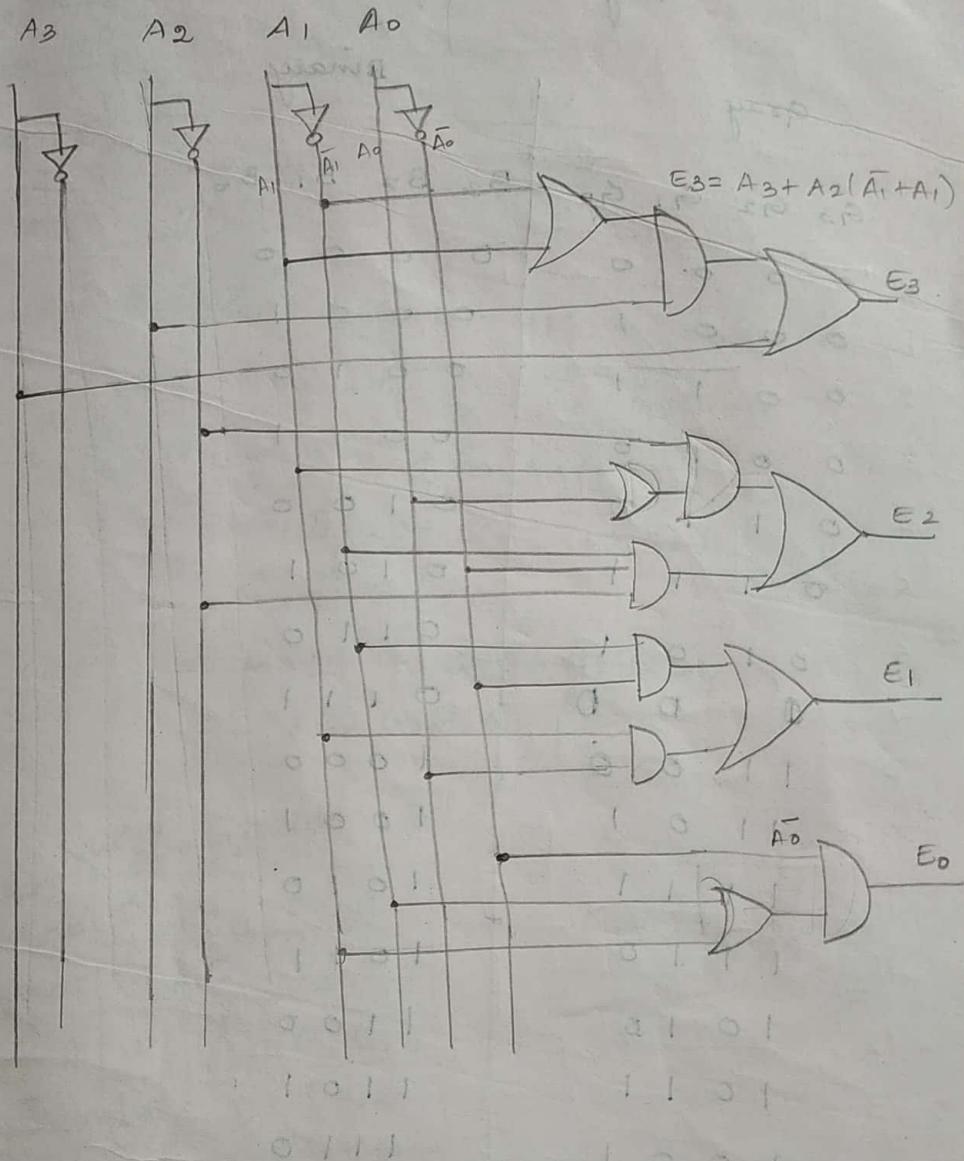

$$E_3 = A_3 + A_2(\bar{A}_1 + A_1)$$

$$E_2 = \bar{A}_2 (A_1 + A_0) + \bar{A}_1 \bar{A}_0 A_2$$

$$E_1 = \bar{A}_1 \bar{A}_0 + A_1 A_0$$

$$E_0 = \bar{A}_0 (\bar{A}_1 + A_1)$$

} Using this logic diagram is easier above

[End - ed]

Deficit Addition

Gray to Binary

Binary

Gray

| | G_3 | G_2 | G_1 | G_0 | B_3 | B_2 | B_1 | B_0 |
|----|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 8 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 9 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 10 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 11 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 12 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| 13 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 14 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 15 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

B_2

| $G_3G_2 \backslash G_1G_0$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 0 | 0 | 0 | 0 |
| 10 | 1 | 1 | 1 | 1 |

$$B_3 = G_3$$

$$B_2 = \bar{G}_3 G_2 + G_3 \bar{G}_2$$

$$B_2 = G_3 \oplus G_2$$

| <u>B_1</u> | $G_3G_2 \backslash G_1G_0$ | $\bar{G}_3G_2 \backslash G_1G_0$ | $\bar{G}_3\bar{G}_2 \backslash G_1G_0$ | $G_3\bar{G}_2 \backslash G_1G_0$ | $\bar{G}_3\bar{G}_2 \backslash G_1G_0$ |
|-------------------------|----------------------------|----------------------------------|--|----------------------------------|--|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 |

$$B_1 = G_1$$

=

($G_3 \oplus G_2$)

=

B_0

| $G_3G_2 \backslash G_1G_0$ | $\bar{G}_3\bar{G}_2 \backslash G_1G_0$ |
|----------------------------|--|
| 00 | 00 |
| 01 | 01 |
| 11 | 11 |
| 10 | 10 |

$$B_0 =$$

= 0

$$= \bar{G}_3 \bar{G}_2$$

$$= (\bar{G}_3 \bar{G}_2)$$

$$= (G_3 G_2)$$

| $\bar{G}_3 \bar{G}_2 \bar{G}_1$ | $G_1 G_2 \bar{G}_0$ | $\bar{G}_1 G_2 G_0$ | $G_1 \bar{G}_2 G_0$ | $G_1 G_2 \bar{G}_0$ |
|---------------------------------|---------------------|---------------------|---------------------|---------------------|
| 0 0 | 1 1 | 0 1 | 1 1 | 0 0 |
| 1 1 | 0 0 | 1 1 | 0 0 | 1 1 |
| 0 0 | 1 1 | 0 0 | 1 1 | 0 0 |
| 1 1 | 0 0 | 1 0 | 0 1 | 1 0 |

$$\begin{aligned}
 B_1 &= G_3 \bar{G}_2 \bar{G}_1 + G_3 G_2 G_1 + \bar{G}_3 \bar{G}_2 G_1 + \bar{G}_3 G_2 \bar{G}_1 \\
 &= G_3 (\bar{G}_2 \bar{G}_1 + G_2 G_1) + \bar{G}_3 (\bar{G}_2 G_1 + G_2 \bar{G}_1) \\
 &= G_3 (G_2 \oplus G_1) + \bar{G}_3 (G_1 \oplus G_2) \\
 &= \bar{G}_3 (G_1 \oplus G_2) + G_3 (\bar{G}_1 \oplus \bar{G}_2) \\
 &= (\bar{G}_3 \oplus G_1 \oplus G_2) \\
 &= G_3 \oplus G_1 \oplus G_2 \\
 &= G_3 \oplus G_2 \oplus G_1
 \end{aligned}$$

| $G_3 G_2 \bar{G}_1$ | $G_1 G_2 \bar{G}_0$ | $\bar{G}_1 G_2 G_0$ | $G_1 \bar{G}_2 G_0$ | $G_1 G_2 \bar{G}_0$ |
|---------------------|---------------------|---------------------|---------------------|---------------------|
| 0 0 | 1 1 | 0 0 | 1 1 | 0 0 |
| 1 1 | 0 0 | 1 1 | 0 0 | 1 1 |
| 0 0 | 1 1 | 0 0 | 1 1 | 0 0 |
| 1 1 | 0 0 | 1 0 | 0 1 | 1 0 |

$$\begin{aligned}
 B_0 &= \bar{G}_3 \bar{G}_2 \bar{G}_1 G_0 + \bar{G}_3 \bar{G}_2 G_1 \bar{G}_0 + \\
 &\quad \bar{G}_3 G_2 \bar{G}_1 \bar{G}_0 + \bar{G}_3 G_2 G_1 G_0 + \\
 &\quad G_3 G_2 \bar{G}_1 G_0 + G_3 G_2 G_1 \bar{G}_0 + \\
 &\quad G_3 \bar{G}_2 \bar{G}_1 \bar{G}_0 + G_3 \bar{G}_2 G_1 G_0 \\
 &= \bar{G}_3 \bar{G}_2 (\bar{G}_1 G_0 + G_1 \bar{G}_0) + \bar{G}_3 G_2 (\bar{G}_1 \bar{G}_0 + G_1 G_0) + \\
 &\quad G_3 G_2 (\bar{G}_1 G_0 + G_1 \bar{G}_0) + G_3 \bar{G}_2 (\bar{G}_1 \bar{G}_0 + G_1 G_0) \\
 &= \bar{G}_3 \bar{G}_2 (G_1 \oplus G_0) + \bar{G}_3 G_2 (G_1 \odot G_0) + G_3 G_2 (G_1 \oplus G_0) \\
 &\quad + G_3 \bar{G}_2 (G_1 \odot G_0) \\
 &= (\bar{G}_3 \bar{G}_2 + G_3 G_2)(G_1 \oplus G_0) + (\bar{G}_3 G_2 + \bar{G}_2 G_3)(G_1 \odot G_0) \\
 &= (G_3 \odot G_2)(G_1 \oplus G_0) + G_3 G_2 (G_3 \oplus G_2)(G_1 \odot G_0)
 \end{aligned}$$

$$\begin{aligned}
 &= (G_3 \odot G_2)(G_1 \oplus G_0) + (\overline{G_3 \oplus G_2}) \overline{(G_1 \odot G_0)} \\
 &= (G_3 \odot G_2)(G_1 \oplus G_2) + (\overline{G_3 \odot G_2})(\overline{G_1 \oplus G_0}) \\
 &= \cancel{G_3 \odot G_2 \odot G_1} \\
 &= (G_3 \odot G_2)(G_1 \oplus G_0) + (\overline{G_3 \odot G_2})(\overline{G_0 \oplus G_1})
 \end{aligned}$$


$$(G_3 \odot G_2) \odot G_1 \oplus G_0$$

$$= (\overline{G_3 \oplus G_2})(G_1 \oplus G_0) + (\overline{G_0 \oplus G_1})(G_2 \oplus G_3)$$

$$= G_3 \oplus G_2 \oplus G_1 \oplus G_0$$

$$B_0 = G_0 \oplus B_1 \oplus G_1$$

Design:-

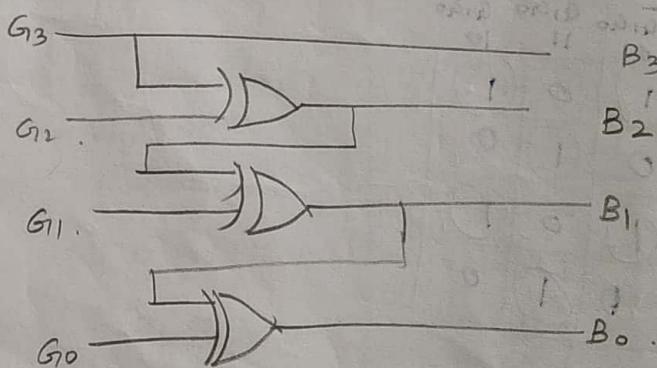

Excess - 3

Excess 3 to Binary

Binary.

| E_3 | E_2 | E_1 | E_0 | B_3 | B_2 | B_1 | B_0 |
|-------------|-------|-------|-------|-------|-------|-------|-------|
| | | | | 0 | 0 | 0 | 0 |
| | | | | 0 | 0 | 0 | 1 |
| | | | | 0 | 0 | 1 | 0 |
| | | | | 0 | 0 | 1 | 1 |
| | | | | 0 | 1 | 0 | 0 |
| | | | | 0 | 1 | 0 | 1 |
| | | | | 0 | 1 | 1 | 0 |
| | | | | 0 | 1 | 1 | 1 |
| | | | | 1 | 0 | 0 | 0 |
| | | | | 1 | 0 | 0 | 1 |
| | | | | 1 | 0 | 1 | 0 |
| | | | | 1 | 0 | 1 | 1 |
| | | | | 1 | 1 | 0 | 0 |
| | | | | 1 | 1 | 0 | 1 |
| | | | | 1 | 1 | 1 | 0 |
| | | | | 1 | 1 | 1 | 1 |
| Don't cares | | | | X | | | |
| Don't cares | | | | X | | | |
| Don't cares | | | | X | | | |

$$1011 = 0A1A2A4A = A$$

$$1001 = 0A1B2B4B = B$$

at previous steps all needed parts exist
need to numbering with 0 suffix

10.8.18

Binary parallel Adder.

Half adder - 2 bits of each input

Full adder - 3 bits

1. Ripple carry Adder (carry propagate Adder)


2. carry look ahead adder.

1. Ripple carry Adder :

(made of full adders)

If n bits are required, the n -number of full adders are required.

4-bit RCA.

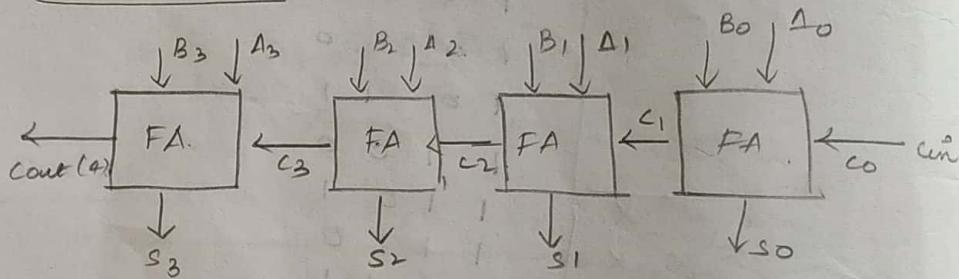

$$A = A_3 A_2 A_1 A_0 = 1101$$

$$B = B_3 B_2 B_1 B_0 = 1001$$

Initially 2/p carry is zero.

$$A = A_3 A_2 \text{ (A1)} A_0$$

$$B = B_3 B_2 \text{ (B1)} B_0$$

$$\underline{S_3 \quad S_2 \quad S_1 \quad S_0}$$


C_4

cout

3 inputs are added

∴ full adders are used

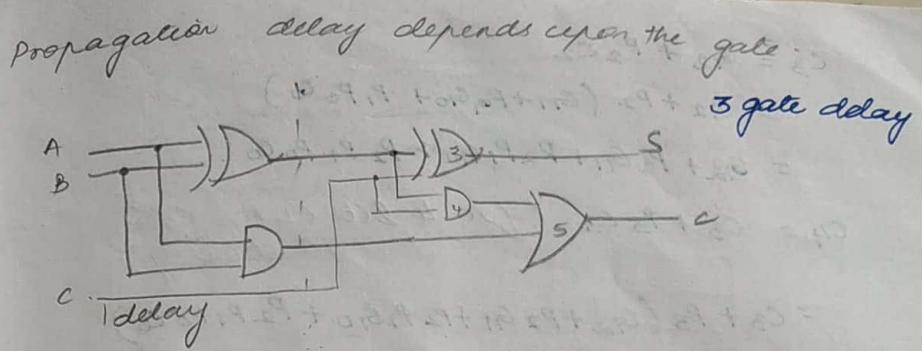Propagation delay: (Generally in nano second)
Time Delay between the input arrivals to the gate & the generation of carry.




In full adder $\rightarrow 2$ gate delay. (in general)

disadvantage:
longer propagation delay.

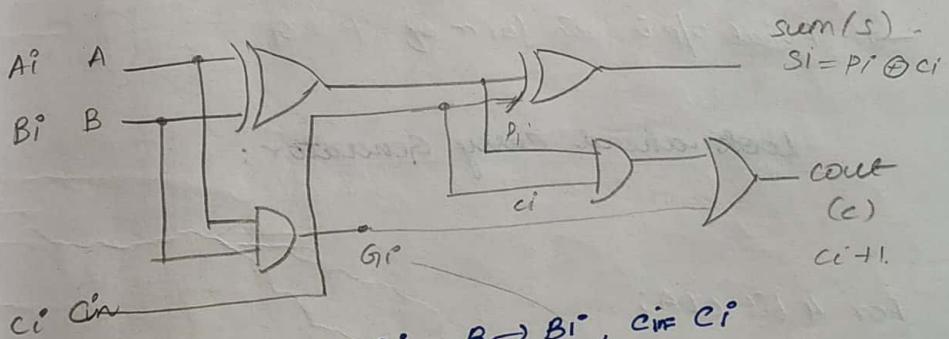2. carry look ahead adder: (high speed parallel adder)
All the carry are generated simultaneously.

We modify based on full adder
[consider it as single bit]



Assume $A \rightarrow A_i$, $B \rightarrow B_i$, $C_i = c_i$

$p_i \rightarrow$ Propagate function $= A_i \oplus B_i$ (for i/p)
 $g_i \rightarrow$ Generate function $= A_i B_i$. (And combination of inputs)

$$c_{i+1} = g_i + p_i c_i$$

apply $i=0$
 $\rightarrow c_1 = g_0 + p_0 c_0$, where $c_0 \rightarrow$ input carry

when $i=2$

$$\rightarrow c_2 = g_1 + p_1 c_1$$

sub c_1 in c_2

$$\begin{aligned} \rightarrow g_2 &= g_1 + p_1 (g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$

$$C_3 = G_2 + P_2 C_2$$

$$= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0.$$

$$C_4 = C_3 + P_3 C_3 \quad (\text{for 4 bit CLA, } C_4 \text{ is the final carry})$$

$$= C_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0)$$

$$= C_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

$$C_n = G_{n-1} + P_{n-1} G_{n-2} + P_{n-1} P_{n-2} G_{n-3} + \dots$$


$$\dots + (P_{n-1} P_{n-2} \dots P_1 P_0 C_0)$$

For 8 bit CLA:

$$\begin{aligned} \text{Cout} = C_7 = & G_7 + P_7 G_6 + P_7 P_6 G_5 + P_7 P_6 P_5 G_4 + \\ & P_7 P_6 P_5 P_4 G_3 + P_7 P_6 P_5 P_4 P_3 G_2 + \\ & P_7 P_6 P_5 P_4 P_3 P_2 G_1 + P_7 P_6 P_5 P_4 P_3 P_2 P_1 G_0 + \\ & P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0 C_0 \quad \text{input carry} \end{aligned}$$

→ Final O/P is in form of P & G

Look ahead carry Generator:

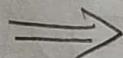

For 4 bit CLA;

we get 4 gate delay (fixed)



from i/p to output sum.

(Very high speed parallel adder)

to generate $G_1, P \rightarrow 1 \text{ gate}$

to generate sum = 1 gate.

Look ahead carry generator

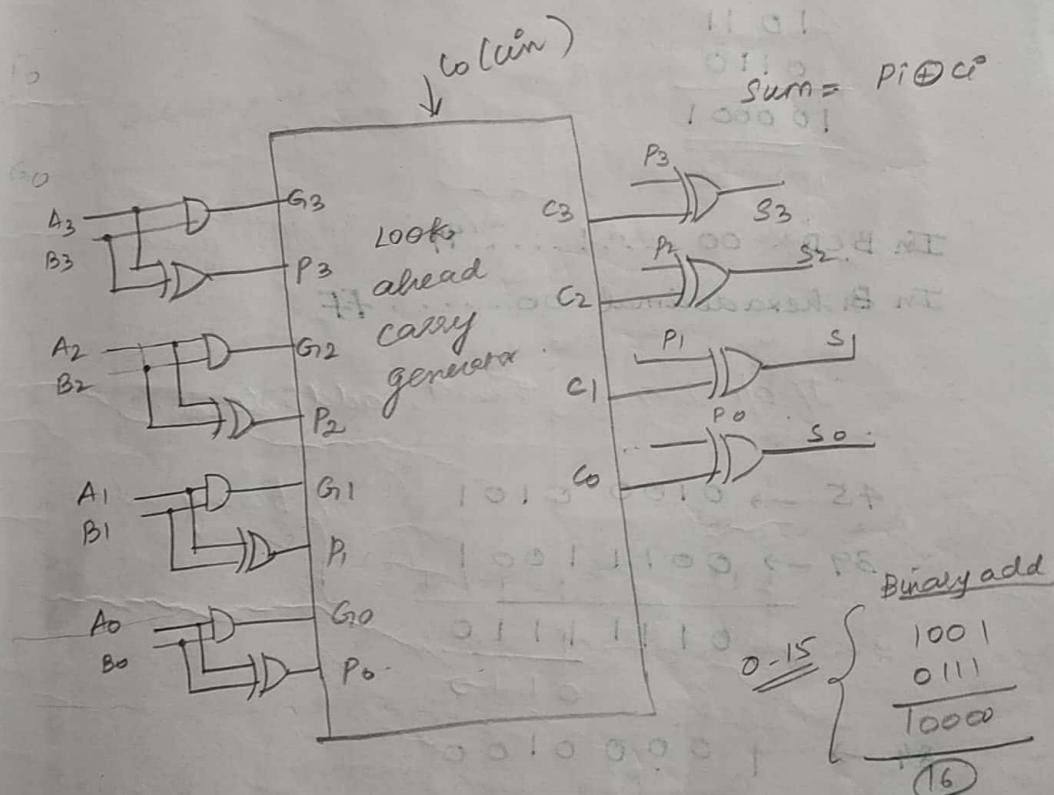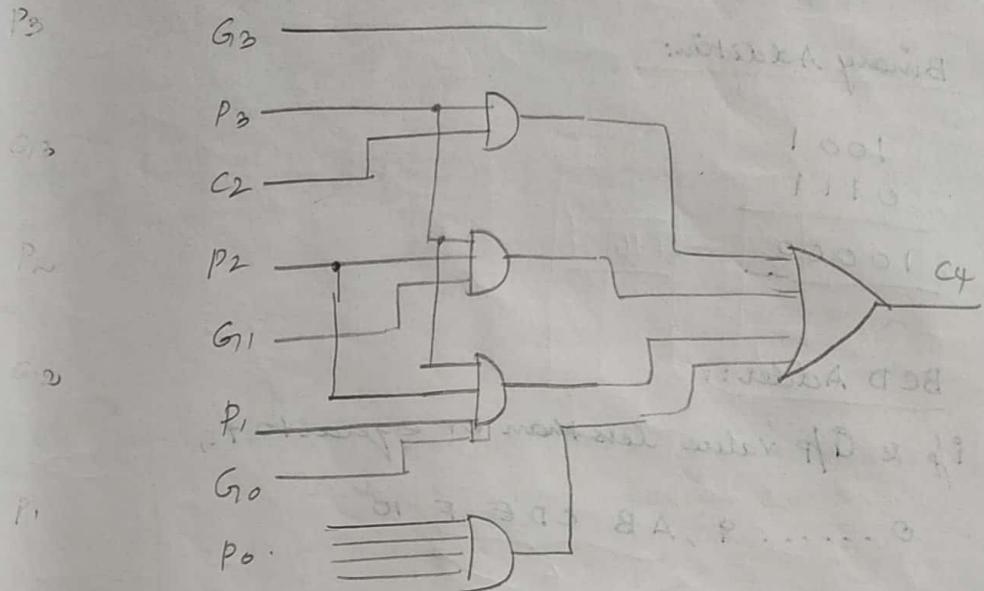

BCD addition

0 to 9
From 10 it repeats.


BCD Adder. (4 bit)

Binary Addition:

$$\begin{array}{r}
 1001 \\
 0111 \\
 \hline
 10000
 \end{array} \rightarrow \boxed{16}$$

BCD Adder:

i/p & o/p value less than or equal to 9.

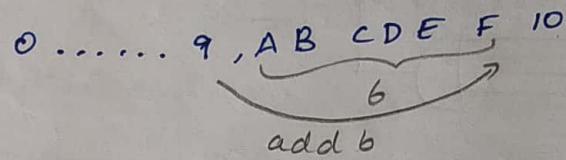

$$\begin{array}{r}
 1011 \\
 0110 \\
 \hline
 100001
 \end{array}$$

In BCD 00.....99 highest value
In Bi hexadecimal 00....FF

If o/p is greater than 9, add 6 do it.

$$45 \rightarrow 0100\ 0101$$


$$39 \rightarrow 0011\ 1001$$

} binary addition

$$\begin{array}{r}
 0111\ 1110 \\
 \hline
 0110
 \end{array}$$

$$84 \rightarrow \underline{1.0000100}$$

0
1
2
3
4
5
6
7
8
9
10
11
12
13
14
15

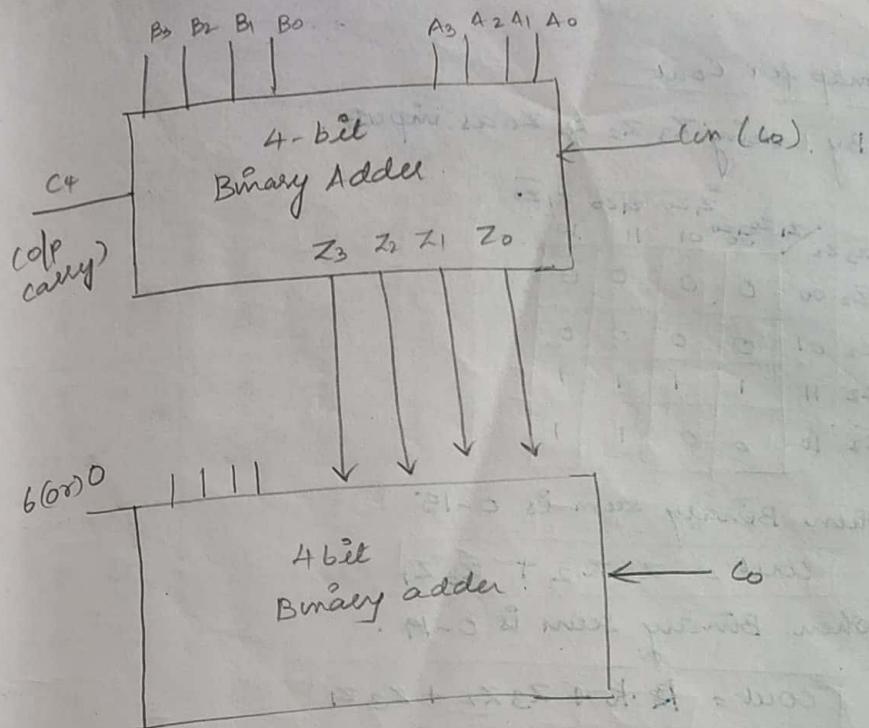

| DECIMAL | Binary sum | | | | | BCD sum. | | | | |
|---------|------------|-------|-------|-------|-------|----------|-------|-------|-------|-------|
| | K | Z_3 | Z_2 | Z_1 | Z_0 | Cout | S_3 | S_2 | S_1 | S_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 4 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 5 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 6 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 7 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 8 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 9 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 10 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 11 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 12 | 0 | 1 | 1 | 0 | 0 | 1 | | | | |
| 13 | 0 | 1 | 1 | 0 | 1 | 1 | | | | |
| 14 | 0 | 1 | 1 | 1 | 0 | 1 | | | | |
| 15 | 0 | 1 | 1 | 1 | 1 | 1 | | | | |
| . | | | | | | | | | | |
| 19. | | | | | | | | | | |

K map for Cout

By taking $Z_3 Z_2 Z_1 Z_0$ as inputs.


| $Z_3 Z_2$ | $Z_1 Z_0$ | $\bar{Z}_1 \bar{Z}_0$ | $Z_1 Z_0$ | $\bar{Z}_1 \bar{Z}_0$ |
|--------------------------|-----------|-----------------------|-----------|-----------------------|
| $\bar{Z}_3 \bar{Z}_2 00$ | 0 0 | 0 0 | 0 0 | 0 0 |
| $\bar{Z}_3 Z_2 01$ | 0 0 | 0 0 | 0 0 | 0 0 |
| $Z_3 Z_2 11$ | 1 1 | 1 1 | 1 1 | 1 1 |
| $Z_3 \bar{Z}_2 10$ | 0 0 | 1 1 | 1 1 | 1 1 |

When Binary sum is 0-15

$$Cout = Z_3 Z_2 + Z_3 Z_1$$

When Binary sum is 0-19.
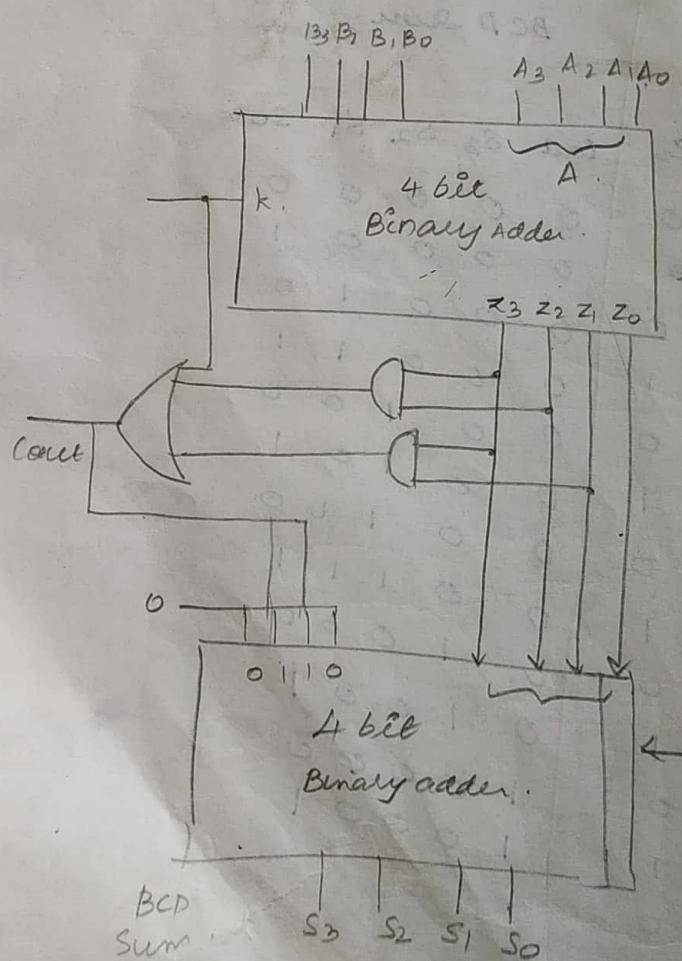
$$Cout = \bar{Z}_3 \cdot k + Z_3 Z_2 + Z_3 Z_1$$



18

IR

A

A_1, A_0

0 0

0 0

0 0

0 1

0 1

0 1

0 1

1 0

1 0

1 0

1 0

1 0

1 0

K map

(B)

B_1, B_0

A_1, A_0

$\bar{A}_1, \bar{A}_0 00$

$\bar{A}_1, A_0 01$

$A_1, A_0 11$

$A_1 \bar{A}_0 10$

1.10.18

Magnitude comparator

| Inputs | | Outputs | | |
|------------|------------|---------|---------|---------|
| A | B | $A > B$ | $A = B$ | $A < B$ |
| A_1, A_0 | B_1, B_0 | | | |
| 0 0 | 0 0 | 0 | 1 | 0 0 |
| 0 0 | 0 1 | 0 | 0 | 1 1 |
| 0 0 | 1 0 | 0 | 0 | 1 2 |
| 0 0 | 1 1 | 0 | 0 | 1 3 |
| 0 1 | 0 0 | 1 | 0 | 0 4 |
| 0 1 | 0 1 | 0 | 1 | 0 5 |
| 0 1 | 1 0 | 0 | 0 | 1 6 |
| 0 1 | 1 1 | 0 | 0 | 1 7 |
| 1 0 | 0 0 | 0 | 0 | 0 8 |
| 1 0 | 0 1 | 0 | 0 | 0 9 |
| 1 0 | 1 0 | 0 | 0 | 0 10 |
| 1 0 | 1 1 | 0 | 0 | 1 11 |
| 1 1 | 0 0 | 1 | 0 | 0 12 |
| 1 1 | 0 1 | 1 | 0 | 0 13 |
| 1 1 | 1 0 | 1 | 0 | 0 14 |
| 1 1 | 1 1 | 0 | 1 | 0 15 |

K map

| | | A > B | | | |
|-----------------------|----|-----------------------|-----------------|-----------------|-----------|
| | | $\bar{B}_1 \bar{B}_0$ | $\bar{B}_1 B_0$ | $B_1 \bar{B}_0$ | $B_1 B_0$ |
| | | 00 | 01 | 11 | 10 |
| $\bar{A}_1 \bar{A}_0$ | 00 | 0 | 0 | 0 | 0 |
| $\bar{A}_1 \bar{A}_0$ | 01 | 1 | 0 | 0 | 0 |
| $\bar{A}_1 \bar{A}_0$ | 11 | 0 | 1 | 0 | 1 |
| $\bar{A}_1 \bar{A}_0$ | 10 | 1 | 1 | 0 | 0 |

A > B

$$= A_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_0 + A_1 \bar{B}_1$$

(ii) $A = B$
 $A = B$

| | | B ₁ B ₀ | 00 | 01 | 11 | 10 |
|--|--|-------------------------------|----|----|----|----|
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |

(iii) $A < B$

| | | B ₁ B ₀ |
|--|--|-------------------------------|-------------------------------|-------------------------------|-------------------------------|-------------------------------|
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |
| | | A ₁ A ₀ | 00 | 01 | 11 | 10 |

$$\boxed{A=B} = \overline{A_1 A_0} \overline{B_1 B_0} + \overline{A_1 A_0} \overline{B_1} B_0 + A_1 A_0 B_1 B_0 + A_1 \overline{A_0} \overline{B_1} \overline{B_0}$$

$$\boxed{A < B} = \overline{A_1} B_1 + \overline{A_1} \overline{A_0} B_0 + \overline{A_0} B_1 B_0$$

case(i) : $\boxed{A > B}$

$$\begin{aligned}
 A > B &= A_1 \overline{B_1} + A_0 \overline{B_1} \overline{B_0} + A_1 A_0 \overline{B_0} \\
 &= A_1 \overline{B_1} + (A_1 + \overline{A_1}) A_0 \overline{B_1} \overline{B_0} + A_1 A_0 (B_1 + \overline{B_1}) \overline{B_0} \\
 &= A_1 \overline{B_1} + A_1 A_0 \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} \overline{B_0} + \\
 &\quad A_1 A_0 B_1 \overline{B_0} + \cancel{A_1 A_0 \overline{B_1} \overline{B_0}} \\
 &= A_1 \overline{B_1} + A_1 A_0 \overline{B_1} \overline{B_0} + A_0 \overline{B_0} (\overline{A_1} \overline{B_1} + A_1 B_1) \\
 &= \underbrace{A_1 \overline{B_1} + A_1 A_0 \overline{B_1} \overline{B_0}}_{\text{use adsorption law.}} + (A_1 \odot B_1) A_0 \overline{B_0} \\
 &= A_1 \overline{B_1} (1 + A_0 \overline{B_0}) + (A_1 \odot B_1) A_0 \overline{B_0} \\
 \boxed{A > B} &= A_1 \overline{B_1} + (A_1 \odot B_1) A_0 \overline{B_0}
 \end{aligned}$$

From (i), (ii) and (iii) cases:-

$$(A = B) = x_1 x_0 \quad \begin{pmatrix} 1 \\ 1 \\ 0 \\ 1 \end{pmatrix}$$

$$(A > B) = A_1 \overline{B_1} + x_1 A_0 \overline{B_0}$$

$$(A < B) = \overline{A_1} B_1 + x_1 \overline{A_0} B_0$$

case (iii)

A < B

case

while

case (ii) : $A \neq B$

$$\begin{aligned}
 A \neq B &= \overline{A_1} B_1 + \overline{A_1} \overline{A_0} B_0 (B_1 + \overline{B_1}) + \overline{A_0} B_1 B_0 (A_1 + \overline{A_1}) \\
 &= \overline{A_1} B_1 + \overline{\overline{A_1} \overline{A_0} B_0} \overline{B_1} + \overline{\overline{A_1} \overline{A_0} \overline{B_1}} B_0 + \overline{A_1} \overline{\overline{A_0} B_1} B_0 \\
 &\quad + \overline{\overline{A_1} \overline{A_0} B_1} B_0 \\
 &= \overline{A_1} B_1 (1 + \overline{A_0} B_0) + \overline{A_0} B_0 (\overline{A_1} \overline{B_1} + A_1 B_1) \\
 &= \overline{A_1} B_1 + \overline{A_0} B_0 \underbrace{(A_1 \odot B_1)}_{x_1} = \overline{A_1} B_1 + \overline{A_0} B_0 x_1
 \end{aligned}$$

case (ii) $A = B$:-

$$= \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 A_0 B_1 B_0 + A_1 \overline{A_0} \overline{B_1}$$

$$\begin{aligned}
 &= \overline{A_1} \overline{B_1} (\overline{A_0} B_0 + A_0 B_0) + A_1 B_1 (A_0 B_0 + \overline{A_0} \overline{B_0}) \\
 &= \overline{A_1} \overline{B_1} (A_0 \odot B_0) + A_1 B_1 (A_0 \odot B_0) \\
 &= (A_0 \odot B_0) (\overline{A_1} \overline{B_1} + A_1 B_1) \\
 &= (A_0 \odot B_0) (A_1 \odot B_1) \\
 &= x_0 x_1 + x_1 x_0
 \end{aligned}$$

Let $x_1 = A_1 \odot B_1$ } $\rightarrow \textcircled{1}$
 $x_0 = A_0 \odot B_0$

similarly $x_1 = A_1 \odot B_1$

While comparing :

LHS \rightarrow RHS

left to Right.

e.g.: $x > y$

$$x = 5 \underline{3} 4 \underline{3} 2 1 7 8$$

$$y = 5 3 4 \underline{2} 1 7 8 7$$

4-bit

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

$$\begin{array}{r} 1101 \\ 1101 \end{array}$$

$$(A > B) = A_3 \bar{B}_3 + X_3 A_2 \bar{B}_2 + X_3 X_2 A_1 \bar{B}_1 + X_3 X_2 X_1 A_0 B_0$$

$$(A < B) = \bar{A}_3 B_3 + X_3 \bar{A}_2 B_2 + X_3 X_2 \bar{A}_1 B_1 + X_3 X_2 X_1 \bar{A}_0 B_0$$

$$(A = B) = X_3 X_2 X_1 X_0$$

21.08.18.

Q. Design a combinational circuit with 3 inputs and 1 output. The output is 1, ~~when~~ when the binary value of input is less than 3. The output is 0 otherwise.



$\Rightarrow x \ y \ z \text{ O/P}$ 2³ \rightarrow 8 combination
Full adder

| | | | | |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 0 |

| \bar{x} | yz | $\bar{y}\bar{z}$ | $\bar{y}z$ | $y\bar{z}$ | yz |
|-----------|------|------------------|------------|------------|------|
| x | 00 | 01 | 11 | 10 | 01 |
| x | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 2 | 1 | 0 | 1 | 0 | 0 |
| 3 | 1 | 1 | 0 | 0 | 0 |
| 4 | 0 | 0 | 0 | 0 | 0 |
| 5 | 0 | 1 | 0 | 0 | 0 |
| 6 | 1 | 0 | 0 | 0 | 0 |
| 7 | 1 | 1 | 1 | 0 | 0 |

$$= \bar{x} \bar{y} + \bar{x} \bar{z}$$

$$= \bar{x} (\bar{y} + \bar{z})$$

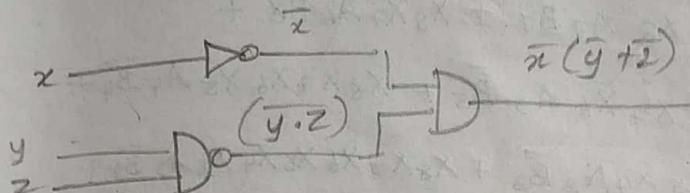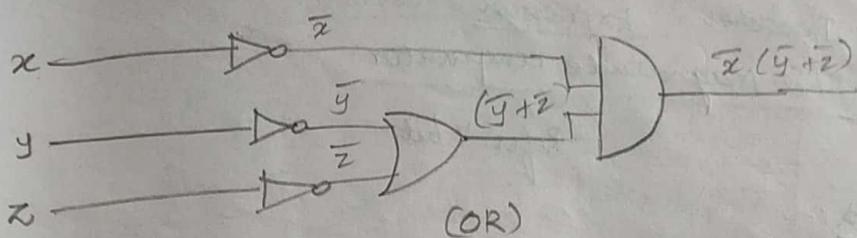


2.Q) Design a combinational circuit with 3 i/p and 1 output. The output is 1 when the binary value of i/p is even no & otherwise 0.

| | x | y | z | O/P |
|---|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 0 |

| x | y | z | $y\bar{z}$ | $\bar{y}\bar{z}$ | $\bar{y}z$ | yz | $y\bar{z}$ | $\bar{y}\bar{z}$ |
|-----------|-----|-----|------------|------------------|------------|------|------------|------------------|
| \bar{x} | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| x | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |

$$= \bar{z}$$

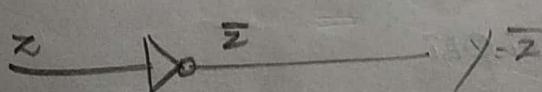

28.08.18

Decoder. Expression
8bit Magnitude comparator:
Refer 4 bit:-

 $\Rightarrow \underline{A \geq B} :-$

$$\begin{aligned}
 &= A_8 \bar{B}_8 + X_8 A_7 \bar{B}_7 + X_8 X_7 A_6 \bar{B}_6 + \\
 &\quad X_8 X_7 X_6 A_5 \bar{B}_5 + X_8 X_7 X_6 X_5 A_4 \bar{B}_4 + \\
 &\quad X_8 X_7 X_6 X_5 X_4 A_3 \bar{B}_3 + X_8 X_7 X_6 X_5 X_4 X_3 A_2 \bar{B}_2 + \\
 &\quad X_8 X_7 X_6 X_5 X_4 X_3 X_2 A_1 \bar{B}_1 + X_8 X_7 X_6 X_5 X_4 X_3 X_2 X_1
 \end{aligned}$$

 $\Rightarrow \cancel{\underline{A \leq B}}$

$$\begin{aligned}
 &= A_7 \bar{B}_7 + X_7 A_6 \bar{B}_6 + X_7 X_6 A_5 \bar{B}_5 + \\
 &\quad X_7 X_6 X_5 A_4 \bar{B}_4 + X_7 X_6 X_5 X_4 A_3 \bar{B}_3 + \\
 &\quad X_7 X_6 X_5 X_4 X_3 A_2 \bar{B}_2 + X_7 X_6 X_5 X_4 X_3 X_2 A_1 \bar{B}_1 + \\
 &\quad X_7 X_6 X_5 X_4 X_3 X_2 X_1 A_0 \bar{B}_0
 \end{aligned}$$

 $\Rightarrow \underline{A < B}$

$$\begin{aligned}
 &= \bar{A}_7 B_7 + X_7 \bar{A}_6 B_6 + X_7 X_6 \bar{A}_5 B_5 + \\
 &\quad X_7 X_6 X_5 \bar{A}_4 B_4 + X_7 X_6 X_5 X_4 \bar{A}_3 B_3 + \\
 &\quad X_7 X_6 X_5 X_4 X_3 \bar{A}_2 B_2 + X_7 X_6 X_5 X_4 X_3 X_2 \bar{A}_1 B_1 + \\
 &\quad X_7 X_6 X_5 X_4 X_3 X_2 X_1 \bar{A}_0 B_0
 \end{aligned}$$

 $\Rightarrow \underline{A = B}$

$$X_7 X_6 X_5 X_4 X_3 X_2 X_1 X_0$$

$$X_C = A_C \oplus B_C$$

Accept
Mostly

2 to

A

B

E

T

I/P


0 0

0 1

1 0

1 1

DECODER

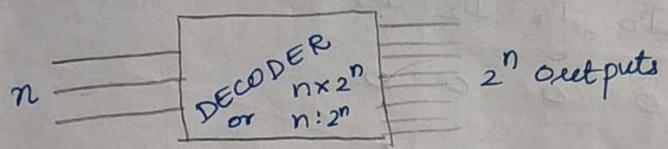

$$\begin{array}{ll} n & 2^n \\ 2 & 2^2 = 4 \\ 3 & 2^3 = 8 \\ 4 & 2^4 = 16 \end{array}$$

example:-

$$2 : 4$$

$$3 : 8$$


$$4 : 16$$

input output

Accepts n inputs and gives 2^n outputs.
Mostly we USE AND gates.

if 4 outputs are required,
we use 4 AND gates.

2 to 4 Decoder:

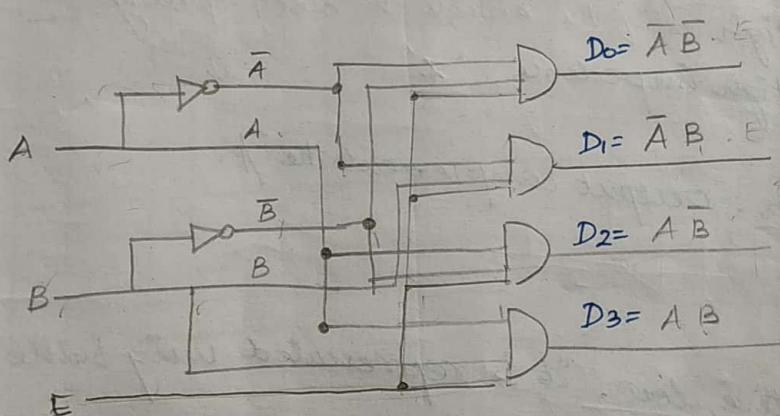

Truth table

| i/p | D ₀ | D ₁ | D ₂ | D ₃ |
|-----|----------------|----------------|----------------|----------------|
| 0 0 | 1 | 0 | 0 | 0 |
| 0 1 | 0 | 1 | 0 | 0 |
| 1 0 | 0 | 0 | 1 | 0 |
| 1 1 | 0 | 0 | 0 | 1 |

[Decoder generates 1 in one of the bits]

Use :-

Interconnecting
peripherals
between i/p and
processor

(At the time any 1 of
the o/p generates 1)

$E \rightarrow$ enable


| E | A | B | D ₀ | D ₁ | D ₂ | D ₃ |
|---|---|---|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

E is the extra bit given to i/p


The above concept represents
TRISTATE device.

1. Low \rightarrow If enable is properly given 0
2. High \rightarrow If the enable is not properly 1
3. High impedance. Z given

Inverter: output complements the i/p.

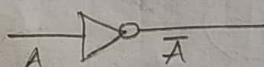

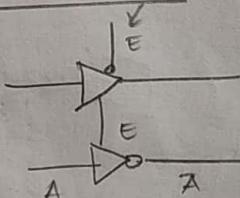If active low, it is represented using bubble.



3 to 8 is widely used. 74LS138

3 to

i/p


| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

A



3 to 8 decoder without Enable

| i/p | o/p | | | | | | | | | |
|-----|-----|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A | B | C | D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

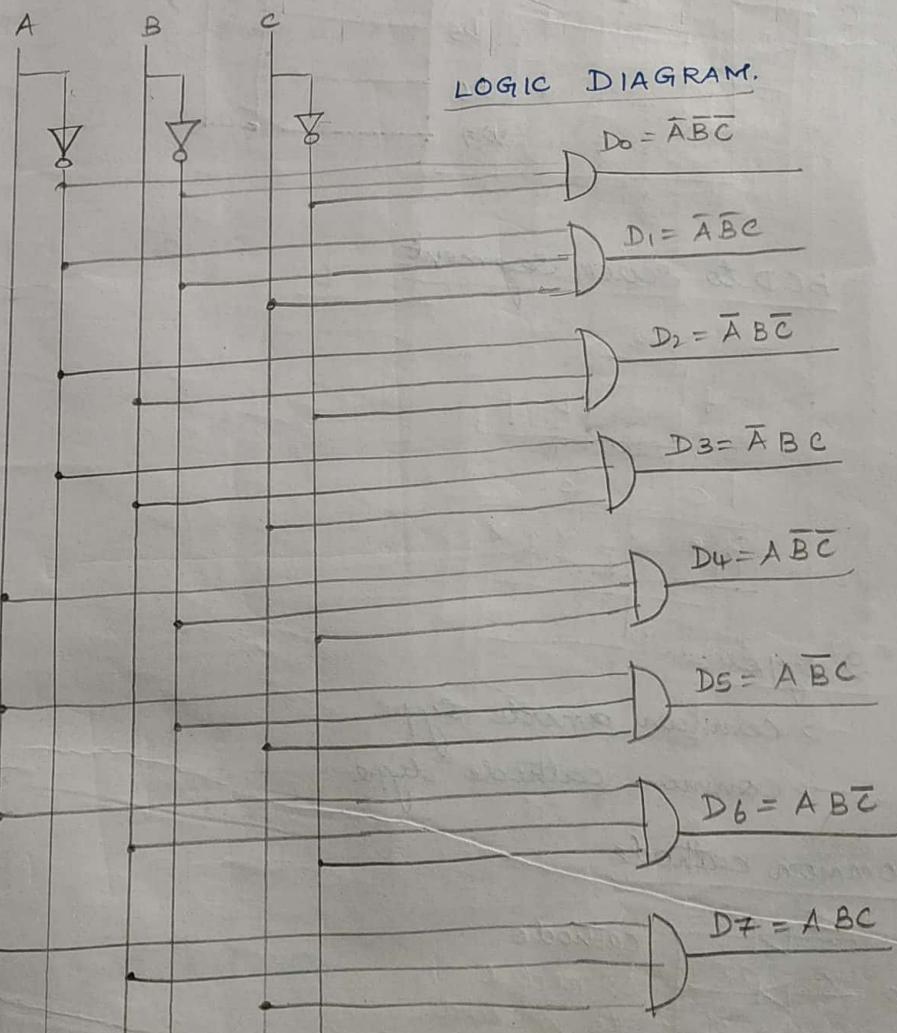


An example of Decoder is
BCD to decimal.


Full adder using Decoder.

$$\text{Sum} = \sum (1, 2, 4, 7)$$

$$\text{Cout} = \sum (3, 5, 6, 7)$$

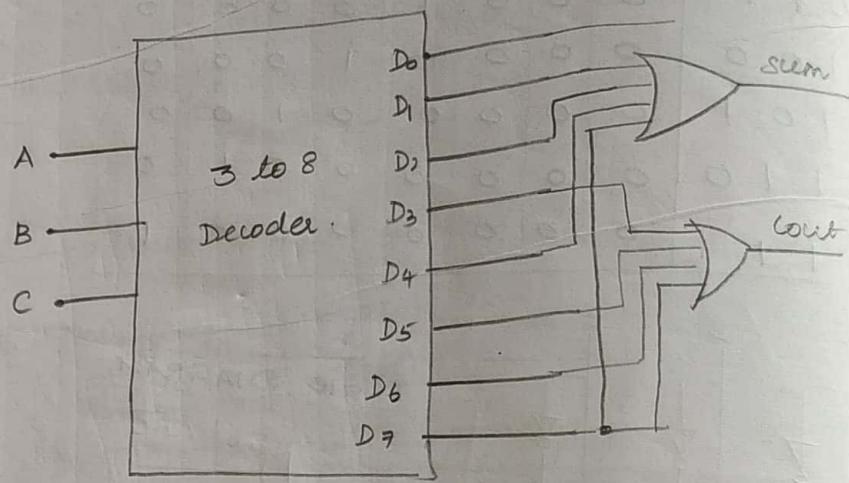


BCD to Seven segment

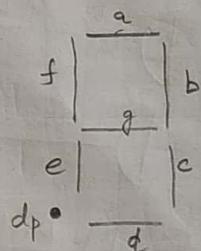


2 types :-

- common anode type
- common cathode type

* Common cathode

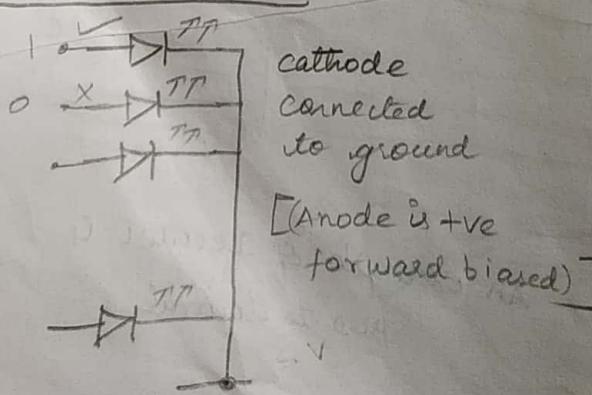

* common anode type:

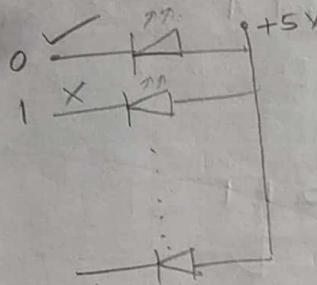

Q) HW How will you design 7-segment display

31.08.18

Digit to ASA + IAA - abcde

DIGIT A₃ A₂ A₁ A₀ a b c d e f g

0 0 0 0 1 1 1 1 1 1 0

0 0 0 1 0 1 1 0 0 0 0

0 0 1 0 1 1 0 1 1 0 1

0 0 1 1 1 1 1 1 0 0 1

0 1 0 0 0 1 1 0 0 1 1

0 1 0 1 1 0 1 1 0 1 1

0 1 1 0 1 0 1 1 1 1 1

0 1 1 1 1 1 1 0 0 0 0

Digit $A_3 A_2 A_1 A_0$ $a b c d e f g$
 $\begin{array}{c} \boxed{} \\ \boxed{} \\ \boxed{} \end{array}$ $\begin{array}{ccccccc} 1 & 0 & 0 & 0 & 1 & 1 & 1 \end{array}$

$\begin{array}{c} \boxed{} \\ \boxed{} \\ \boxed{} \end{array}$ $\begin{array}{ccccccc} 1 & 0 & 0 & 1 & 1 & 1 & 0 \end{array}$

Kmap for a :

| | | $A_1 A_0$ | $\bar{A}_1 \bar{A}_0$ | $\bar{A}_1 A_0$ | $A_1 \bar{A}_0$ | $A_1 A_0$ |
|-----------|----|-----------|-----------------------|-----------------|-----------------|-----------|
| | | 00 | 01 | 11 | 10 | |
| $A_3 A_2$ | 00 | 1 | 0 | 1 | 1 | |
| | 01 | 0 | 1 | 1 | 1 | |
| $A_3 A_2$ | 11 | X | X | X | X | |
| | 10 | 1 | 1 | X | X | |

$$a = A_3 + A_1 + A_2 A_0 +$$

$$A_3 \bar{A}_0$$

For b :

| | | $A_1 \bar{A}_0$ | $\bar{A}_1 \bar{A}_0$ | $\bar{A}_1 A_0$ | $A_1 \bar{A}_0$ | $A_1 A_0$ |
|-----------|----|-----------------|-----------------------|-----------------|-----------------|-----------|
| | | 00 | 01 | 11 | 10 | |
| $A_3 A_2$ | 00 | 1 | 1 | 1 | 1 | |
| | 01 | 1 | 0 | 1 | 0 | |
| $A_3 A_2$ | 11 | X | X | X | X | |
| | 10 | 1 | 1 | X | X | |

$$b = A_3 + \bar{A}_2 +$$

$$\bar{A}_1 \bar{A}_0 + A_1 A_0$$

For c :

$$A_3 A_2 / A_1$$

$$A_3 A_2 00$$

$$\bar{A}_3 A_2 01$$

$$A_3 A_2 11$$

$$A_3 \bar{A}_2 10$$

c =

| | $A_1 A_0$ | $\bar{A}_1 \bar{A}_0$ | $\bar{A}_1 A_0$ | $A_1 \bar{A}_0$ | $A_1 \bar{A}_0$ |
|--------------------------|-----------|-----------------------|-----------------|-----------------|-----------------|
| $A_3 A_2$ | 1 | 0 | 1 | 1 | 0 |
| $\bar{A}_3 \bar{A}_2 00$ | 0 | 0 | 1 | 1 | 10 |
| $\bar{A}_3 A_2 01$ | 1 | 0 | 1 | 1 | 6 |
| $A_3 A_2 11$ | X | X | X | X | X |
| $A_3 \bar{A}_2 10$ | 1 | 1 | X | X | 10 |

$$A_2 + \bar{A}_1 + A_1 A_0 = c$$

+ $A_2 A_0 +$

| | $A_1 A_0$ | $\bar{A}_1 \bar{A}_0$ | $\bar{A}_1 A_0$ | $A_1 \bar{A}_0$ | $A_1 \bar{A}_0$ |
|--------------------------|-----------|-----------------------|-----------------|-----------------|-----------------|
| $A_3 A_2$ | 1 | 0 | 1 | 1 | 0 |
| $\bar{A}_3 \bar{A}_2 00$ | 0 | 0 | 1 | 1 | 10 |
| $\bar{A}_3 A_2 01$ | 0 | 1 | 0 | 1 | 6 |
| $A_3 A_2 11$ | X | X | X | X | X |
| $A_3 \bar{A}_2 10$ | 1 | 0 | 1 | X | X |

$$d = A_1 \bar{A}_0 + \bar{A}_2 \bar{A}_0 + \bar{A}_2 A_0 + \bar{A}_2 \bar{A}_1 + A_2 \bar{A}_1 A_0$$

For f

| | $A_1 A_0$ | 01 | 11 | 10 |
|--------------------------|-----------|----|----|----|
| $A_3 A_2$ | 1 | 0 | 0 | 1 |
| $\bar{A}_3 \bar{A}_2 00$ | 0 | 1 | 1 | 0 |
| $\bar{A}_3 A_2 01$ | 1 | 1 | 0 | 1 |
| $A_3 A_2 11$ | X | X | X | X |
| $A_3 \bar{A}_2 10$ | 1 | 0 | 1 | X |

$$\bar{A}_1 \bar{A}_0 + A_3 + \bar{A}_1 \bar{A}_0 A_2 + \bar{A}_2 \bar{A}_1$$


For g $A_2 \bar{A}_0 \Rightarrow f$

| | $A_1 A_0$ | 01 | 11 | 10 |
|--------------------------|-----------|----|----|----|
| $A_3 A_2$ | 1 | 0 | 0 | 1 |
| $\bar{A}_3 \bar{A}_2 00$ | 0 | 0 | 1 | 1 |
| $\bar{A}_3 A_2 01$ | 1 | 1 | 0 | 1 |
| $A_3 A_2 11$ | X | X | X | X |
| $A_3 \bar{A}_2 10$ | 1 | 0 | 1 | X |

$$g = A_3 + A_1 \bar{A}_0 + A_1 \bar{A}_2 + A_2 \bar{A}_1$$

LOGIC DIAGRAM

for 7 segment display
[From the k map]

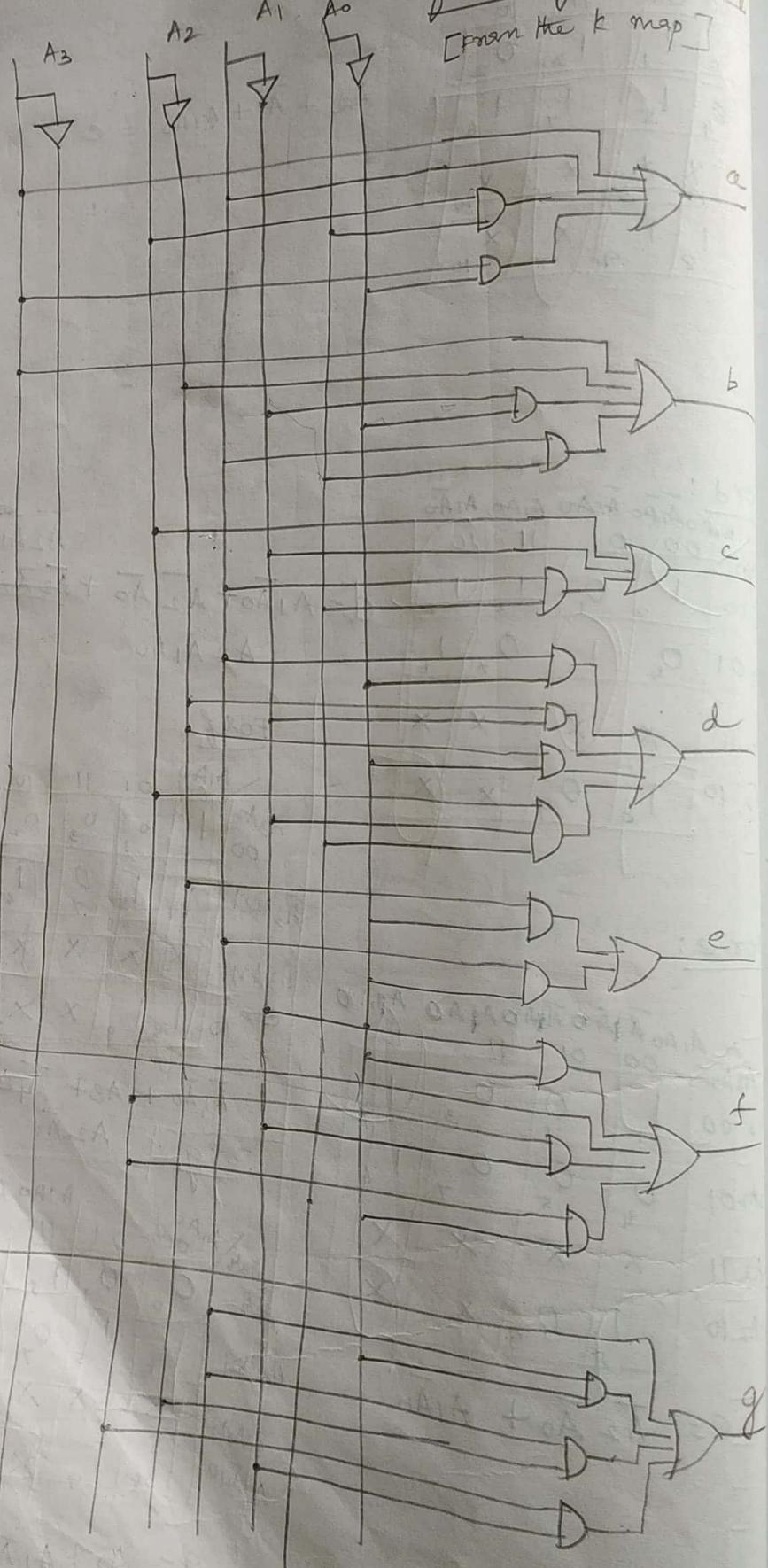

2^n inputs

4

Inputs

$D_0 \ D_1$

1 0

0 1

0 0

0 0

D_0

D_1

D_2


D_3

EX-OR

2ⁿ inputs need n outputs

For 2 inputs

| Inputs | | | | Outputs | | |
|----------------|----------------|----------------|----------------|---------|---|---|
| D ₁ | D ₂ | D ₃ | D ₄ | X | B | A |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |

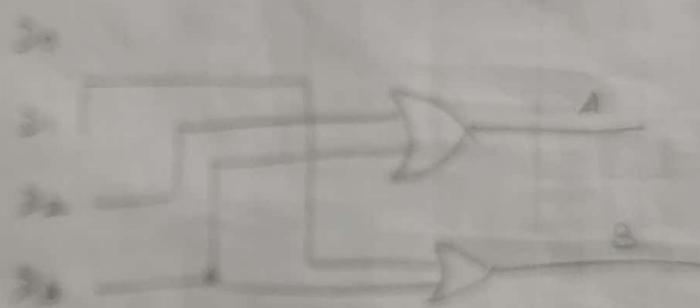


Logic diagram

Block diagram for 1 in of 2 in
A and B

8:3 Encoder:

| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | A | B | C |
|-------|-------|-------|-------|-------|-------|-------|-------|---|---|---|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

LOGIC DIAGRAM.

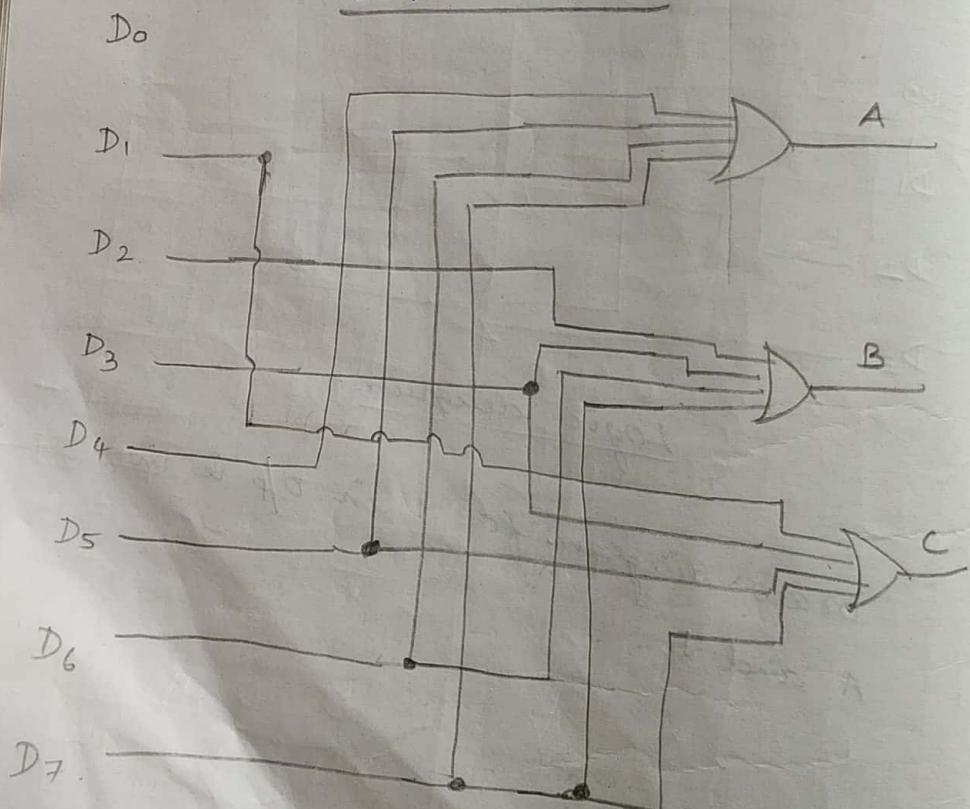

A B C

0 0 0

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0


1 1 1

Multiplexer (or) Mux

2^n inputs 1 output


& has n number of select lines

Also called as Data Selector

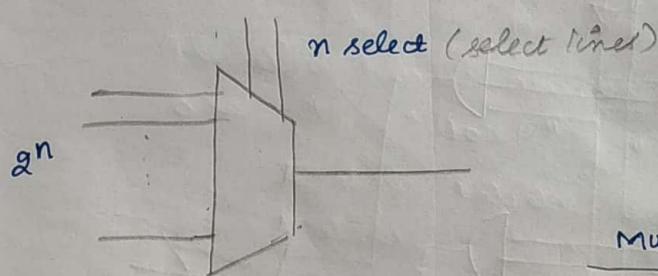

examples:


1 \Rightarrow 2:1 MUX

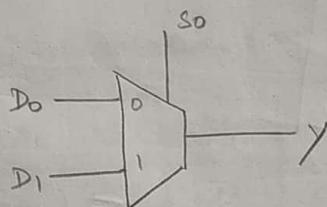

| MUX | Select lines |
|------|--------------|
| 2:1 | 1 |
| 4:1 | 2 |
| 8:1 | 3 |
| 16:1 | 4 |

$$\begin{array}{ll} S_0 = 0 & Y = D_0 \\ S_0 = 1 & Y = D_1 \end{array}$$

LOGIC DIAGRAM:


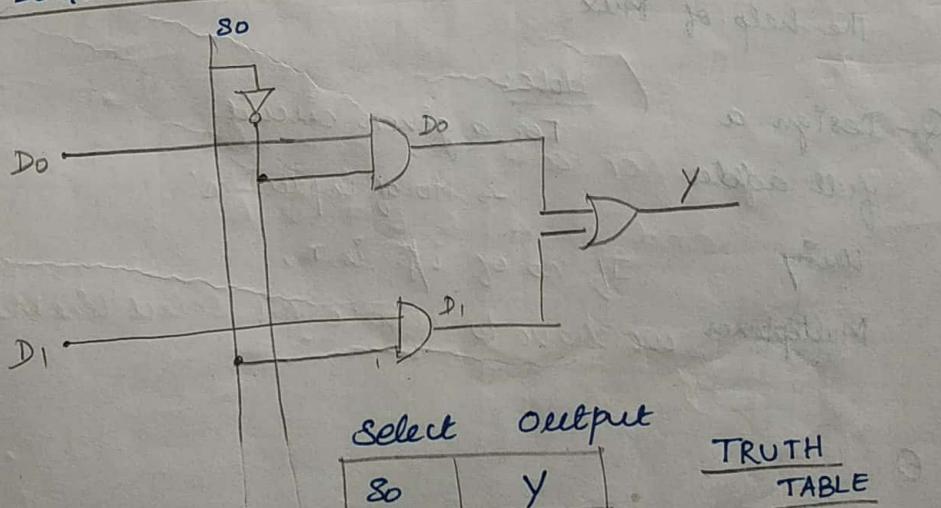


| Select | output |
|--------|--------|
| 0 | D_0 |
| 1 | D_1 |

TRUTH TABLE

$2 \Rightarrow$

4:1 MUX

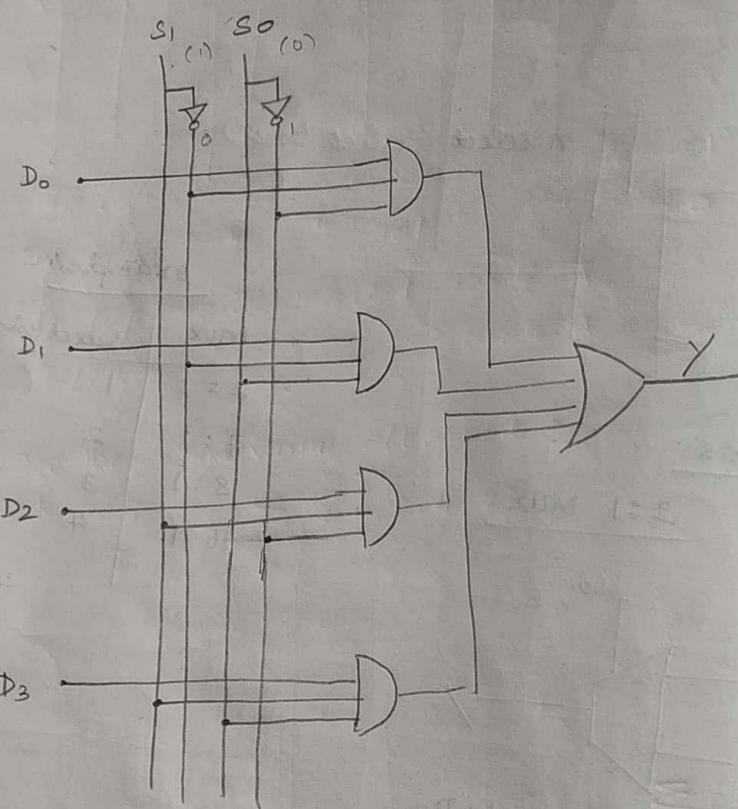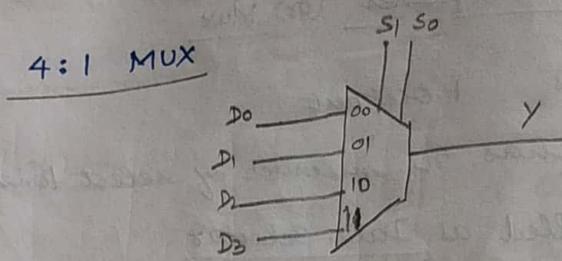

Advantage:

We can design any digital ckt with
the help of Mux

Q. Design a
full adder
using
Multiplexer

Note:

For a given circuit.


→ No of inputs 'n'

If no of i/p is n,
we have to choose $n-1$ select line Mux

For the true
seen
cout =

i/p \rightarrow 3
(A B C)

2

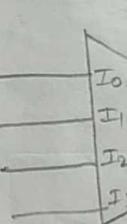

for Imple
sel

A B

| | | |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 2 | 0 | 1 |
| 3 | 0 | 1 |
| 4 | 1 | 0 |
| 5 | 1 | 1 |
| 6 | 1 | 1 |
| 7 | 1 | 1 |

Ø

Form the Truth table of full adder

$$\text{sum} = \Sigma(1, 2, 4, 7)$$


$$\text{cout} = \Sigma(3, 5, 6, 7)$$

i/p $\rightarrow 3$ output
(A B C) sum, carry.


2 select lines \rightarrow so choose 4:1 MUX

(They have 2 select lines)

4:1 MUX

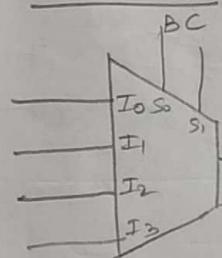

(we use separate mux for sum & carry)

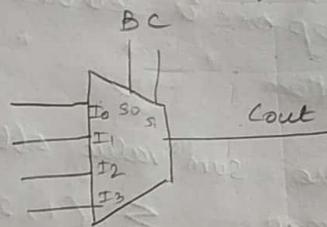

For Implementation table draw the
Select lines truth table of full adder
first.

| A | B | C | sum | carry |
|---|---|---|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 2 | 0 | 1 | 1 | 0 |
| 3 | 0 | 1 | 0 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

at line MUX)

Implementation table for sum.

| | I_0 | I_1 | I_2 | I_3 |
|-----------|-------|-------|-------|-------|
| \bar{A} | 0 | 1 | 2 | 3 |
| A | 4 | 5 | 6 | 7 |

A \bar{A} \bar{A} A

- (2) If both the nos are circled write as 1
 If both " " not " " as 0
 If top one is selected write A
 If bottom " " write A
- (1) See the sum value obtained from
 K map $\Sigma (1, 2, 4, 7)$

Implementation table for carry

| | I_0 | I_1 | I_2 | I_3 |
|-----------|-------|-------|-------|-------|
| \bar{A} | 0 | 1 | 2 | 3 |
| A. | 4 | 5 | 6 | 7 |
| | 0 | A | A | 1 |

$$\Sigma (3, 5, 6, 7)$$

(from full add)

always for a 0, 1 2 3 $\in A$

and 4 5 6 7 $\in \bar{A}$

Using 8

| | A | B | C |
|---|----------------|----------------|----------------|
| 0 | I ₀ | | |
| 1 | | I ₁ | |
| 1 | | | I ₂ |
| 0 | | | I ₃ |
| 1 | | | I ₄ |
| 0 | | | I ₅ |
| 0 | | | I ₆ |
| 1 | | | I ₇ |

$$Q. F_1 = \Sigma (0, 1)$$


$$F_2 = \Sigma (1)$$

$$\Rightarrow \bullet i/p -$$

8:1 M

| | A | B | C |
|----|---|---|---|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 |
| 3 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 |
| 5 | 0 | 1 | 0 |
| 6 | 0 | 1 | 1 |
| 7 | 0 | 1 | 1 |
| 8 | 1 | 0 | 0 |
| 9 | 1 | 0 | 0 |
| A | 1 | 0 | 1 |
| 10 | 1 | 0 | 1 |
| 11 | 1 | 0 | 0 |
| 12 | 1 | 1 | 0 |
| 13 | 1 | 1 | 0 |
| 14 | 1 | 1 | 1 |
| 15 | 1 | 1 | 1 |

Using 8:1 MUX

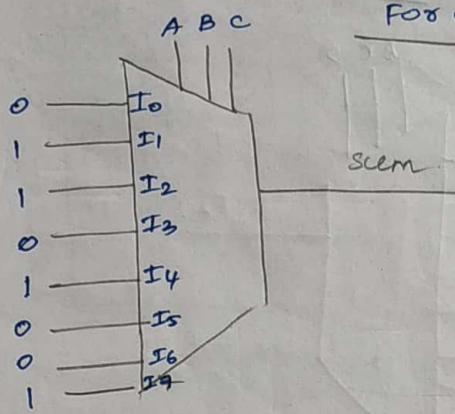


For example

$$Q. F_1 = \Sigma (0, 1, 3, 5, 7, 9, 11, 12)$$

$$F_2 = \Sigma (1, 5, 7, 11, 12, 13, 15)$$

\Rightarrow $i/p \rightarrow s4 \Rightarrow n$
no of select lines $n-1=3$
(choose 8:1 MUX)

| 8:1 MUX | | | | For F_1 | | | | | | | |
|-----------|----|---|---|-----------|-------|-------|-------|-------|-------|-------|-------|
| A | B | C | D | I_0 | I_1 | I_2 | I_3 | I_4 | I_5 | I_6 | I_7 |
| \bar{A} | 0 | 0 | 0 | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| | 1 | 0 | 0 | 1 | 0 | 1 | 2 | 3 | 4 | 5 | 7 |
| | 2 | 0 | 0 | 1 | 0 | 1 | 2 | 3 | 4 | 5 | 6 |
| | 3 | 0 | 0 | 1 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| | 4 | 0 | 1 | 0 | 0 | 1 | 2 | 3 | 4 | 5 | 6 |
| | 5 | 0 | 1 | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| | 6 | 0 | 1 | 1 | 0 | 1 | 2 | 3 | 4 | 5 | 6 |
| | 7 | 0 | 1 | 1 | 1 | 0 | 1 | 2 | 3 | 4 | 5 |
| For F_2 | | | | | | | | | | | |
| A | 8 | 1 | 0 | 0 | 0 | 1 | 2 | 3 | 4 | 5 | 7 |
| | 9 | 1 | 0 | 0 | 1 | 0 | 1 | 2 | 3 | 4 | 5 |
| | 10 | 1 | 0 | 1 | 0 | 1 | 2 | 3 | 4 | 5 | 6 |
| | 11 | 1 | 0 | 1 | 1 | 0 | 1 | 2 | 3 | 4 | 5 |
| | 12 | 1 | 1 | 0 | 0 | 1 | 2 | 3 | 4 | 5 | 6 |
| | 13 | 1 | 1 | 0 | 1 | 0 | 1 | 2 | 3 | 4 | 5 |
| | 14 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 2 | 3 | 4 |
| | 15 | 1 | 1 | 1 | 1 | 0 | 1 | 2 | 3 | 4 | 5 |

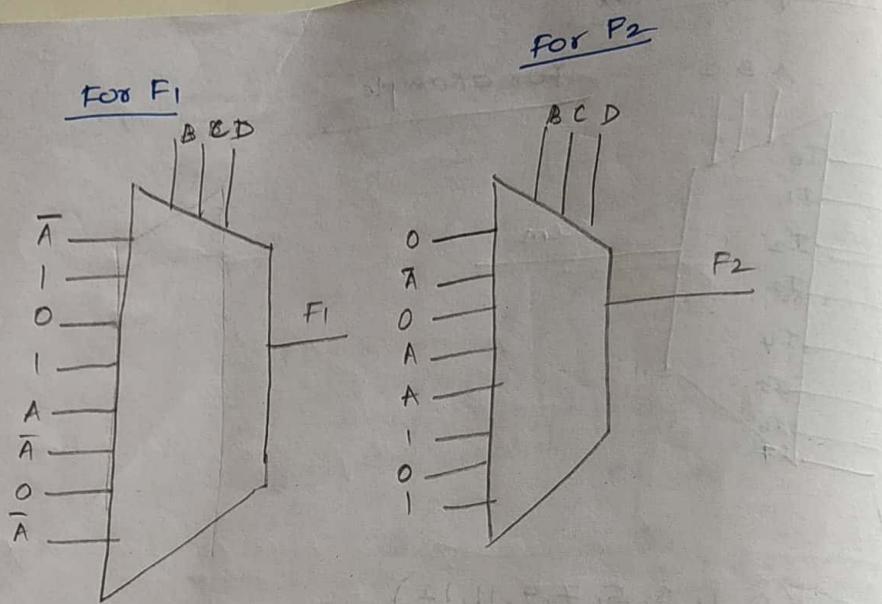

4/9/18

Priority Encoder.

4:2


| D ₀ | D ₁ | D ₂ | D ₃ | Y ₁ | Y ₀ |
|----------------|----------------|----------------|----------------|----------------|----------------|
| 8 | 1 | 0 | 0 | 00 | |
| 4, 12 | x | 1 | 0 | 01 | |
| 2, 6, 10, 14 | x | x | 1 | 10 | |
| 1, 3, 5, 7 | x | x | x | 11 | |
| 9, 11, 13, 15 | | | | | |

$y_1 \Rightarrow$

| D ₀ | D ₁ | D ₂ | D ₃ | 00 | 01 | 11 | 10 |
|----------------|----------------|----------------|----------------|----|----|----|----|
| 00 | 00 | 0 | 1 | 1 | 1 | 1 | 2 |
| 01 | 01 | 1 | 1 | 1 | 1 | 1 | 1 |
| 11 | 11 | 1 | 1 | 1 | 1 | 1 | 1 |
| 10 | 10 | 1 | 1 | 1 | 1 | 1 | 1 |
| | | | | 8 | 9 | 11 | 10 |

$$y_1 = D_3 + D_2$$

Logic Diagram

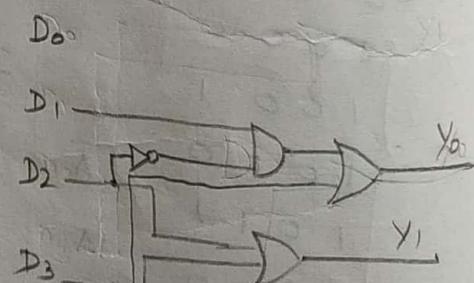

$$Y_2 = \Sigma(2, 4, 5, 6) = D_2 D_3$$

$$Y_1 = \Sigma(2, 4, 5, 6) = D_2 D_3$$

$$Y_0 = \Sigma(2, 4, 5, 6) = D_2 D_3$$

Draw

For Y_0

| $D_0 D_1$ | $D_2 D_3$ | 00 | 01 | 11 | 10 |
|-----------|-----------|----|----|----|----|
| 00 | 00 | 0 | 1 | 1 | 3 |
| 01 | 14 | 1 | 1 | 7 | 6 |
| 11 | 10 | 1 | 1 | 5 | 14 |
| 10 | 8 | 1 | 9 | 11 | 10 |

000

in priority
encoder
we get
simultaneous
encoder.

$$Y_0 = D_3 + D_1 \bar{D}_2$$

\Rightarrow 8:3 PE

| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | x | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 2 | x | x | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 3 | x | x | x | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 4 | x | x | x | x | 1 | 0 | 0 | 1 | 0 | 0 |
| 5 | x | x | x | x | x | 1 | 0 | 1 | 0 | 1 |
| 6 | x | x | x | x | x | x | 1 | 1 | 1 | 0 |
| 7 | x | x | x | x | x | x | x | 1 | 1 | 1 |

$$Y_2 = \Sigma(4, 5, 6, 7)$$

expression written from
MSB

$$= D_4 + D_5 \bar{D}_6 \bar{D}_7 + D_6 \bar{D}_7 + D_7$$

$$Y_1 = \Sigma(2, 3, 6, 7)$$


$$= D_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_6 \bar{D}_7 + D_7$$

$$Y_0 = \Sigma(1, 3, 5, 7)$$


$$= D_7 + D_5 \bar{D}_6 \bar{D}_7 + D_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7$$

Draw logic diagram:-


Demultiplexers

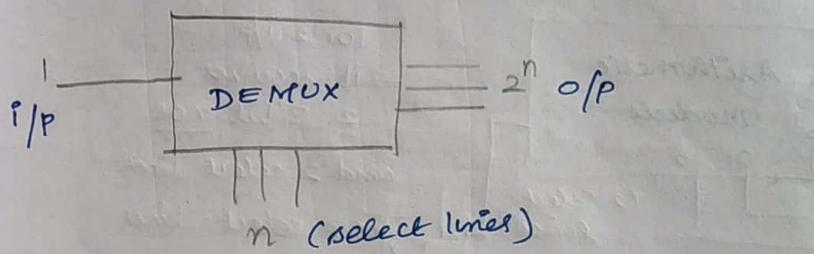

1:4 Demux

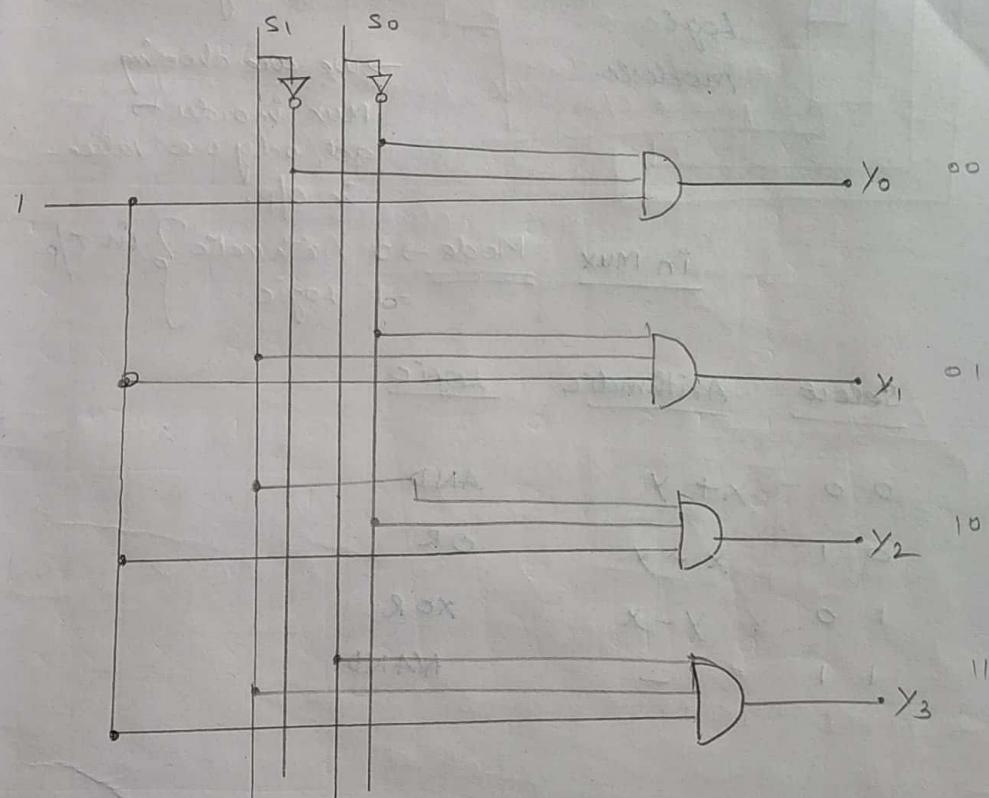

8-bit ALU:-

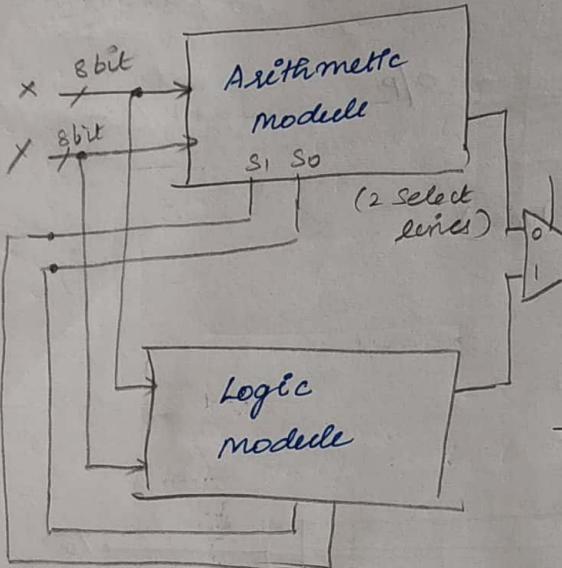

For 2⁸ i/p
→ it receives
2 8-bit nos
and 2 select lines.
These select lines
are fed to
the select lines
of Logic module.

→ We are choosing
Mux in order to
get only one value
in O/P.




in Mux Mode → 0 Arithmetic } in O/P
 = 1 Logic }

| Select | Arithmetic | Logic |
|--------|------------|-------|
| 0 0 | $x + y$ | AND |
| 0 1 | $x - y$ | OR |
| 1 0 | $y - x$ | XOR |
| 1 1 | - | NAND |


For performing Arithmetic operations:
 $x + y$ and $x - y$.

Using 4 bit → construct 4 F.A
(RCA)


4 bit

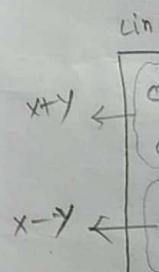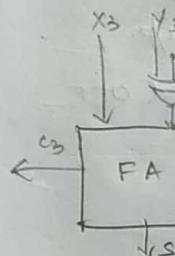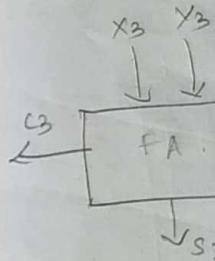

4 bit Adder & Subtractor

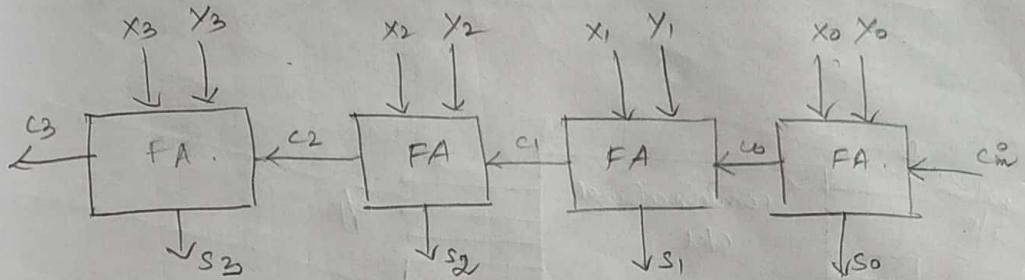

For $X+Y$ & $X-Y$

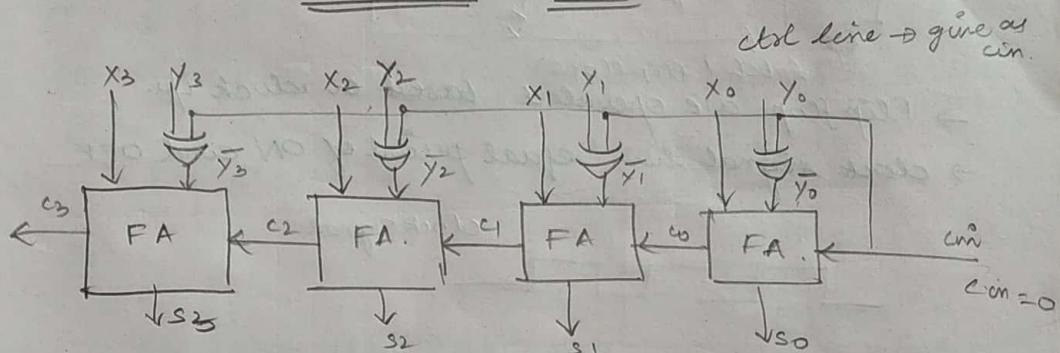

| lin \neq Y o/p | |
|------------------|--------------|
| $x+y$ | $0\ 0\ 0\ 0$ |
| | $0\ 1\ 1\ 1$ |
| $x-y$ | $1\ 0\ 1\ 0$ |
| | $1\ 1\ 0\ 0$ |

when $c_{in} = 0$


$$x+y+0$$

when $c_{in} = 1$

$$x+\overline{y}+1$$


$$= x-y$$

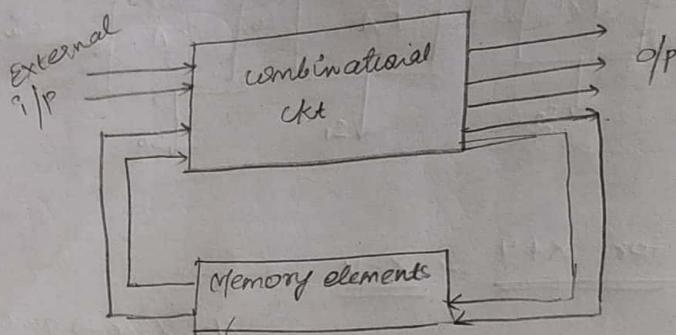7.9.18 UNIT - 3 SYNCHRONOUS SEQUENTIAL CIRCUITS




- Flip flops are operated based on clock i/p.
- clock signal has equal period of ON and OFF

clock signal.

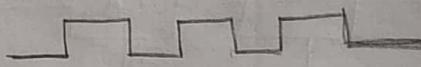


LATCHES:-

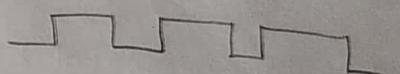- Does not have clock signal
- It has combination of gates
- They are mostly used as feed back elements in asynchronous ckt
- LEVEL TRIGGERED signals (Latches)
- O/p responds during the level
- Flip flops are edge triggered clock signal.



* SR latch (Basic latch)


NOR NAND

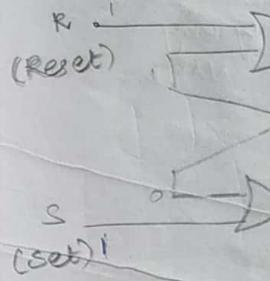

NOR


| A | B | |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

SR la

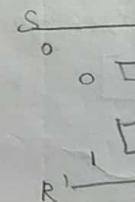

NAND

| A | B | |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

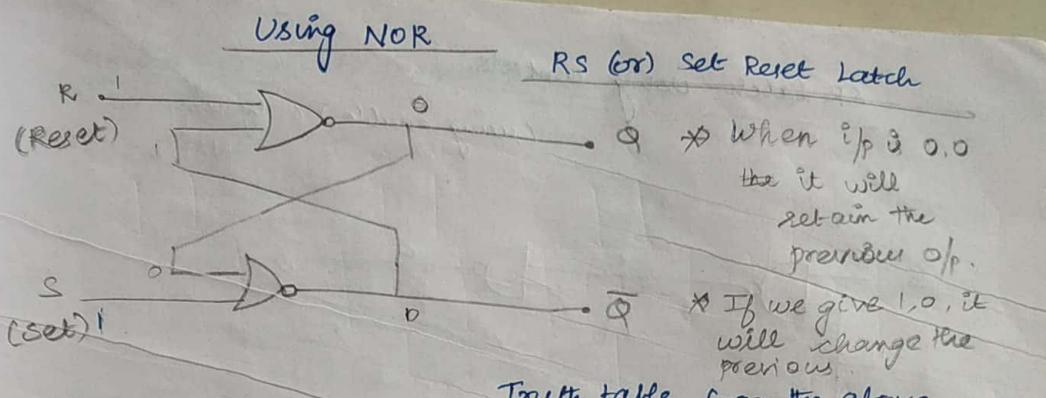


NOR

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Truth table from the above diagram

| R | S | Q | \bar{Q} |
|---|---|---|-----------|
| 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 |

(in flip flop, it is indetermined state)

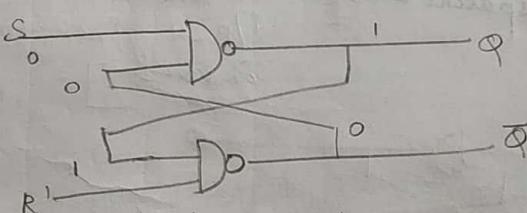SR latch using NAND gate

initial case
assume 0,1;
depending upon o/p
change the previous value.

NAND


| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| S | R | Q | \bar{Q} |
|---|---|---|-----------|
| 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |


→ retain the previous value

→ invalid

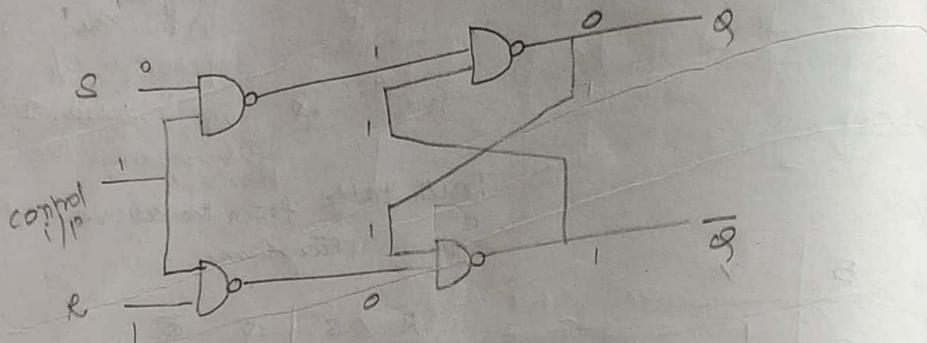SR latch using controls.
 (using enable) only using NAND




symbol of Latch

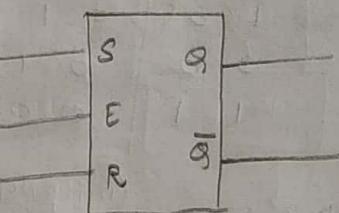

For 'Q' we
put bubble

Positive edge

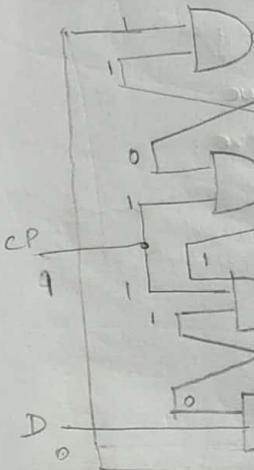

clk ↑

D _____



latch Q _____

flip flop Q _____

→ Q

the O/p

TRUE

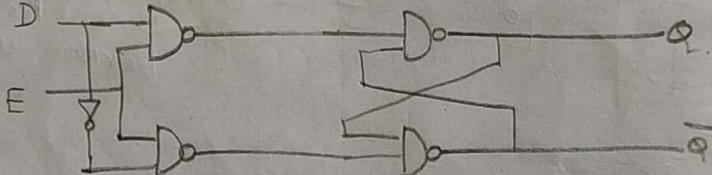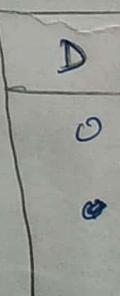

(Mostly 'D' flip flop
is used for
designing)

- * Respond to changes given to level (in lab)
- * concept of latch & flip flop is it follows the i/p
(op follows i/p)

if D is 1, Q is
if " " 0, " " 0


if E is 0, Q is 0
if " " 1, Q " 1

enable) only using
NAND.

Positive edge triggered D-flip flop.


→ one of i/p is 0, the o/p is
1 (first part)

both i/p \Rightarrow 1 o/p is 0

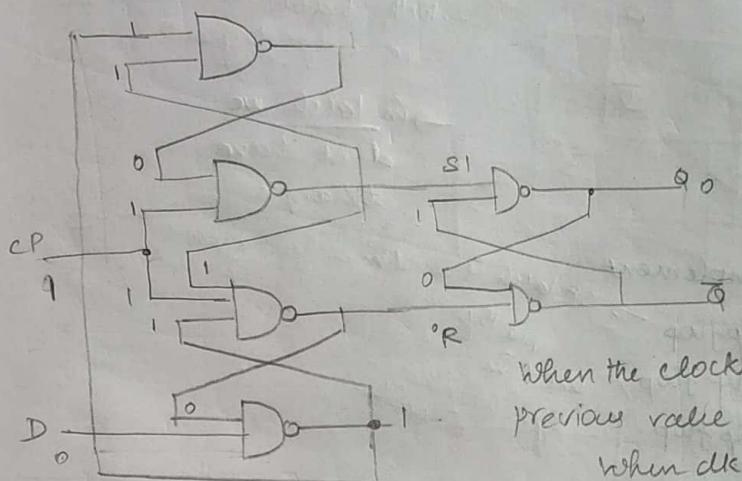

When the clock pulse is 0,
previous value is retained

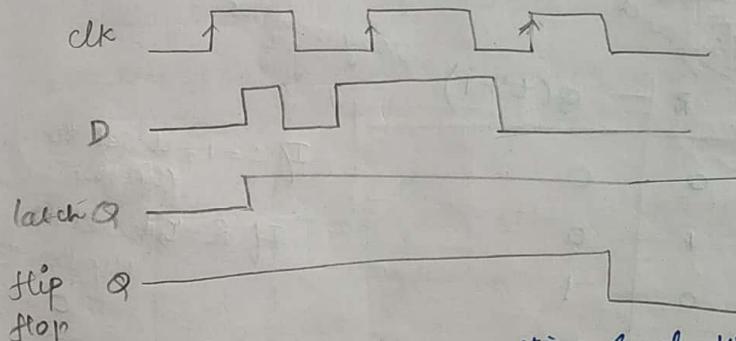When clk pulse is 1
there is a change,
output follows the i/p




→ Only at the transition level, when
the o/p changes, it is called as flip flop.

TRUTH TABLE for D flip flop (characteristic Table)

| D | Q |
|---|---|
| 0 | 0 |
| 1 | 1 |

| $Q(t)$ before P clock | D | $Q(t+1)$ |
|-----------------------------|---|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

D value
retained
at t.

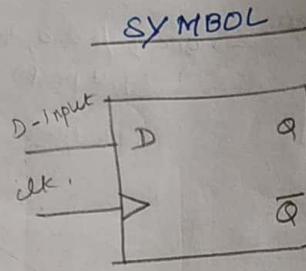

- without bubble +ve edge trigger
- with bubble -ve edge trigger
- in latch we don't have triangle

We can implement

| | |
|-----------------------|--|
| S-R flip flop | → SR latch is used in a synchronous circuit. |
| J-K flip flop | not yet used in synchronous circuits. |
| (Toggle) T flip flop. | used in synchronous circuits. |
| D flip flop | $\boxed{01}$ |

SR FLIP FLOP

| Q | S | R | $Q(t+1)$ | Using NOT gate. |
|-----|-----|-----|----------|------------------------------------|
| 0 | 0 | 0 | 0 | If $S=1$, it sets the flip flop |
| 0 | 0 | 1 | 0 | If $R=1$, it resets the flip flop |
| 0 | 1 | 0 | 1 | |
| 0 | 1 | 1 | I.D. | 0 |
| 1 | 0 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 1 | |
| 1 | 1 | 1 | I.D. | |

General characteristic table of SR Latch.

| S | R | $Q(t)$ |
|-----|-----|--------------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 → (Reset) |
| 1 | 0 | 1 → set |
| 1 | 1 | Ineterminate |


JK FLIP

| J | K |
|---|---|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| 1 | 1 |

| Q | J | K |
|-----|-----|-----|
| 0 | 0 | 0 |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |
| 1 | 1 | 1 |

T flip flop
to avoid ...

Apply k map

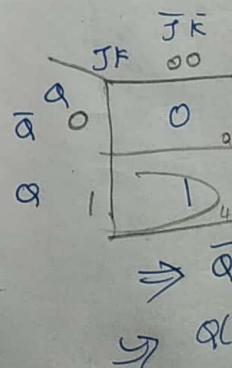

at bubble
edge trigger
bubble
edge trigger

at we
nt have
single
synchronous
circuit

NOT
gate.

If $S=1$, it set the
flip flop

If $R=1$, it reset the
flip flop

0

JK FLIP FLOP

| J | K | $Q(t+1)$ |
|---|---|-------------------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\overline{Q(t)}$ |

| Q | J | K | $Q(t+1)$ |
|---|---|---|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

T flip flop is implemented from JK flip flop
to avoid racing condition (complemented form)

Apply K map for $Q(t+1)$


for J-K

| | $\bar{J}\bar{K}$ | $\bar{J}K$ | $J\bar{K}$ | $J\bar{K}$ |
|-------------|------------------|------------|------------|------------|
| JF | 00 | 01 | 11 | 10 |
| \bar{Q}_0 | 0 | 0 | 1 | 1 |
| Q_1 | 1 | 0 | 0 | 1 |

$$\Rightarrow \bar{Q}J + Q\bar{K} \quad \text{characteristic eqn of JK flip flop}$$


$$\Rightarrow Q(t+1) = \bar{Q}(t)J + Q(t)\cdot K$$

$$= \bar{Q} J + Q \bar{K}$$

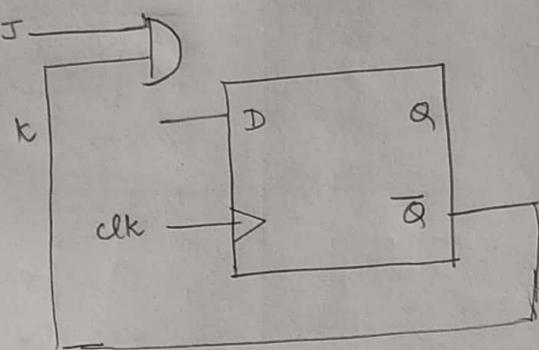


J K flip flop D-Flip flop

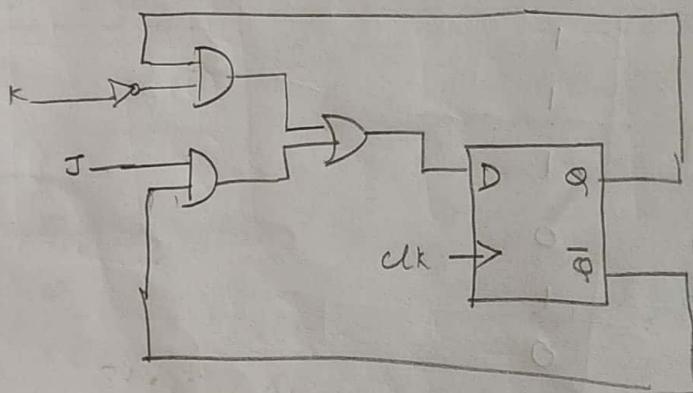char egn of D flip flop is D for $Q(t+1)$
(since it follows the I/P)




| a | SR | $\bar{S}\bar{R}$ | $\bar{S}R$ | SR | $S\bar{R}$ |
|-----------|----|------------------|------------|----|------------|
| \bar{Q} | 0 | 1 | x | 1 | |
| Q | 1 | | x | 1 | |

$$Q(t+1) = S + Q\bar{R}$$

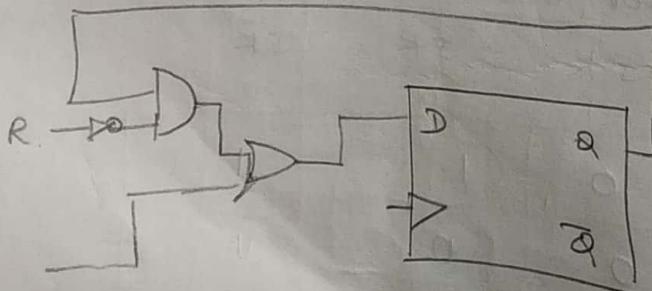


11.09.18

JK flip flop.

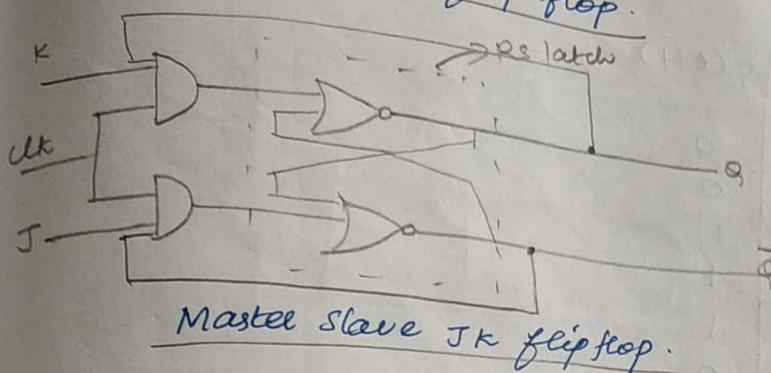

| J | K | Q(t+1) |
|---|---|--------|
| 0 | 0 | Q(t) |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q̄(t) |

Master slave JK flip flop.

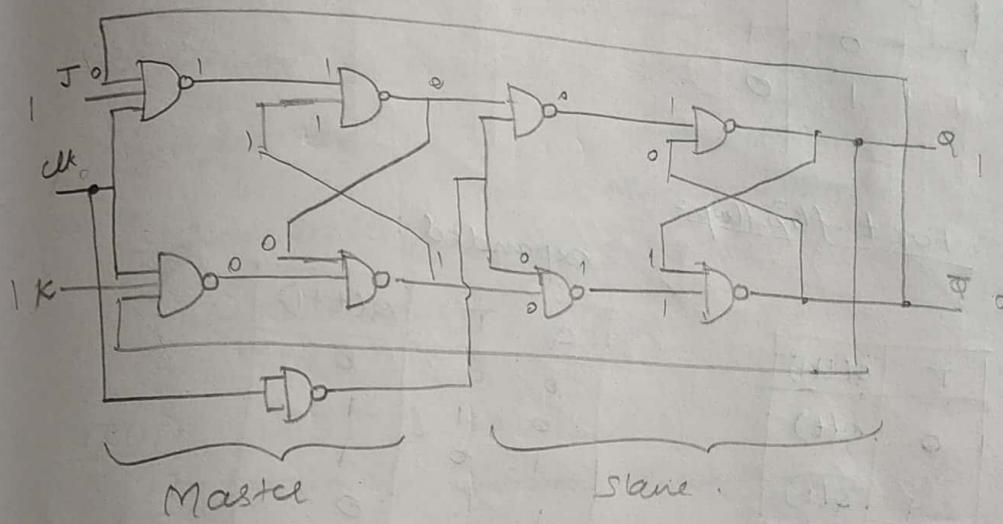

→ Master receives external if
→ Mostly 1 1 condition is used to avoid racing condition

→ During -ve pulse cycle there is no change in the MASTER.

→ no change in slave (positive)
change in Master.

→ NO RACING CONDITION (negative)

No change in master
change in slave.

2 flip flop connected in cascade,
it is master flip flop.

| Q | J | K | $Q(t+1)$ |
|-----|-----|-----|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

For T flip flop:-

expanded:


| T | $Q(t+1)$ |
|-----|-------------------|
| 0 | $Q(t)$ |
| 1 | $\overline{Q(t)}$ |

| Q | T | $Q(t+1)$ |
|-----|-----|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$$Q(t+1) = \overline{Q}T + Q\overline{T}$$

$$= Q \oplus T$$

T flip flop from D flip flop.

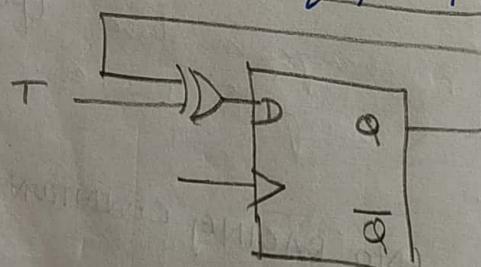

1. TRUTH

FO

TE

2. STATE

O/

is

3. Trans

4. Excite


is a

flip

5. Chara

i/p

SR from D

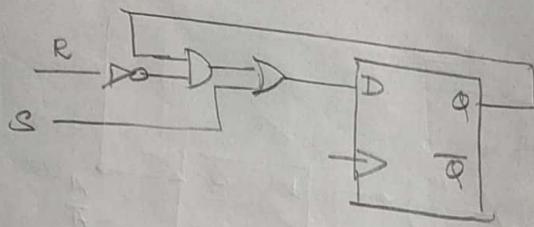

Synchronous seq. ckt.

Analysis

⇒ circuit or equations

↓
equations

↓
State table

↓
State diagram

Design

↓ (From problem specification)

state diagram

↓

state table

↓

transition table

↓

equations

↓

logical Diagram

1. TRUTH TABLE:

For known i/p, ~~for gate~~ depending upon the type of gate o/p is generated

2. STATE TABLE:


O/p for various i/p + Present state, ^{next} State is obtained.

3. Transition table:

4. Excitation table: O/p is known, $Q(t)$ and $Q(t+1)$ is also known, present state \downarrow next state flip flop inputs are found

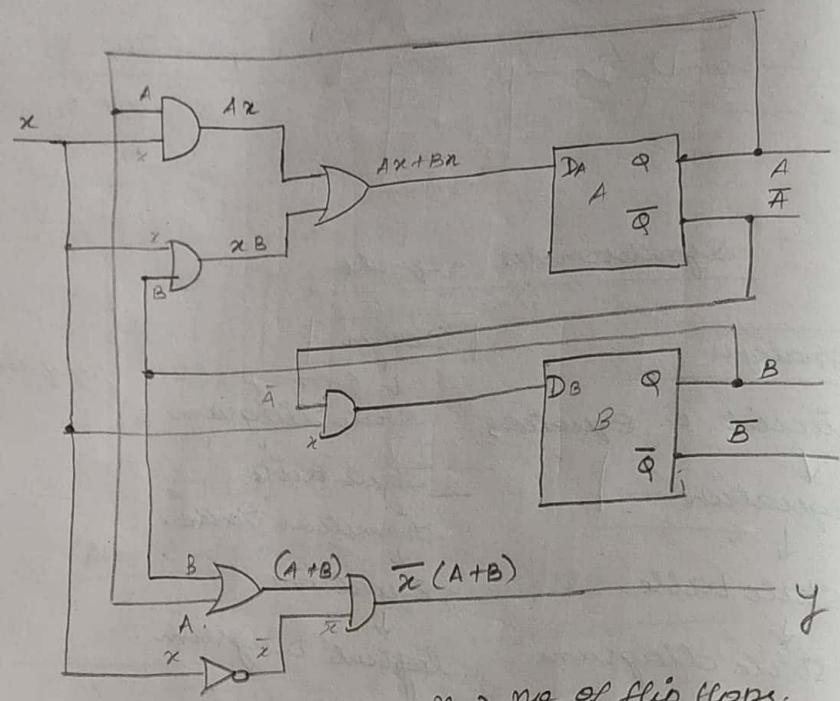5. Characteristic table:

Next state value, we have to find. i/p & present states are known.



$n \rightarrow$ no of flip flops.

$2^n \rightarrow$ no of states.

Equations.

State equations:

$$A(t+1) = D_A = xA + xB = x(A+B)$$

$$B(t+1) = D_B = x\bar{A}$$

Output Equation:

$$y = \bar{x}(A+B)$$

State table:


PS \rightarrow Present state (depends on 2 flip flops)

| | P | S | x | N.S | | Output |
|--------------------|---|---|---|--------|--------|--------------------|
| 00 \rightarrow a | 0 | 0 | 0 | A(t+1) | B(t+1) | $y = \bar{x}(A+B)$ |
| 01 \rightarrow b | 0 | 0 | 1 | 0 | 0 | 0 |
| 10 \rightarrow c | 0 | 0 | 1 | 0 | 1 | 0 |
| 11 \rightarrow d | 0 | 1 | 0 | 0 | 0 | 1 |
| | 0 | 1 | 1 | 1 | 1 | 0 |
| | 1 | 0 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 1 | 1 | 0 | 1 |
| | 1 | 1 | 0 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 | 0 |

Final State Table

| P S | N S |
|-----|-------|
| AB | $x=0$ |
| a | a |
| b | a |
| c | a |
| d | a |

State Diagram

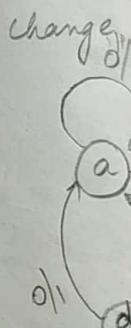


Final State Table \Rightarrow Mealy

| PS | NS | | Output Y | | |
|----|--------|--------|----------|--------|--|
| AB | $x=0$ | $x=1$ | $x=0$ | $x=1$ | |
| a | a b | b a | 0 1 | 0 0 | $00 \rightarrow a$ $01 \rightarrow b$ |
| b | a d | d a | 0 1 | 0 0 | $10 \rightarrow c$ $11 \rightarrow d$ |
| c | a c | c a | 1 1 | 0 0 | |
| d | a c | c a | 1 1 | 0 0 | |


state Diagram

- \nearrow Mealy state diagram
(O/p depends on present state, i/p)
- \searrow Moore state diagram.
(depends on present state)

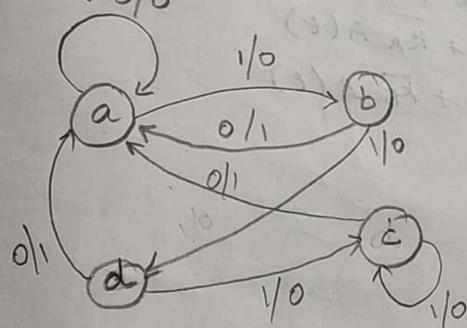change in state \rightarrow arrow (represented)



14/09/18

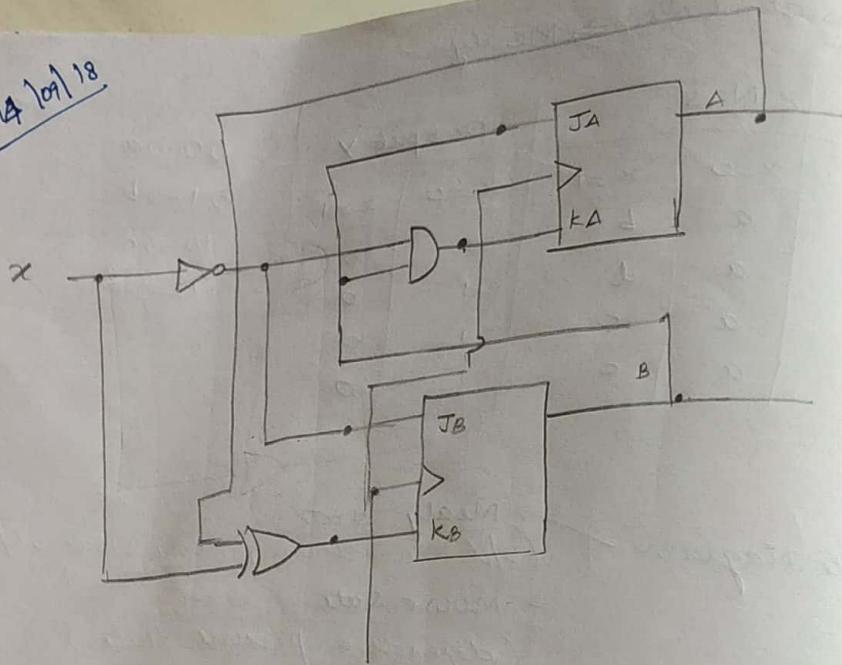

$$Q(t+1) = J \bar{Q}(t) + \bar{K} Q(t)$$

$$A(t+1) = J_A \bar{A}(t) + \bar{K}_A A(t)$$

$$B(t+1) = J_B \bar{B}(t) + \bar{K}_B B(t)$$

$$J_A = B$$

$$J_B = \bar{x}$$

$$K_A = \bar{x} B$$

$$\bar{K}_A = \overline{\bar{x} B}$$

$$= x + \bar{B}$$

$$K_B = \bar{x} \oplus \bar{A} - x \oplus A$$

$$\bar{K}_B = \bar{x} \oplus \bar{A}$$

$$= x A + \bar{x} \bar{A}$$

$$A(t+1) =$$

$$B(t+1) =$$

$$A(t+1)$$

$$B(t+1)$$

$$P$$

$$A$$

$$\begin{cases} 0 \\ 0 \\ \vdots \\ 0 \end{cases}$$

$$\begin{cases} 1 \\ \vdots \\ 0 \end{cases}$$

$$A(t+1) = B\bar{A}(t) + (x + \bar{B}) A(t)$$

$$B(t+1) = \bar{x}\bar{B}(t) + (x_A + \bar{x}\bar{A}) B(t)$$

$$\begin{aligned} A(t+1) &= B\bar{A}(t) + (x + \bar{B}) A(t) \\ &= B\bar{A}(t) + x A(t) + \bar{B} A(t) \\ &= B\bar{A}(t) + \bar{B} A(t) + x A(t) \\ &= \cancel{B \odot \bar{A}(t)} + x A(t) \\ &= B \oplus A(t) + x A(t) \end{aligned}$$

$$\begin{aligned} B(t+1) &= \bar{x}\bar{B}(t) + x A B(t) + \bar{x}\bar{A} B(t) \\ &= \bar{x}\bar{B}(t) + B(t) (x \odot A) \end{aligned}$$


State Table:

| P | S | x | Ns | | Output |
|---|---|---|--------|--------|--------|
| A | B | x | A(t+1) | B(t+1) | |
| { | 0 | 0 | 0 | 1 | 1 |
| | 0 | 0 | 0 | 0 | 0 |
| | 0 | 1 | 1 | 1 | 0 |
| | 0 | 1 | 1 | 1 | 1 |
| { | 1 | 0 | 1 | 0 | 0 |
| | 1 | 0 | 1 | 0 | 0 |
| | 1 | 1 | 0 | 0 | 1 |
| | 1 | 1 | 0 | 1 | |


New state table:

| P S | NS | |
|-----|-------|-------|
| | $x=0$ | $x=1$ |
| a | b | a |
| b | d | c |
| c | d | c |
| d | a | d |

QD

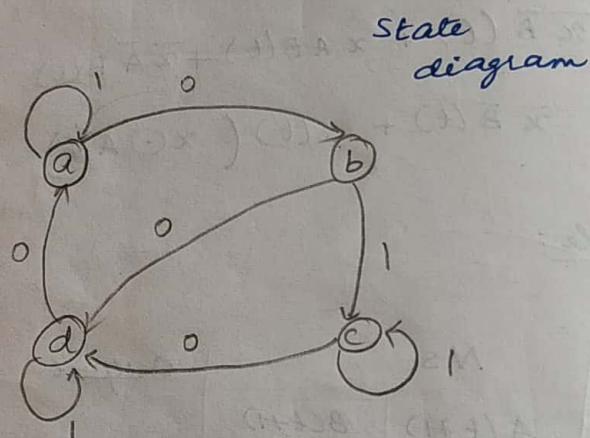


2.

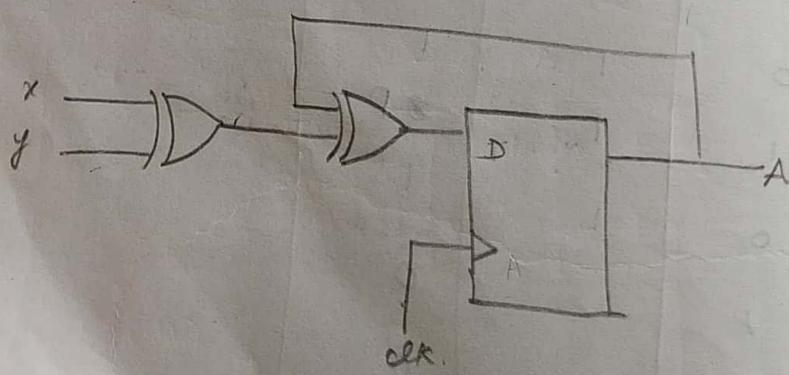

D =

sta

A

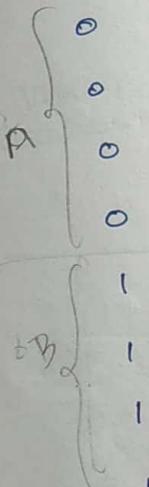

Final

P8

$$Q(t+1) = D \quad \text{D flip flop.}$$

$$\begin{aligned} D &= (x \oplus y) \oplus A \\ &= A \oplus (x \oplus y) \\ &= A \oplus x \oplus y. \end{aligned}$$


State Table:

| A | x | y | Q(t+1) = D |
|---|---|---|------------|
| A | 0 | 0 | 0 |
| | 0 | 1 | 1 |
| | 1 | 0 | 1 |
| | 1 | 1 | 0 |
| B | 0 | 0 | 1 |
| | 0 | 1 | 0 |
| | 1 | 0 | 0 |
| | 1 | 1 | 1 |

Final State:


B8

State diagram

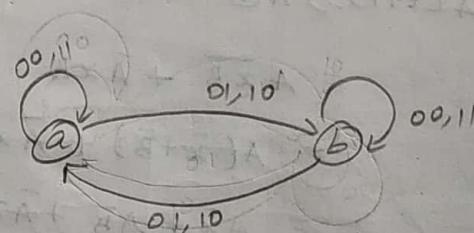

| PS | NS | | | |
|----|-----------|----|----|----|
| A | $xy = 00$ | 01 | 10 | 11 |
| 0 | a | b | b | a |
| 1 | b | a | a | b |

3.

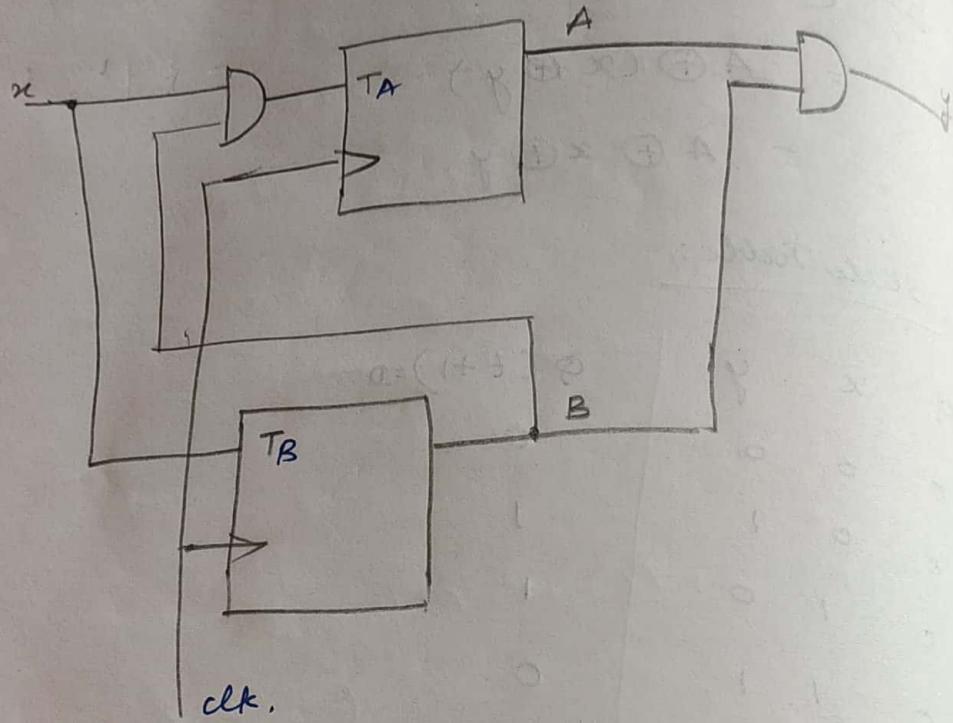

$$Q(t+1) = Q \oplus T$$

$$A(t+1) = A \oplus T_A$$

$$B(t+1) = B \oplus T_B$$

$$T_A = x \cdot B$$

$$T_B = x$$

$$A(t+1) = A \oplus x \cdot B$$

$$= A \bar{x} \bar{B} + \bar{A} x B$$

$$= A(\bar{x} + \bar{B}) + \bar{A} x B$$

$$= A\bar{x} + A\bar{B} + \bar{A} x B.$$

$$y = A \cdot B$$

$$B(t+1) = B \oplus x$$

$$= B\bar{x} + \bar{B}x.$$

Moore's state Table: II

| P S | | N.S | | O/P y |
|-----|---|-------|-------|-------|
| A | B | $x=0$ | $x=1$ | |
| | | A | B | |
| 0 | 0 | b | | 0 |
| 0 | 1 | c | | 0 |
| 1 | 0 | d | | 0 |
| 1 | 1 | a | | 1 |


output is represented
in moore state
table.

Table I.

| P.S | | | N.S | | $y = A \cdot B$ |
|-----|---|-----|----------|----------|-----------------|
| A | B | x | $A(t+1)$ | $B(t+1)$ | |
| a | 0 | 0 | 0 | 0 | 0 |
| | 0 | 1 | 0 | 1 | 0 |
| b | 0 | 0 | 0 | 1 | 0 |
| | 0 | 1 | 1 | 0 | 0 |
| c | 1 | 0 | 1 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 |
| d | 1 | 0 | 1 | 1 | 1 |
| | 1 | 1 | 0 | 0 | 1 |

Moore's state diagram

it depends only on B.

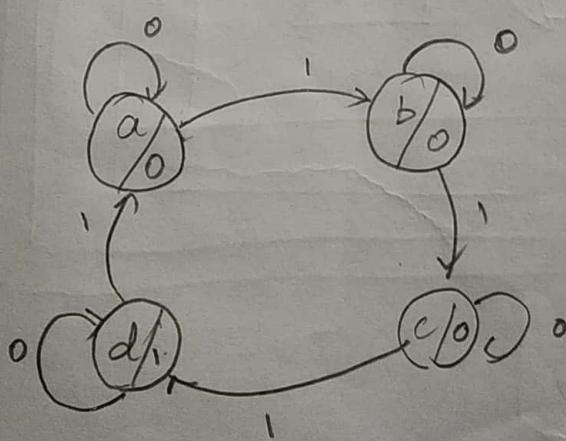

4. A sequential circuit has 2 JK flipflops 'A' and 'B', 2 inputs 'x' and 'y' and 1 output z. The flipflop i/p equations and ctkt o/p eqns are

$$JA = \boxed{Bx + B'y'}$$

$$KA = B'y'$$


$$JB = A'x$$

$$KB = A + xy'$$

$$z = Ax'y' + Bx'y' \Rightarrow (A+B)x'y'$$


- (i) Draw the logic diagram of the ckt
- (ii) Tabulate the state table
- (iii) Derive the state eqns for A and B
- (iv) Draw the state diagram.

refer JK flipflop.

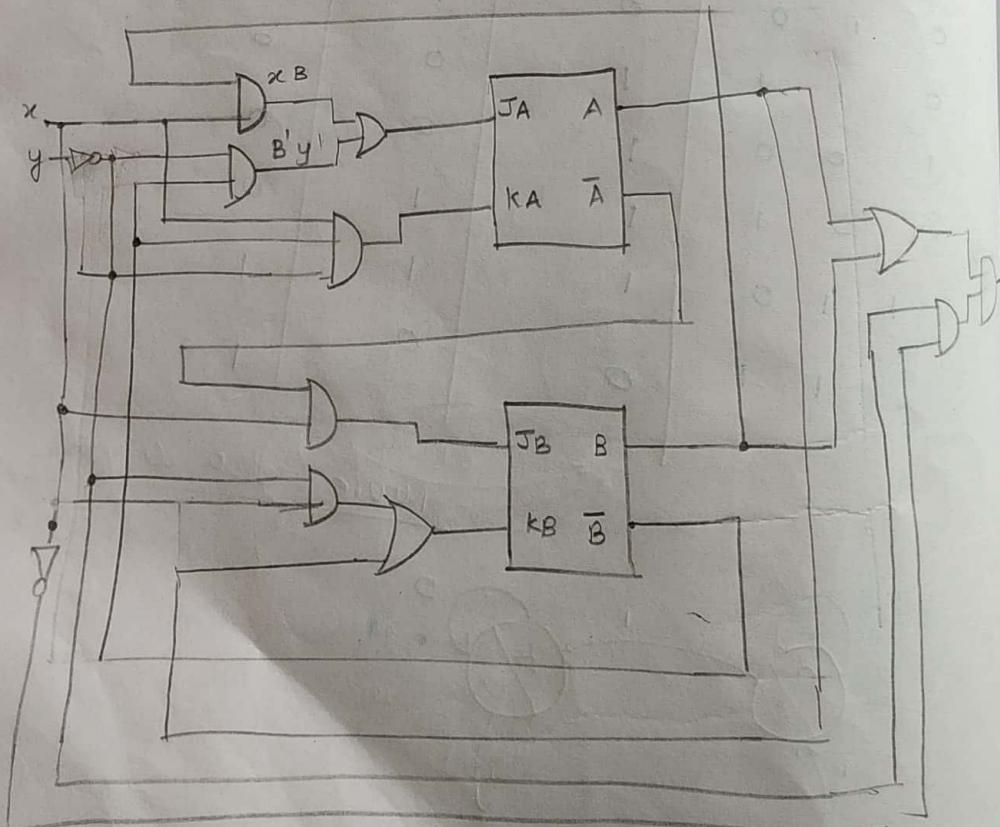

flops
and
ations

B.
JK flipflop.

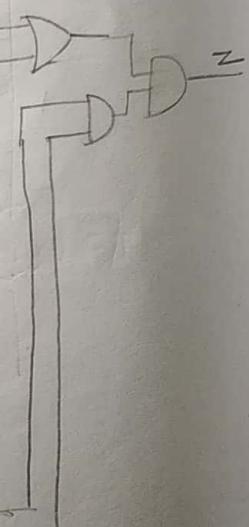


| A | B | x | y | A(t+1) | | B(t+1) | z |
|---|---|---|---|--------|---|--------|---|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |

| PS | N.S | x | y | $x=01$ | 10 | 11 | 00 | 01 | 10 | 11 | O/P |
|----|-----|---|---|--------|----|----|----|----|----|----|---------|
| A | B | | | a | a | b | b | c | c | d | |
| a | c | | | a | a | b | b | c | c | d | 0 0 0 0 |
| b | b | | | a | a | a | a | b | b | c | 0 0 0 0 |
| c | c | | | b | b | c | c | a | a | d | 0 0 0 0 |
| d | a | | | c | c | a | a | b | b | c | 0 0 0 0 |

25/09/18

Design of clocked sequential logic circuit

Problem statement. (no of i/p & o/p)

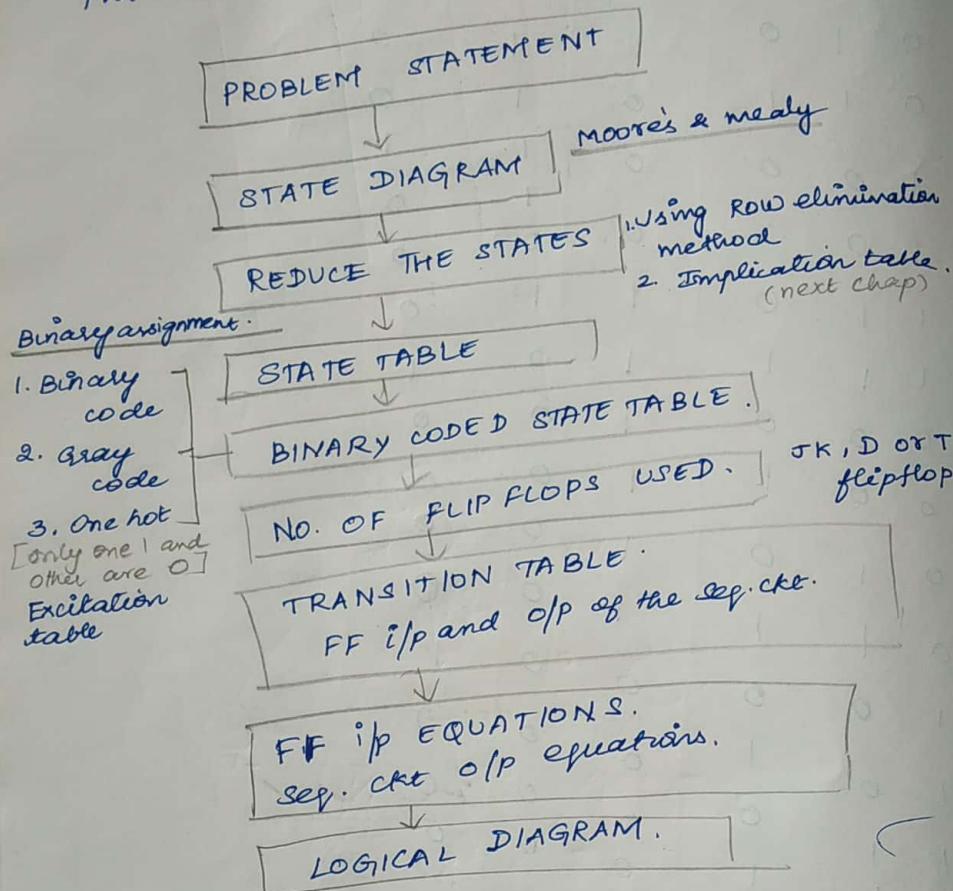

State Reduction by Row elim method

- ① → Assume some i/p
a → initial state
2. o/p → & values for each circle (i.e) o/p
(1 and 0)


3. For the given i/p 'x' find y and states.
assume initial state as 'a'.

4. check the o/p, if o/p are same for given i/p
if same next state same o/p elim any 1

Retain

circuit

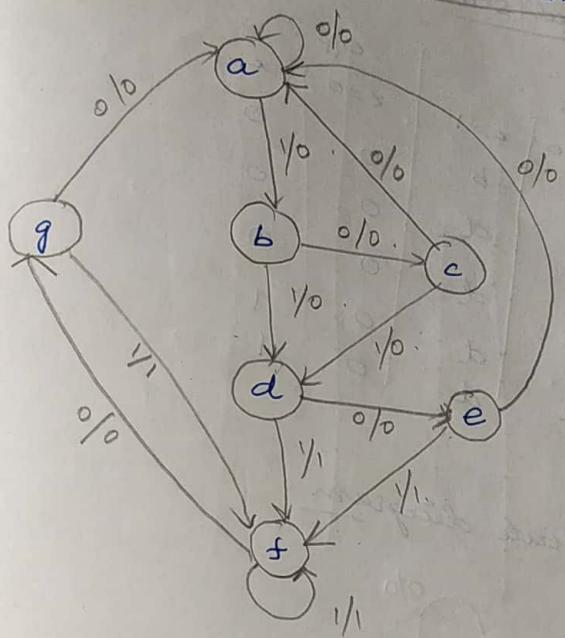State Reduction: by Row elimination Method.



for example:

states. a b d e f f f f g + f g
x 1 1 0 1 1 1 1 0 1 1 0

y 0 0 0 1 1 1 1 0 1 1 0

convert into state table (obtain same o/p)


| P.S | N.S | | O/P. | |
|-----------------|-----|-----|------|-----|
| | x=0 | x=1 | x=0 | x=1 |
| a | a | b | 0 | 0 |
| b | c | d | 0 | 0 |
| c | a | d | 0 | 1 |
| $\Rightarrow d$ | e | *d | 0 | 1 |
| $\checkmark e$ | a | *d | 0 | 1 |
| $\Rightarrow f$ | g | f | 0 | 1 |
| \cancel{g} | a | f | 0 | 1 |

Retain the g with ' \checkmark ' & f is replace with d.

Reduced state table:

| P.S | N.S | | O/P | |
|-----|-------|-------|-------|-------|
| | $x=0$ | $x=1$ | $x=0$ | $x=1$ |
| a | a | b | 0 | 0 |
| b | c | d | 0 | 0 |
| c | a | d | 0 | 0 |
| d | e | d | 0 | 1 |
| e | a | d | 0 | 1 |

Reduced state diagram.

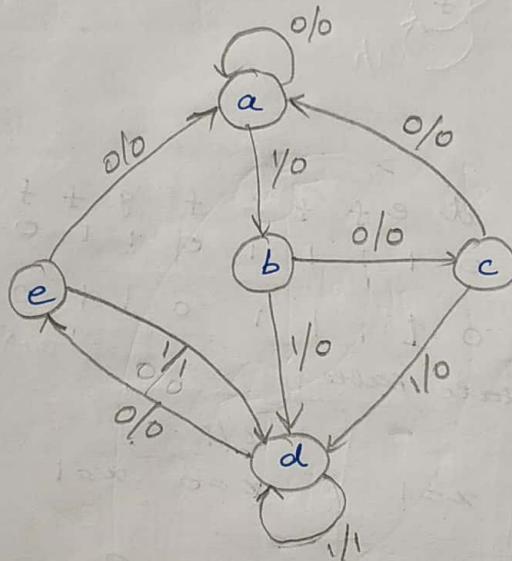

For the new state table take the same i/p combinations.

check whether $\textcircled{I} = \textcircled{II}$

states

| | a | b | c | d | e | f | g | h | i | j | k | l | m | n | o | p |
|-----|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| x = | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | |
| y = | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | |

$$\textcircled{I} = \textcircled{II}$$

The o/p of the original state table is equal to new state table.

Q.2)

| P.S | N.S | | O/P | |
|-----------------|-------|-------|-------|-------|
| | $x=0$ | $x=1$ | $x=0$ | $x=1$ |
| $\rightarrow a$ | f | b | 0 | 0 |
| $\Rightarrow b$ | d | fa | 0 | 0 |
| $\rightarrow c$ | f | eb | 0 | 0 |
| $\checkmark d$ | g | a | 1 | 0 |
| $\rightarrow e$ | d | ea | 0 | 0 |
| f | f | b | 1 | 1 |
| g | g | kd | 0 | 1 |
| $\checkmark h$ | g | a | 1 | 0 |


replace c by a
replace e by b
replace i by d.

| states | a | b | c | e | g | h | i | j | k | l | m | n | o | p |
|--------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| x = | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| o/p | 0 | 0 | 0 | 0 | | | | | | | | | | |

| states | a | f | b | c | e | g | h | i | j | k | l | m | n | o | p |
|--------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|-----|
| x | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | → Q |
| o/p | 0 | 1 | 0 | 0 | ? | | | | | | | | | | |

Reduced state table

| P.S | N.S | | O/P | | |
|-----|-------|-------|-------|-------|-----|
| | $x=0$ | $x=1$ | $x=0$ | $x=1$ | |
| a | f | b | 0 | 0 | (T) |
| b | d | a | 0 | 0 | |
| d | g | a | 1 | 0 | |
| f | f | b | 1 | 1 | |
| g | g | d | 0 | 1 | |

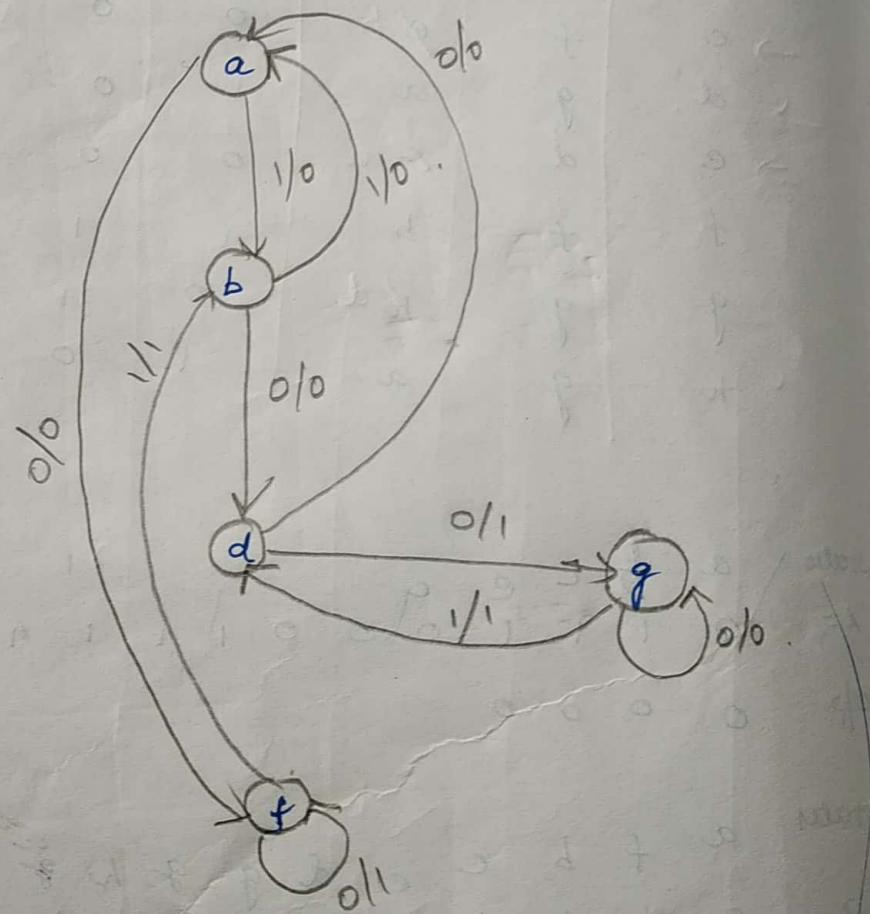

| states | a | f | b | a | b | d | g | f | d | a | b | a | f |
|--------|---|---|---|---|---|---|---|---|---|---|---|---|---|
| x | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 |
| O/P | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| | | | | | | | | | | | | | |

$\textcircled{I} = \textcircled{II} \rightarrow \textcircled{III}$

Binary Assignment.

Binary
 (depends on no of states)
 \Rightarrow no of bits
 $n \rightarrow 2^n$
 $5 \rightarrow 2^3$
 $\therefore n \Rightarrow 3$
 Minimum bits required $\Rightarrow 3$
 $n=2$ (not possible)

| | | |
|---|-------|-------|
| a | 0 0 0 | 0 0 0 |
| b | 0 0 1 | 0 0 1 |
| c | 0 1 0 | 0 1 1 |
| d | 0 1 1 | 0 1 0 |
| e | 1 0 0 | 1 1 0 |

Gray
 [1 bit variation]

one hot
 → logic '1' represents hot bit
 → It consists of 'n' number of bits
 → consists of 1 hot bit

[we use 10 flip flop when $2^n=10$]

| |
|-----------|
| 0 0 0 0 1 |
| 0 0 0 1 0 |
| 0 0 1 0 0 |
| 0 1 0 0 0 |
| 1 0 0 0 0 |

Here $2^n=5$
 \Rightarrow we need 5 flip flops]

27/09/18

Excitation table.

① In SR flip flop, we have to find S, R values

R value can be anything

| $q(t)$ | $q(t+1)$ | S | R |
|--------|----------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | 0 |

From JK flip flop

char table:

| $q(t)$ | J | K | $q(t+1)$ |
|--------|---|---|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

JK ft

| $q(t)$ | $q(t+1)$ | J | K |
|--------|----------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | | |

① D ff char table.

| $Q(t)$ | D | $Q(t+1)$ |
|--------|---|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

T flip flop char table

Q/P DD

D FF

| $Q(t)$ | $Q(t+1)$ | D |
|--------|----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

4. T flip flop char table.

| $Q(t)$ | T | $Q(t+1)$ |
|--------|---|----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

T-ff

| $Q(t)$ | $Q(t+1)$ | T | Q(t+1) |
|--------|----------|---|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |

Q. Design a sequential logic circuit to detect the sequence of 3 consecutive one's or more. Use D flip flop.

(16m)

Soln:

1 1 1

[single I/P and single O/P
⇒ sequence detector]

Initial state
assume as 'a'.

If it receives 1 → goes to new state


If it receives 0 → it is in its own state

Sequence of bits:
0 1 1 1 0 1 1 1 1 0 1 0 1 1 1 0
0 1 0 0 0 1 1 0 0 0 0 0 1 0 0 0


From LSB

for 3 and more than 3
is it is written as
rest are 0]


Mealy State Diagram m/c

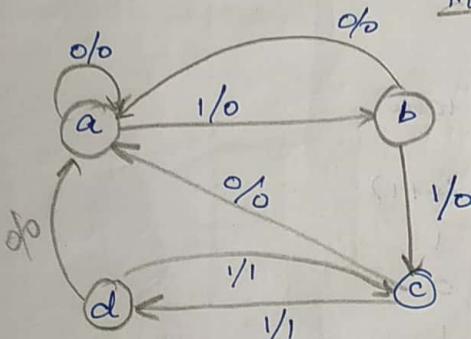

Moore State Diagram m/c.

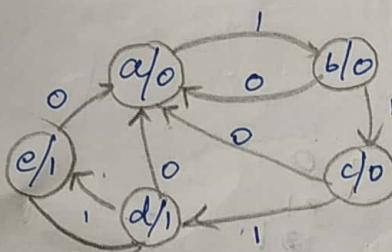

For example → overlapping

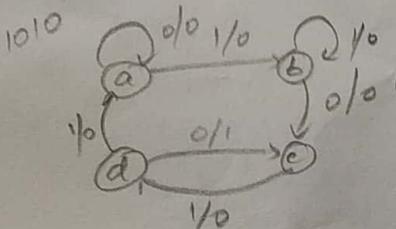

10 10 10
000101

From M

state

PS

a
00

b
01

c
10

d
11

Trans

| P | S |
|------|-----|
| A(0) | B |
| 0 a | 0 0 |
| 1 a | 0 0 |
| 2 b | 0 1 |
| 3 b | 0 1 |
| 4 c | 1 0 |
| 5 c | 1 0 |
| 6 d | 1 1 |
| 7 d | 1 1 |

From Mealy state m/c.
Take i/p as x .

state table :

| PS | x | NS | Output z |
|----|-----|----|------------|
| a | 0 | a | 0 |
| a | 1 | b | 0 |
| b | 0 | a | 0 |
| b | 1 | c | 0 |
| c | 0 | a | 0 |
| c | 1 | d | 1 |
| d | 0 | a | 0 |
| d | 1 | c | 1 |

$2^n = 4$
 $n = 2$
We assign 2 bit values

\Rightarrow no of flip flops

Transition table :

| P A(t) | S B(t) | x | NB A(t+1) | BS B(t+1) | O/P Z | D _A | D _B |
|-----------|-----------|-----|--------------|--------------|-------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| a | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| b | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| b | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| c | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| c | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| d | 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| d | 1 | 1 | 1 | 0 | 1 | 1 | 0 |

PS X as i/p draw 3 variable k map
for Z.

| | | B(t)x | | | | |
|------|--|-------|----|----|----|---|
| | | 00 | 01 | 11 | 10 | |
| A(t) | | 0 | 0 | 0 | 0 | 0 |
| | | 1 | 0 | 1 | 1 | 0 |
| | | | 4 | 5 | 7 | 6 |

$$Z = Ax.$$

for DA

| | | B(t)x | | | | |
|------|--|-------|----|-----|----|---|
| | | 00 | 01 | 101 | 10 | |
| A(t) | | 0 | 0 | 0 | 0 | |
| | | 1 | 0 | 1 | 1 | |
| | | | 4 | 5 | 7 | 6 |

$$\begin{aligned}
 DA &= \overline{A(t)} \overline{B(t)} \overline{x} + B(t) \overline{x} \\
 &= A(t) \overline{B(t)} \\
 &= A(t)x + Bx \\
 &= x(A+B)
 \end{aligned}$$


for DB

B

| | | B(t)x | | | | |
|------|--|-------|----|----|----|---|
| | | 00 | 01 | 11 | 10 | |
| A(t) | | 0 | 0 | 0 | 0 | |
| | | 1 | 0 | 1 | 1 | |
| | | | 4 | 5 | 7 | 6 |

$$DB = \overline{B}x.$$

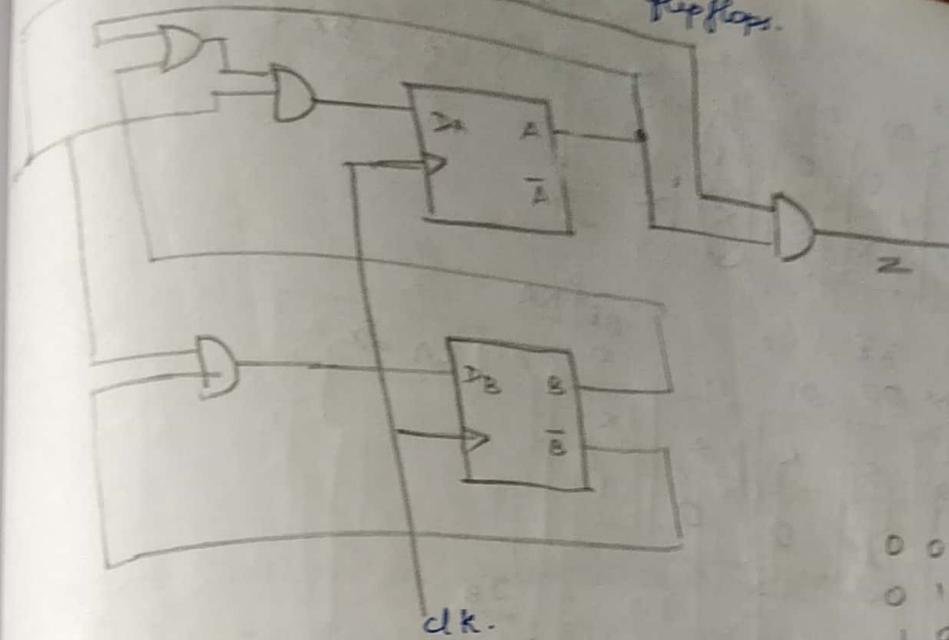since $n=2$, we have to draw 2 flipflops.



| | | | |
|---|---|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | A |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

By using ~~-S~~ JK flipflop. for same α .

| P A(t) B(t) | S A(t+1) B(t+1) | O/P Z | JA | KA | JB | KB | |
|-------------------|-----------------------|----------|----|----|----|----|---|
| 0 0 0 | 0 0 | 0 | 0 | X | 0 | X | 0 |
| 0 0 1 | 0 1 | 0 | 0 | X | 1 | X | 1 |
| 0 1 0 | 0 0 | 0 | 0 | X | X | 1 | 2 |
| 0 1 1 | 1 0 | 0 | 1 | X | X | 0 | 3 |
| 1 0 0 | 0 0 | 0 | X | 1 | 0 | X | 4 |
| 1 0 1 | 1 1 | 0 | 1 | X | 1 | X | 5 |
| 1 1 0 | 0 0 | 1 | X | 0 | X | 1 | 6 |
| 1 1 1 | 1 0 | | | | | | 7 |

RAJ

Q)

solt:

$A \begin{matrix} Bx \\ \bar{Bx} \end{matrix}$

| | 00 | 01 | 11 | Bx | JA |
|---|----|----|----|----|-----------|
| 0 | 0 | 0 | 1 | 0 | $JA = Bx$ |
| 1 | X | X | X | X | |

$\bar{A} \begin{matrix} B\bar{x} \\ Bx \end{matrix}$


| | 00 | 01 | 11 | B\bar{x} | KA |
|---|----|----|----|----------|----------------|
| 0 | X | X | X | X | $KA = \bar{x}$ |
| 1 | 1 | 0 | 0 | 1 | |

$A \begin{matrix} Bx \\ \bar{Bx} \end{matrix}$

| | 00 | 01 | 11 | 10 | JB |
|---|----|----|----|----|----------|
| 0 | X | 1 | X | X | $JB = x$ |
| 1 | 0 | 1 | X | X | |


$\bar{A} \begin{matrix} Bx \\ \bar{Bx} \end{matrix}$

| | 00 | 01 | 11 | Bx | B\bar{x} | KB |
|---|----|----|----|----|----------|----------|
| 0 | X | X | 1 | 1 | 1 | $KB = 1$ |
| 1 | X | X | X | 1 | 1 | |

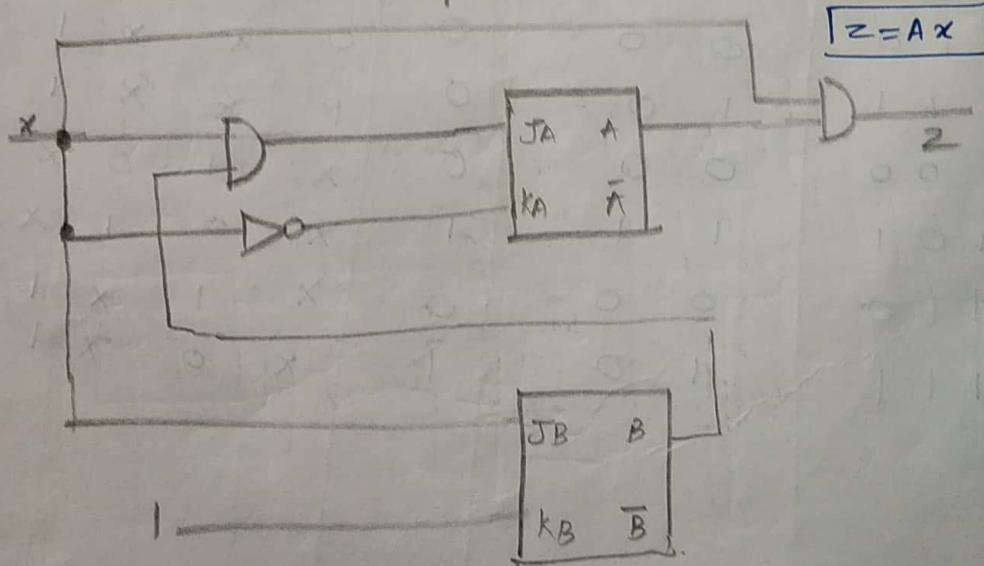

Design a sequential logic ckt to detect the sequence of 1101. Use T flip flop.


Soln:-

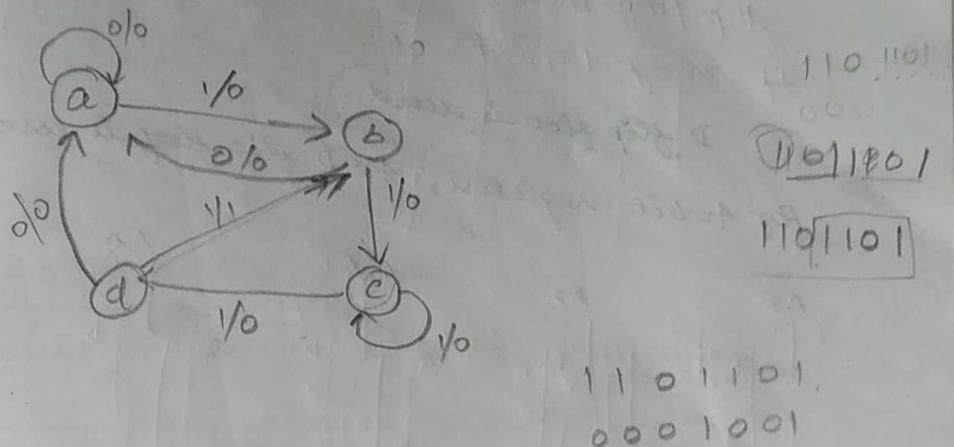

3. Detect Design a sequential logic ckt that with 2 JK flipflops A and B and 2 i/p E and F.

If $E=0$, the circuit remains in the same state regardless of the value of F. When $E=1$ and $F=1$, the ckt goes through the state transitions from 00 to 01, to 10, to 11, back to 00 and repeats. When $E=1$ and $F=0$, the ckt goes through the state transitions from 00 to 11, to 10, to 01, back to 00 and repeats.

Soln:-

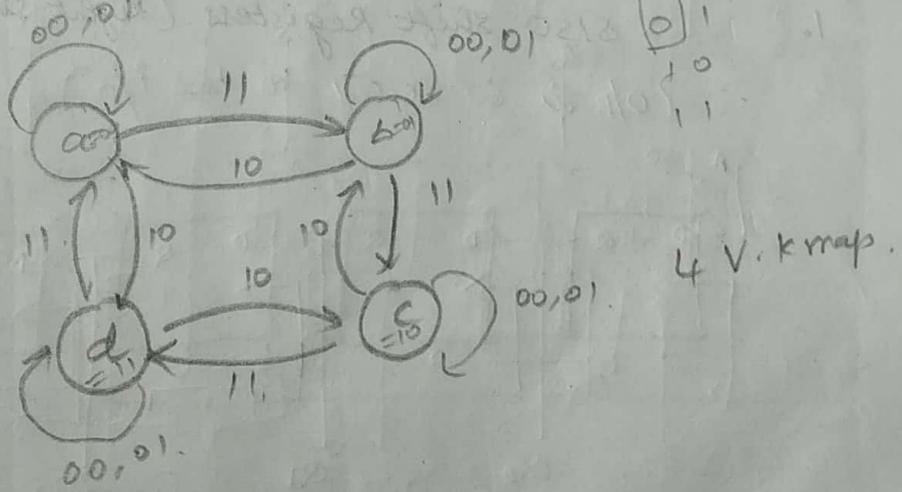

05/10/18


Registers.

flip flop \rightarrow store 1 bit info

If many flipflops \rightarrow registers.

D flip flop is used.

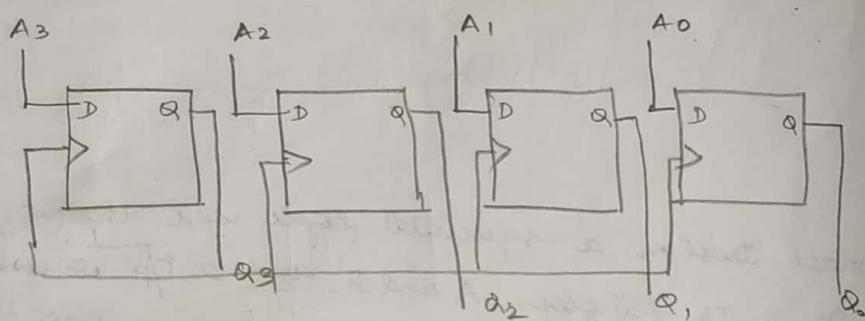For 4-bit registers, 4-D flip flop is used.




Shift registers:

1. serial in serial out - SISO
2. " " parallel " - PSIPO
3. parallel in serial out - PISO
4. parallel in parallel out - PIPO

shift registers (2 operations)

left shift Right shift.

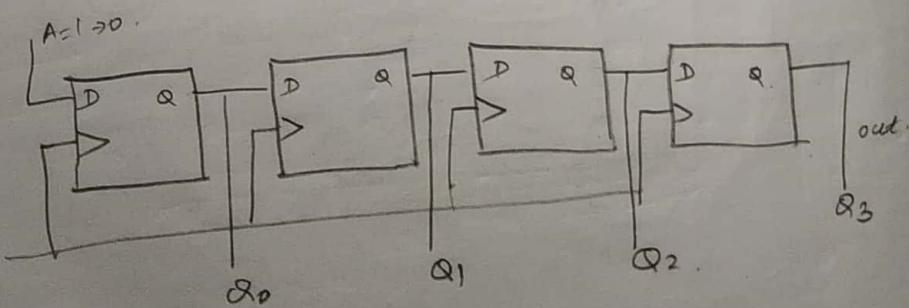1. SISO shift Registers. (right shift)
(O/P is connected to the I/P)




| clk | Q ₀ | Q |
|-----|----------------|---|
| 1 | 1 | 0 |
| 2 | 1 | 1 |
| 3 | 1 | 1 |
| 4 | 0 | 1 |
| 5. | 0 | 0 |

O/p \rightarrow Q₃
O/P \rightarrow Q₀ Q

2. serial

and it

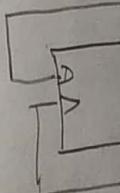

| clk |
|-----|
| 1 |
| 2 |
| 3 |
| 4 |
| 5 |

| clk | Q_0 | Q_1 | Q_2 | Q_3 |
|-----|-------|-------|-------|-------|
| 1 | 1 | 0 | 0 | 0 |
| 2 | 1 | 1 | 0 | 0 |
| 3 | 1 | 1 | 1 | 0 |
| 4 | 0 | 1 | 1 | 1 |
| 5. | 0 | 0 | 1 | 1 |


O/p $\rightarrow Q_3 \rightarrow$ SISO

O/P $\rightarrow Q_0, Q_1, Q_2, Q_3 \rightarrow$ SIPO

2. serial in parallel out (left shift)

i/p is given to the last flip flop.
and it is feed back to the previous feed back.


serial in
 $A = 1/0$

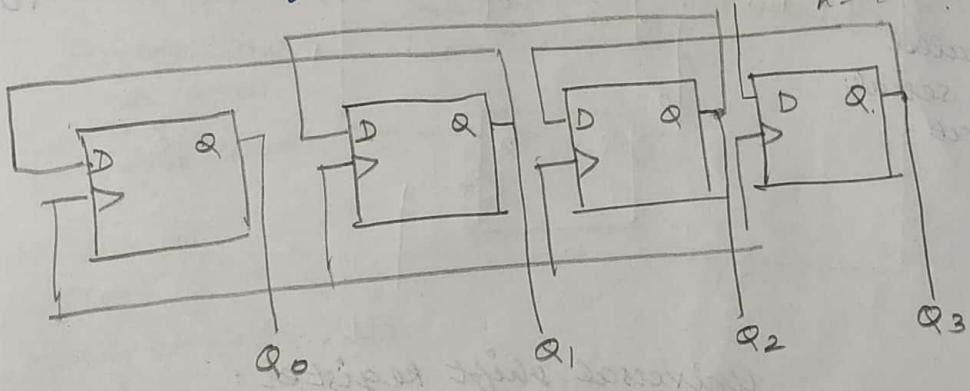


| clk | Q_0 | Q_1 | Q_2 | Q_3 |
|-----|-------|-------|-------|-------|
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 1 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 1 | 1 | 0 |
| 5 | 1 | 1 | 1 | 1 |

when i/p is $A_1 \rightarrow 0$
 $A = 0$.


without using shift register.

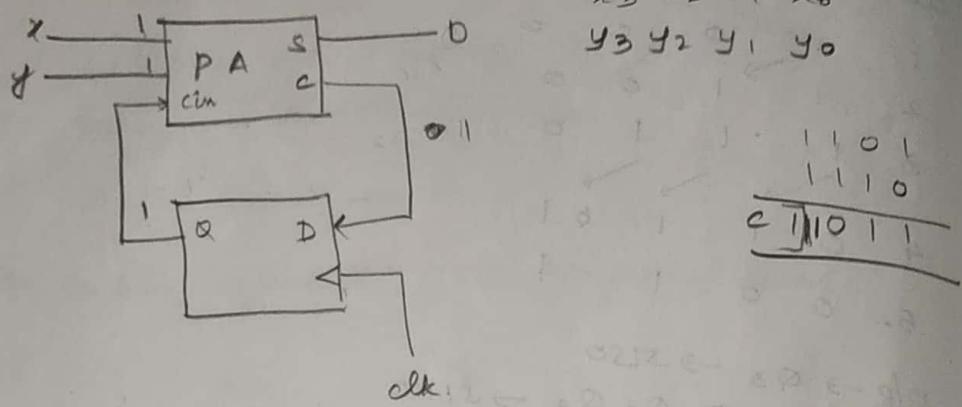

After using shift registers..

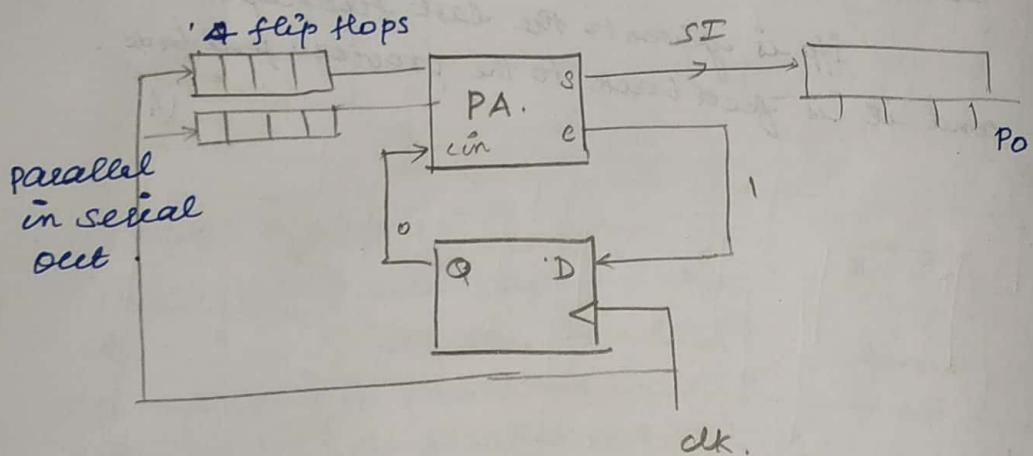

universal shift register:

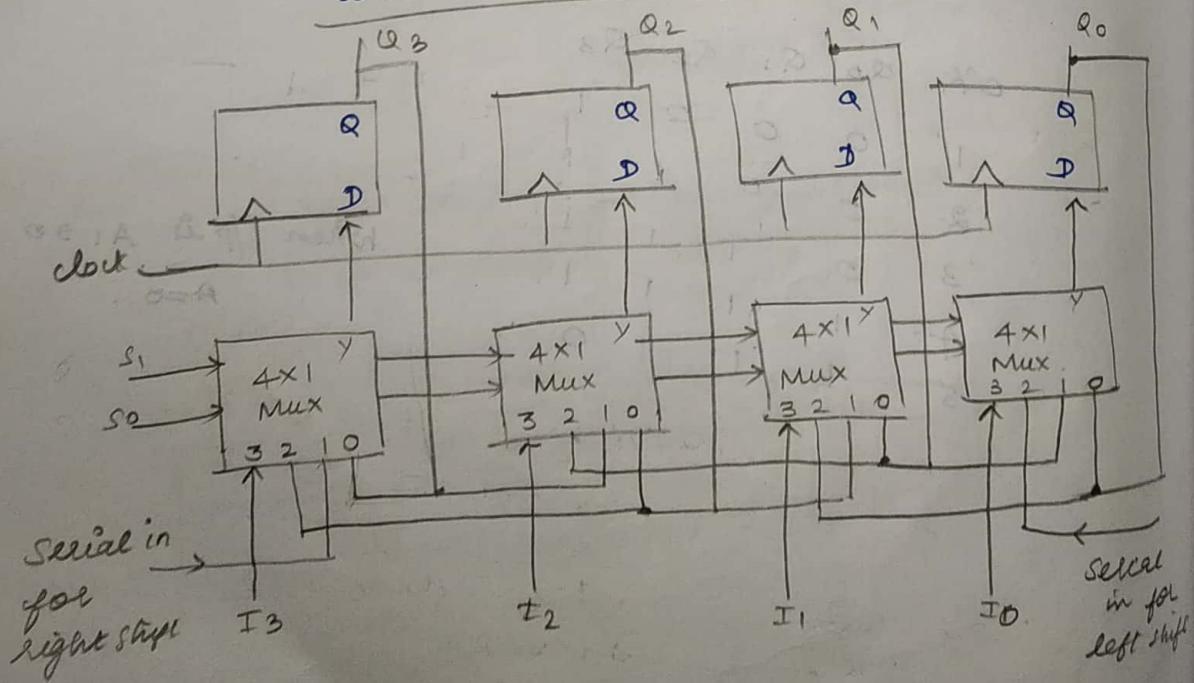

$I_1, I_2, I_3, I_0 \rightarrow$ parallel inputs.

| S_1 | S_0 | |
|-------|-------|-----------------------------|
| 0 | 0 | No change. |
| 0 | 1 | Right shift (serial in) |
| 1 | 0 | Left shift (serial in) |
| 1 | 1 | (parallel in) serial out |


No of clock = No of shift

$$\begin{array}{l} 00 \rightarrow 0 \\ 01 \rightarrow 1 \\ 10 \rightarrow 2 \\ 11 \rightarrow 3 \end{array}$$

Counters
 Asynchronous counter Synchronous counter.
 Binary [Ripple counter]

We can use JK, D, T
flip flop.

Mostly we won't use
D flip flop.

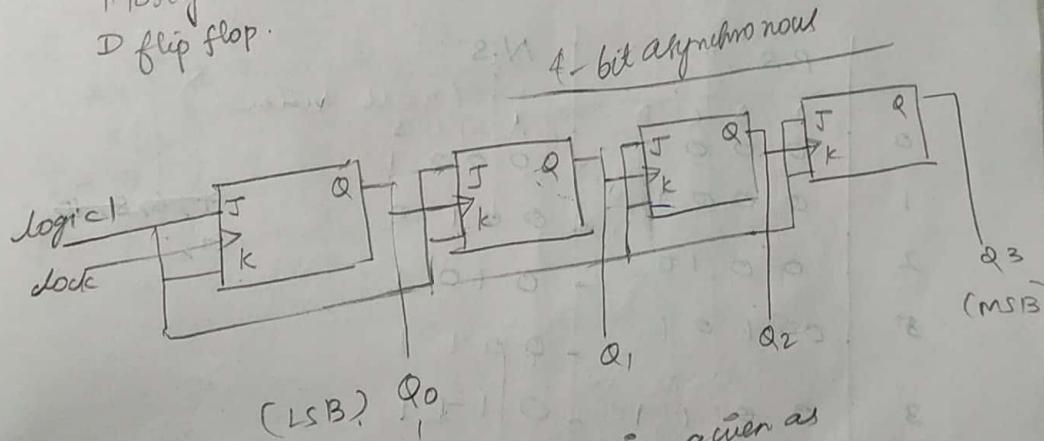

- O/P of the flip flop is given as clock for Nxt flip flop \rightarrow counter

- When there is $1 \rightarrow 0$ transition and flip flop complements the previous op. $0 \rightarrow 1$.

\Rightarrow Follows negative edge transition signal

Serial
in for
left shift

| Q_3 | Q_2 | Q_1 | Q_0 | |
|-------|-------|-------|-------|---|
| 0 | 0 | 0 | 0 | complement for a clock |
| 0 | 0 | 0 | 1 | previous value retained |
| 0 | 0 | 1 | 0 | → 0 to 1 transition, there is no 1 to 0 transition |
| 0 | 0 | 1 | 1 | |
| 0 | 1 | 0 | 0 | |
| 0 | 1 | 0 | 0 | |

To obtain +ve edge trigger
get output from \bar{Q} instead of Q .

SYNCHRONOUS COUNTER

4-bit synchronous counter

current sequence:

0
1
2
5
3
7
9
15

{ regular

4, 6, 8, 10, 11, 12, 13, 14
→ Don't cares.

0
1
2
5
3
7
9
15

AB
00
01
11
10

AB
00
01

AB
00
01

AB
11
10

AB
00
01

AB
00
01

| | P.S | | | | N.S (next values) | | | |
|----|-----|---|---|---|----------------------|---|---|---|
| | A | B | C | D | A | B | C | D |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 2 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 5 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 3 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 15 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

at least
4 bits are
required
for represent.

| | JA | KA | JB | KB | Jc | Kc | JD | KD |
|----|-----|-----|-----|-----|-----|-----|-----|--------|
| 0 | 0 X | 0 X | 0 X | 0 X | 0 X | 0 X | 1 X | |
| 1 | 0 X | 0 X | 1 X | | 1 X | X 1 | X 1 | 00 0X |
| 2 | 0 X | | X 1 | | X 1 | | 1 X | 01 1X |
| 5 | 0 X | | 1 X | | 1 X | | X 0 | 10 X 1 |
| 8 | 1 X | | X 1 | | X 0 | | X 0 | 11 X 0 |
| 7 | | | 1 X | | X 1 | | X 0 | |
| 9 | X 0 | | X 1 | | X 1 | | X 1 | |
| 15 | X 1 | | X 1 | | | | | |

13, 14

| | AB | CD | JA |
|----|-----|-------------|----|
| | 00 | 00 01 11 10 | |
| 00 | 0 | 0 0 0 0 | |
| 01 | X 0 | 1 X | |
| 11 | X X | X X | |
| 10 | X X | X X | |

KB

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

KA

| | AB | CD | CD | CD |
|----|-----|------------------|----|----|
| | 00 | 00 01 | 11 | 10 |
| 00 | X 0 | X 1 X 3 X 2 | | |
| 01 | X 4 | X 5 X 6 X 7 | | |
| AB | 11 | X 12 X 13 1 X 14 | | |
| 10 | X 8 | O X 11 X 10 | | |


$$KA = B$$

JB

| | AB | CD | CD | CD |
|----|------|----------------|----|----|
| | 00 | 00 01 11 10 | | |
| 00 | 0 | 0 1 3 2 | | |
| 01 | X 2 | X 5 X 7 X 8 | | |
| 11 | X 12 | X 13 X 15 X 16 | | |
| 10 | X 9 | 1 X 11 X 10 | | |


$$JB = A + C$$

07-10-18

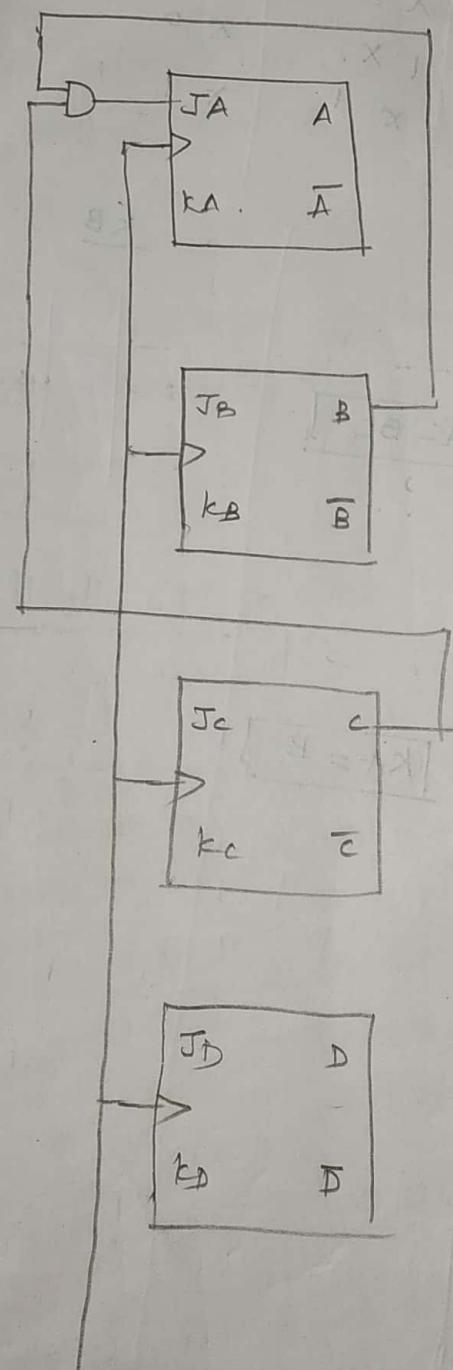

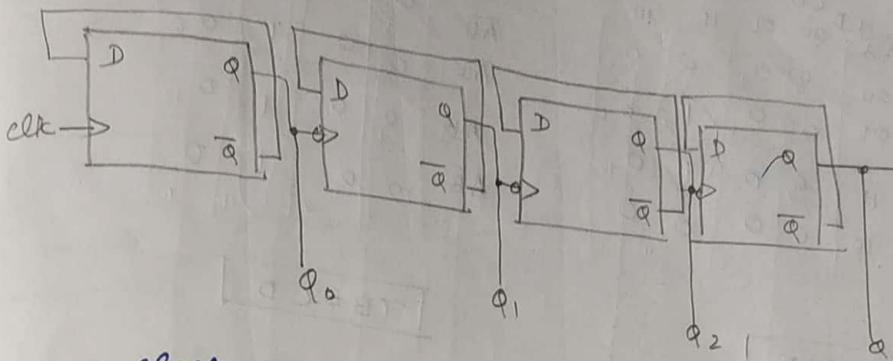1.10.18

Asynchronous binary ripple counter using Dff




clock accepts only -ve edge i-o
if +ve have to be accepted (D-Q) is connected.

Synchronous binary ripple counter

(no input, no output, only clock change)

using T flip-flop

upcount

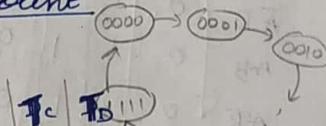

| P.S | N.S | T _A | T _B | T _C | T _D | |
|------|------|----------------|----------------|----------------|----------------|----|
| 0000 | 0001 | 00 | 0 | 0 | 1 | 0 |
| 0001 | 0010 | 0 | 0 | 0 | 1 | 1 |
| 0010 | 0011 | 0 | 0 | 1 | 1 | 2 |
| 0011 | 0100 | 0 | 1 | 1 | 1 | 3 |
| 0100 | 0101 | 0 | 0 | 0 | 1 | 4 |
| 0101 | 0110 | 0 | 0 | 0 | 1 | 5 |
| 0110 | 0111 | 0 | 0 | 1 | 1 | 6 |
| 0111 | 1000 | 1 | 0 | 0 | 1 | 7 |
| 1000 | 1001 | 0 | 0 | 1 | 1 | 8 |
| 1001 | 1010 | 0 | 0 | 0 | 1 | 9 |
| 1010 | 1011 | 0 | 0 | 1 | 1 | 10 |
| 1011 | 1100 | 0 | 1 | 0 | 1 | 11 |
| 1100 | 1101 | 0 | 0 | 0 | 1 | 12 |
| 1101 | 1110 | 0 | 0 | 0 | 1 | 13 |
| 1110 | 1111 | 0 | 0 | 1 | 1 | 14 |
| 1111 | 0000 | 1 | 0 | 1 | 1 | 15 |

TA

| | CD | $\bar{C}D$ | $\bar{D}C$ | CD | $C\bar{D}$ |
|------------------|----|------------|------------|----|------------|
| AB | 00 | 01 | 11 | 10 | 02 |
| $\bar{A}\bar{B}$ | 00 | 01 | 0 | 02 | 0 |
| $\bar{A}B$ | 01 | 0 | 5 | 17 | 06 |
| AB | 11 | 02 | 03 | 15 | 04 |
| A \bar{B} | 10 | 0 | 0 | 0 | 0 |

TB

| | CD | $\bar{C}D$ | $\bar{D}C$ | CD | $C\bar{D}$ |
|------------------|----|------------|------------|----|------------|
| AB | 0 | 0 | 1 | 0 | 2 |
| $\bar{A}\bar{B}$ | 0 | 0 | 5 | 1 | 06 |
| $\bar{A}B$ | 04 | 05 | 1 | 06 | 0 |
| AB | 02 | 03 | 13 | 14 | 04 |
| A \bar{B} | 0 | 0 | 1 | 0 | 0 |

$$TA = BCD$$

$$| TB = CD$$

TC

| | CD | $\bar{C}D$ | $\bar{D}C$ | CD | $C\bar{D}$ |
|------------------|----|------------|------------|----|------------|
| AB | 00 | 11 | 1 | 0 | 2 |
| $\bar{A}\bar{B}$ | 00 | 15 | 1 | 06 | 0 |
| $\bar{A}B$ | 08 | 19 | 11 | 10 | 0 |
| A \bar{B} | 02 | 13 | 14 | 0 | 15 |

| | CD | $\bar{C}D$ | $\bar{D}C$ | CD | $C\bar{D}$ |
|------------------|----|------------|------------|----|------------|
| AB | 1 | 1 | 1 | 1 | 1 |
| $\bar{A}\bar{B}$ | 1 | 1 | 1 | 1 | 1 |
| $\bar{A}B$ | 1 | 1 | 1 | 1 | 1 |
| AB | 1 | 1 | 1 | 1 | 1 |
| A \bar{B} | 1 | 1 | 1 | 1 | 1 |

$$| TC = D$$


$$| TD = 1$$

For n-bit counters.

v w x y z

| \bar{v} | \bar{w} | \bar{x} | \bar{y} | \bar{z} |
|-------------------|------------------|-----------------|----------------|----------------|
| $\frac{TV}{wxyz}$ | $\frac{Tw}{xyz}$ | $\frac{Tx}{yz}$ | $\frac{Ty}{z}$ | $\frac{Tz}{1}$ |
| ... | ... | ... | ... | ... |

LOGIC DIAGRAM.

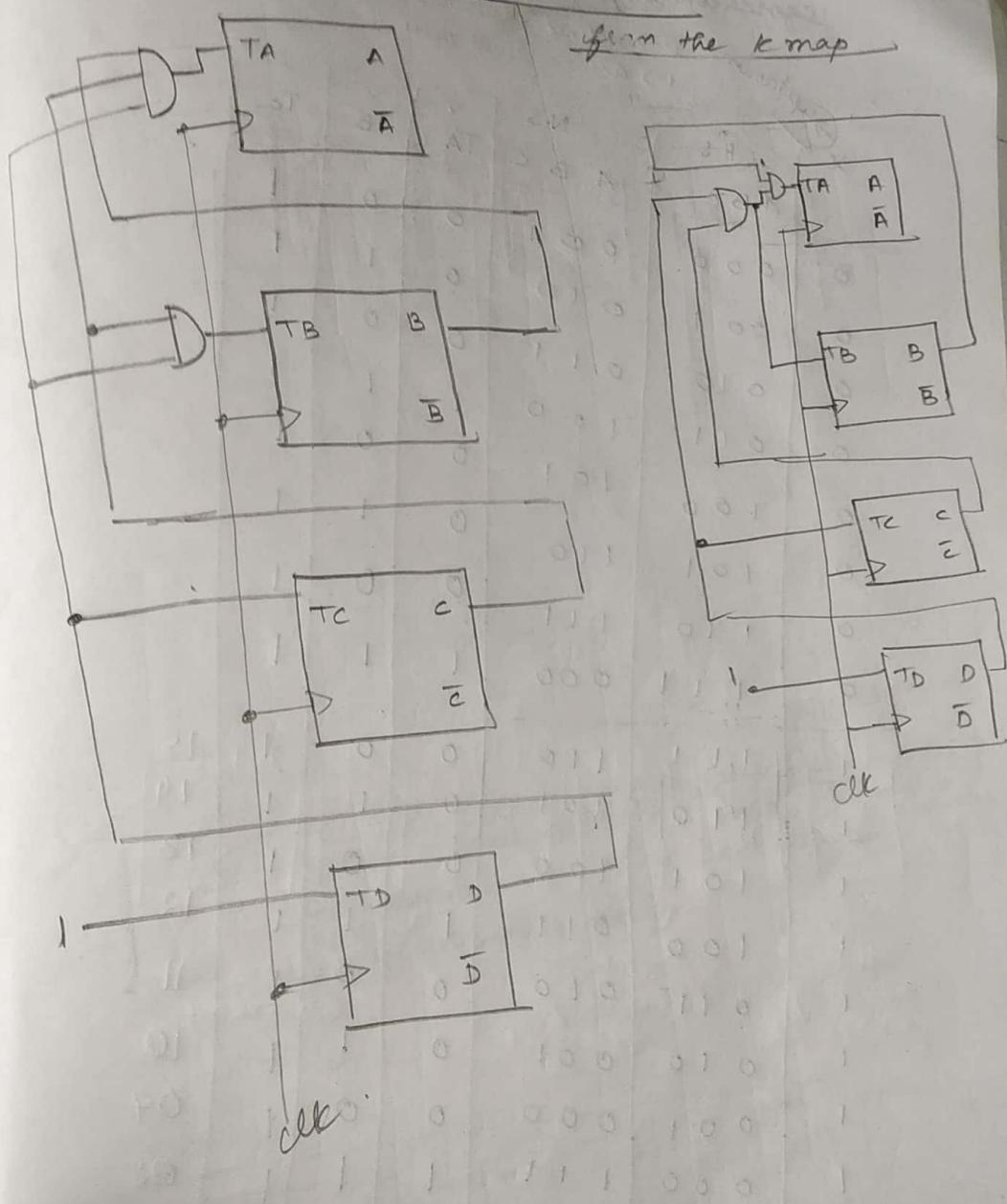

| Q ₃ | Q ₂ | Q ₁ | Q ₀ | A ₃ | A ₂ | A ₁ | A ₀ | AT |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0000 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0001 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0010 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0011 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0100 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0101 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0110 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0111 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1000 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1001 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1010 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1011 |
| 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1100 |
| 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1101 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1110 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1111 |

$$\begin{aligned}
 & Q_3 + Q_2 \\
 & Q_3 + Q_1 \\
 & Q_3 + Q_0 \\
 & Q_2 + Q_1 \\
 & Q_2 + Q_0 \\
 & Q_1 + Q_0
 \end{aligned}$$

3bit synchronous up/down counter using T-ff.

$x \rightarrow$ up/down
0 → assume up count.
1 → assume down count

| x | P.S | NS | | | TA | TB | TC | Q(T) |
|---|-----|-----|---|---|----|----|----|------|
| | | A | B | C | | | | |
| 0 | 000 | 001 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 001 | 010 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 010 | 011 | 0 | 0 | 1 | 1 | 1 | 2 |
| 0 | 011 | 100 | 1 | 1 | 1 | 1 | 1 | 3 |
| 0 | 100 | 101 | 0 | 0 | 1 | 1 | 1 | 4 |
| 0 | 101 | 110 | 0 | 1 | 1 | 1 | 1 | 5 |
| 0 | 110 | 111 | 0 | 0 | 1 | 1 | 1 | 6 |
| 0 | 111 | 000 | 1 | 1 | 1 | 1 | 1 | 7 |
| 1 | 111 | 110 | 0 | 0 | 1 | 1 | 1 | 85 |
| 1 | 110 | 101 | 0 | 1 | 1 | 1 | 1 | 94 |
| 1 | 101 | 100 | 0 | 0 | 1 | 1 | 1 | 13 |
| 1 | 100 | 011 | 1 | 1 | 1 | 1 | 1 | 12 |
| 1 | 011 | 010 | 0 | 0 | 1 | 1 | 1 | 14 |
| 1 | 010 | 001 | 0 | 1 | 1 | 1 | 1 | 10 |
| 1 | 001 | 000 | 0 | 0 | 0 | 1 | 1 | 09 |
| 1 | 000 | 111 | 1 | 1 | 1 | 1 | 1 | 08 |

| | $\bar{B}C$ | $\bar{B}\bar{C}$ | TA |
|-------------|------------|------------------|------------|
| X_A | $\bar{B}C$ | $\bar{B}C$ | $\bar{B}C$ |
| \bar{X}_A | 0, 0 | 1, 0 | 0 |
| X_A | 0, 1 | 1, 0 | 0 |
| \bar{X}_A | 1, 0 | 0, 1 | 0 |

$$\begin{aligned}
 TA &= \bar{X}BC + \bar{X}\bar{B}\bar{C} \\
 &= \cancel{B} \oplus C \\
 &= \bar{X}BC + X\bar{B}\bar{C}
 \end{aligned}$$

| | $\bar{B}C$ | $\bar{B}\bar{C}$ | TB |
|-------------|------------|------------------|------------|
| X_A | $\bar{B}C$ | $\bar{B}C$ | $\bar{B}C$ |
| \bar{X}_A | 0, 0 | 1, 1 | 0 |
| X_A | 0, 1 | 1, 1 | 0 |
| \bar{X}_A | 1, 0 | 0, 0 | 1 |

$$\begin{aligned}
 TB &= C\bar{X} + X\bar{C} \\
 &= X \oplus C
 \end{aligned}$$


| | $\bar{B}C$ | $\bar{B}\bar{C}$ | TC |
|-------------|------------|------------------|------------|
| X_A | $\bar{B}C$ | $\bar{B}C$ | $\bar{B}C$ |
| \bar{X}_A | 1, 1 | 1, 1 | 1 |
| X_A | 1, 1 | 1, 1 | 1 |
| \bar{X}_A | 1, 1 | 1, 1 | 1 |

$$TC = 1$$

$$TA = \bar{x}BC + x\bar{B}c$$

$$TB = x \oplus c \Rightarrow x\bar{c} + \bar{x}c$$

$$TC = 1.$$

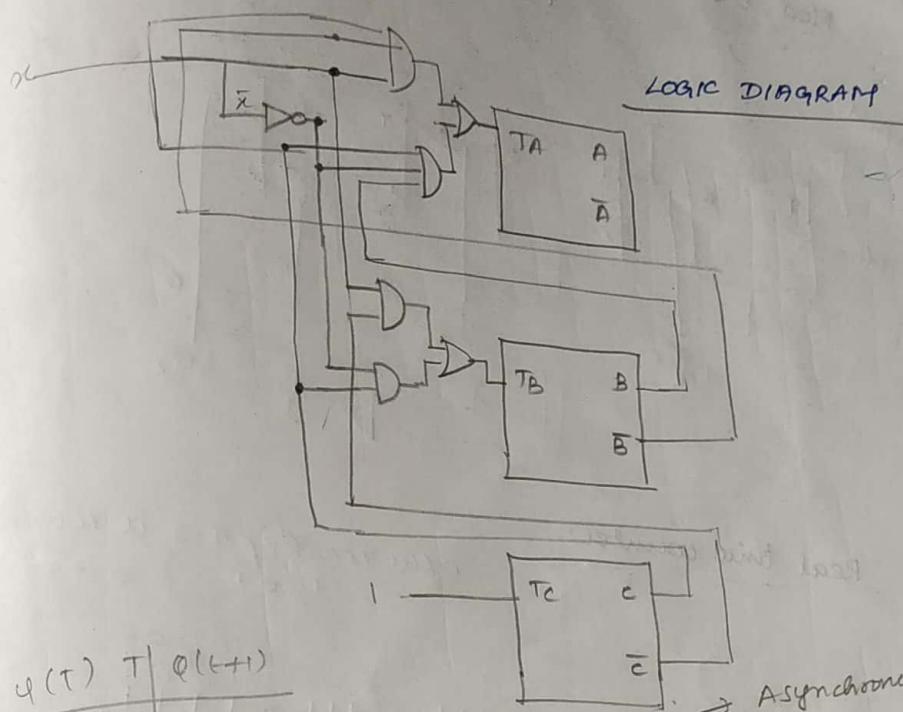


| $Q(T)$ | T | $Q(T+1)$ |
|--------|-----|----------|
| 0 0 0 | 0 | 0 0 0 |
| 0 0 1 | 1 | 0 0 1 |
| 0 1 0 | 0 | 0 1 0 |
| 0 1 1 | 1 | 0 1 1 |
| 1 0 0 | 0 | 1 0 0 |
| 1 0 1 | 1 | 1 0 1 |
| 1 1 0 | 0 | 1 1 0 |
| 1 1 1 | 1 | 1 1 1 |

BCD Ripple counter (Decade counter)
use either JK or T or $\text{Mod } 10$ counter

Asynchronous \rightarrow direct gate diagram.
Synchronous \rightarrow design

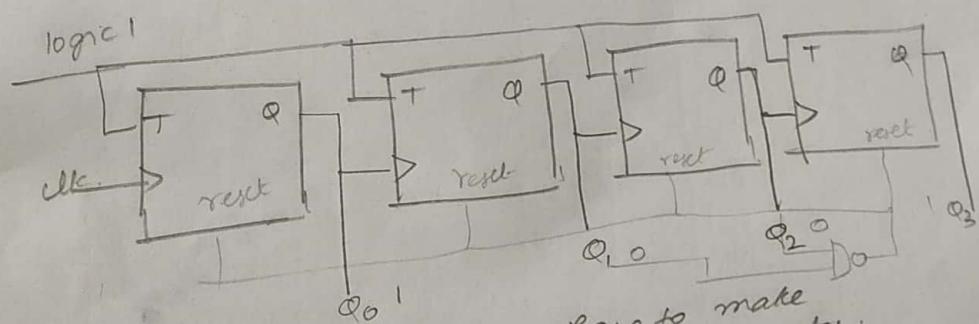$0 \text{ to } 9$ (4 bits) \rightarrow 4 flip flops.



From the above we have to make
BCD ripple counter.

0 0 0 0 for

1 0 0 1


0 0 0 0

(Reset \rightarrow accepts
active low)
(Preset \rightarrow active
low)

Mod - 5 counter

(3 bits enough)

For Mod 10
(4 bits)

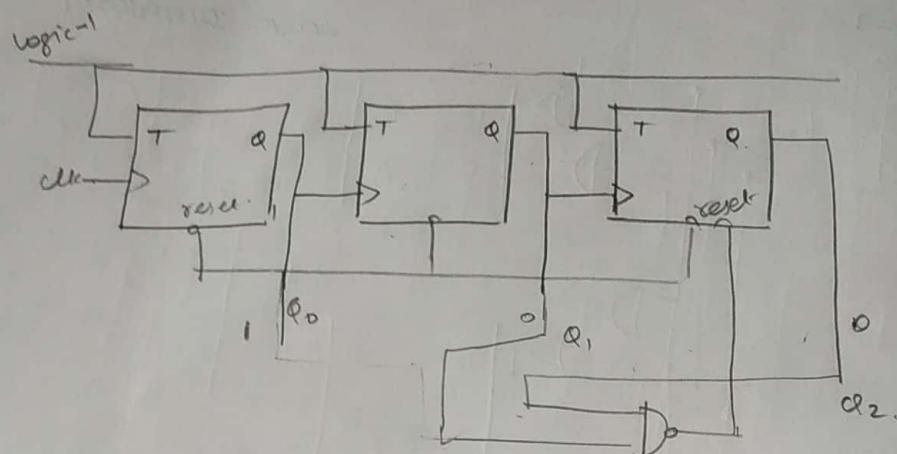

Real time counter:

after reaching 9 \rightarrow it becomes
1001 0000

