

**Problem 1**

For each of the following functions, find all of the prime implicants, using the Quine-McCluskey method.

(a)  $f(a, b, c, d) = \Sigma m(1, 5, 7, 9, 11, 12, 14, 15)$

(b)  $f(a, b, c, d) = \Sigma m(0, 1, 3, 5, 6, 7, 8, 10, 14, 15)$

**Problem 2**

A sequential circuit has three  $D$  flip-flops,  $A$ ,  $B$ , and  $C$ , and one input,  $x$ . It is described by the following flip-flop input functions:

$$DA = (BC' + B'C)x + (BC + B'C')x'$$

$$DB = A$$

$$DC = B$$

- (a) Derive the state table for the circuit.
- (b) Draw two state diagrams: one for  $x = 0$  and the other for  $x = 1$ .

**Problem 3**

An asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the circuit are as follows:

$$Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$$

$$Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$$

$$z = x_2 + y_1$$

- (a) Draw the logic diagram of the circuit.
- (b) Derive the transition table and output map.
- (c) Obtain a flow table for the circuit.

**Problem 4**

Design a combinational circuit with three inputs and one output. The output is equal to logic-1 when the binary value of the input is less than 3. The output is logic-0 otherwise.

----


**Problem 1**

For this function, find a minimum sum-of-products solution, using the Quine-McCluskey method.

$$f(a, b, c, d) = \sum m(1, 3, 4, 5, 6, 7, 10, 12, 13) + \sum d(2, 9, 15)$$

**Problem 2**

A sequential circuit has one flip-flop,  $Q$ ; two inputs,  $x$  and  $y$ ; and one output,  $S$ . It consists of a full-adder circuit connected to a  $D$  flip-flop, as shown in Fig. P6-8. Derive the state table and state diagram of the sequential circuit.

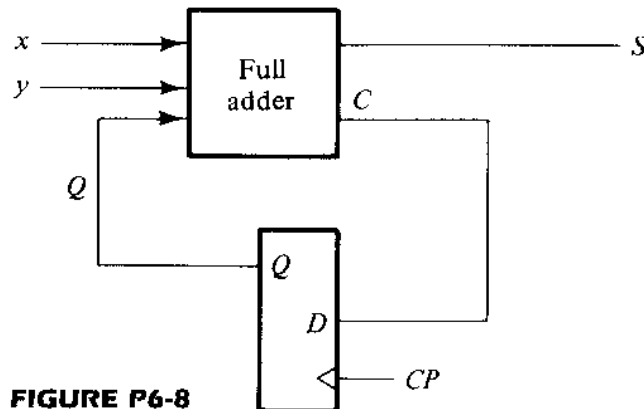

**FIGURE P6-8**

**Problem 3**

Convert the flow table of Fig. P9-5 into a transition table by assigning the following binary values to the states:  $a = 00$ ,  $b = 11$ , and  $c = 01$ .

- Assign values to the extra fourth state to avoid critical races.
- Assign outputs to the don't-care states to avoid momentary false outputs.
- Derive the logic diagram of the circuit.

	$x_1 x_2$			
	00	01	11	10
$a$	$\textcircled{a}, 0$	$b, -$	$c, -$	$\textcircled{a}, 1$
$b$	$a, -$	$\textcircled{b}, 0$	$\textcircled{b}, 0$	$c, -$
$c$	$a, -$	$b, -$	$\textcircled{c}, 1$	$\textcircled{c}, 0$

**FIGURE P9-5**

**Problem 4**

Design a combinational circuit with three inputs,  $x$ ,  $y$ , and  $z$ , and three outputs,  $A$ ,  $B$ , and  $C$ . When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input.

**Problem 1**


For each of the following functions, find all of the prime implicants using the Quine-McCluskey method.

(a)  $f(a, b, c, d) = \sum m(0, 3, 4, 5, 7, 9, 11, 13)$

(b)  $f(a, b, c, d) = \sum m(2, 4, 5, 6, 9, 10, 11, 12, 13, 15)$

**Problem 2**


A sequential circuit has one flip-flop,  $Q$ ; two inputs,  $x$  and  $y$ ; and one output,  $S$ . It consists of a full-adder circuit connected to a  $D$  flip-flop, as shown in Fig. P6-8. Derive the state table and state diagram of the sequential circuit.

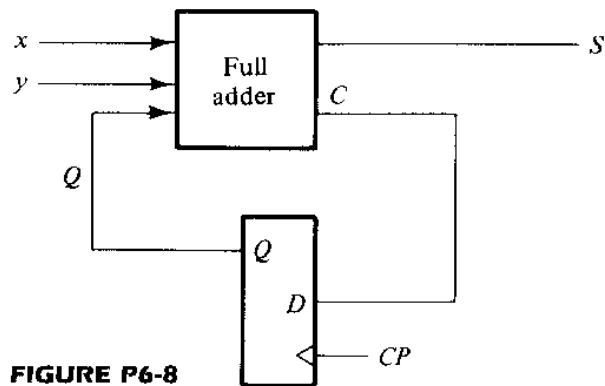

**Problem 3**

For the asynchronous sequential circuit shown in Fig. P9-9:

- (a) Derive the Boolean functions for the outputs of the two SR latches  $Y_1$  and  $Y_2$ . Note that the  $S$  input of the second latch is  $x_1' y_1'$ .
- (b) Derive the transition table and output map of the circuit.

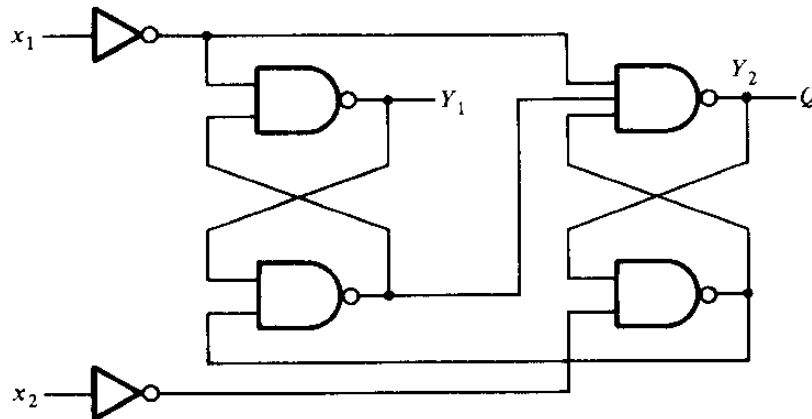

**Problem 4**

Design a combinational circuit that adds one to a 4-bit binary number,  $A_3 A_2 A_1 A_0$ . For example, if the input of the circuit is  $A_3 A_2 A_1 A_0 = 1101$ , the output is 1110. The circuit can be designed using four half-adders.

**Problem 1**

For each function, find a minimum sum-of-products solution using the Quine-McCluskey method.

(a)  $f(a, b, c, d) = \sum m(2, 3, 4, 7, 9, 11, 12, 13, 14) + \sum d(1, 10, 15)$

(b)  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 8, 9, 11, 13) + \sum d(7, 10, 12)$

**Problem 2**

Reduce the number of states in the following state table and tabulate the reduced state table.

Present State	Next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

**Problem 3**

Obtain a primitive flow table for a circuit with two inputs,  $x_1$  and  $x_2$ , and two outputs,  $z_1$  and  $z_2$ , that satisfy the following four conditions:

- (a) When  $x_1x_2 = 00$ , the output is  $z_1z_2 = 00$ .
- (b) When  $x_1 = 1$  and  $x_2$  changes from 0 to 1, the output is  $z_1z_2 = 01$ .
- (c) When  $x_2 = 1$  and  $x_1$  changes from 0 to 1, the output is  $z_1z_2 = 10$ .
- (d) Otherwise, the output does not change.

**Problem 4**

Design a combinational circuit with four inputs that represent a decimal digit in BCD and four outputs that produce the 9's complement of the input digit. The six unused combinations can be treated as don't-care conditions.

**Problem 1**


Using the Quine-McCluskey method, find all minimum sum-of-products expressions for

(a)  $f(A, B, C, D, E) = \sum m(0, 1, 2, 3, 4, 8, 9, 10, 11, 19, 21, 22, 23, 27, 28, 29, 30)$

(b)  $f(A, B, C, D, E) = \sum m(0, 1, 2, 4, 8, 11, 13, 14, 15, 17, 18, 20, 21, 26, 27, 30, 31)$

**Problem 2**

Analyze the circuit of Fig. P6-18 and prove that it is equivalent to a  $T$  flip-flop.

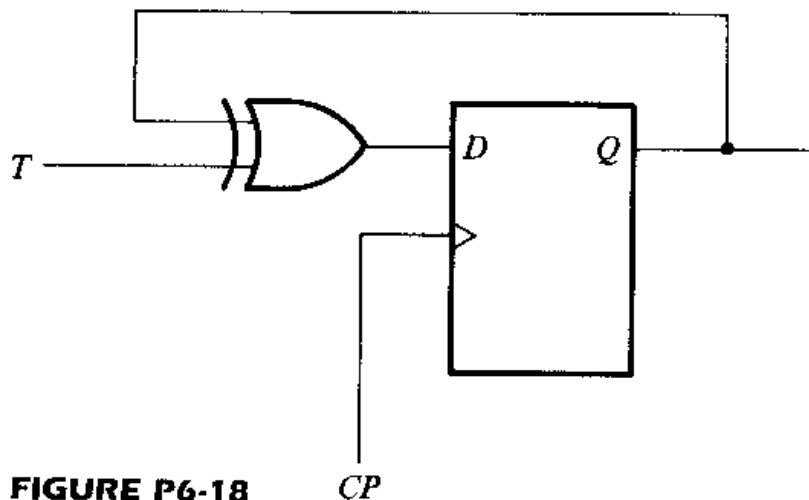

**FIGURE P6-18**

**Problem 3**

The Boolean functions for the inputs of an  $SR$  latch are as follows. Obtain the circuit diagram using a minimum number of NAND gates.

$$S = x_1'x_2'x_3 + x_1x_2x_3$$

$$R = x_1x_2' + x_2x_3'$$

**Problem 4**

Design a combinational circuit that detects an error in the representation of a decimal digit in BCD. The output of the circuit must be equal to logic-1 when the inputs contain any one of the six unused bit combinations in the BCD code.

Problem 1

- (a) Use the Quine-McCluskey method to find all prime implicants of  $f(a, b, c, d, e) = \Sigma m(1, 2, 4, 5, 6, 7, 9, 12, 13, 15, 17, 20, 22, 25, 28, 30)$ . Find all essential prime implicants, and find all minimum sum-of-products expressions.
- (b) Repeat part (a) for  $f'$ .

Problem 2

Design a sequential circuit with two  $JK$  flip-flops,  $A$  and  $B$ , and two inputs,  $E$  and  $x$ . If  $E = 0$ , the circuit remains in the same state regardless of the value of  $x$ . When  $E = 1$  and  $x = 1$ , the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00, and repeats. When  $E = 1$  and  $x = 0$ , the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00, and repeats.

Problem 3

- (a) Obtain a binary state assignment for the reduced flow table shown in Fig. P9-19. Avoid critical race conditions.
- (b) Obtain the logic diagram of the circuit using NAND latches and gates.

	$x_1, x_2$			
	00	01	11	10
$a$	$\textcircled{a}, 0$	$\textcircled{a}, 1$	$b, -$	$d, -$
$b$	$a, -$	$\textcircled{b}, 0$	$\textcircled{b}, 0$	$c, -$
$c$	$a, -$	$- , -$	$d, -$	$\textcircled{c}, 0$
$d$	$a, -$	$a, -$	$\textcircled{d}, 1$	$\textcircled{d}, 1$

**FIGURE P9-19**

Problem 4

Design a combinational circuit that converts a binary number of four bits to a decimal number in BCD. Note that the BCD number is the same as the binary number as long as the input is less than or equal to 9. The binary number from 1010 to 1111 converts into BCD numbers from 1 0000 to 1 0101.