

21.08.18.

19. Design a combinational circuit with 3 inputs and 1 output. The output is 1, ~~when~~ when the binary value of input is less than 3. The output is 0 otherwise.

⇒



x	y	z	O/P
0	0	0	1
1	0	0	1
2	0	1	1
3	0	1	0
4	1	0	0
5	1	0	0
6	1	1	0
7	1	1	0

$2^3 \rightarrow 8$ combinations
Full adder

	yz 00	yz 01	yz 11	yz 10
\bar{x} 0	1	1	0	1
x 1	0	0	0	0

$$= \bar{x}\bar{y} + \bar{x}\bar{z}$$

$$= \bar{x}(\bar{y} + \bar{z})$$

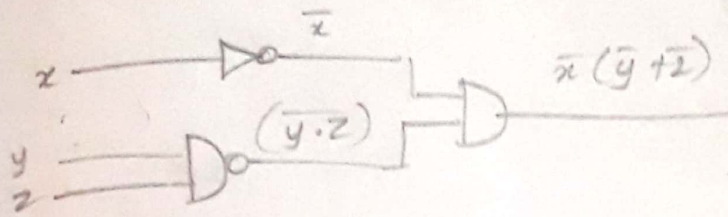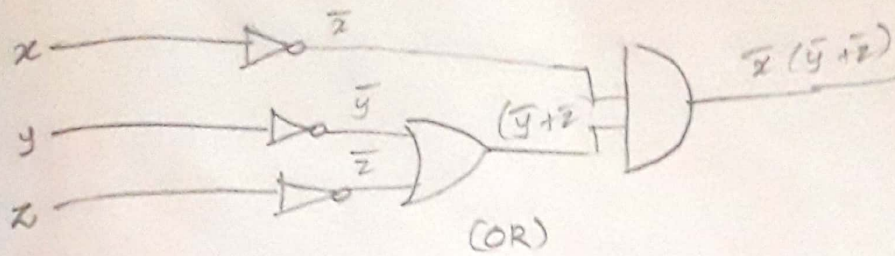

2. Q) Design a combinational circuit with 3 i/p and 1 output. The output is 1 when the binary value of i/p is even no & otherwise 0.

	x	y	z	O/P
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0

x \ yz	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$$= \bar{z}$$

